

ELEKTROTEHNIČKI FAKULTET U BEOGRADU
KATEDRA ZA ELEKTRONIKU

ENERGETSKA ELEKTRONIKA
LABORATORIJSKE VEŽBE

VEŽBA BROJ 4:
UPRAVLJANJE BUCK KONVERTOROM:
IMPULSNO-ŠIRINSKA MODULACIJA

IME I PREZIME	BR. INDEKSA	GRUPA	OCENA
1.			
2.			

DATUM _____

VREME _____

DEŽURNI U LABORATORIJU _____


D.0

$$V_0 = \underline{\hspace{2cm}} \text{ V} \quad R_X = \underline{\hspace{2cm}} \Omega$$

D.1. Snimanje karakteristike impulsno-širinskog modulatora, $D(v_{TP2})$

Tabela 4.1.


$v_{(TP2)}[\text{V}]$	$T_{POS} [\mu\text{s}]$	$T_S [\mu\text{s}]$	D

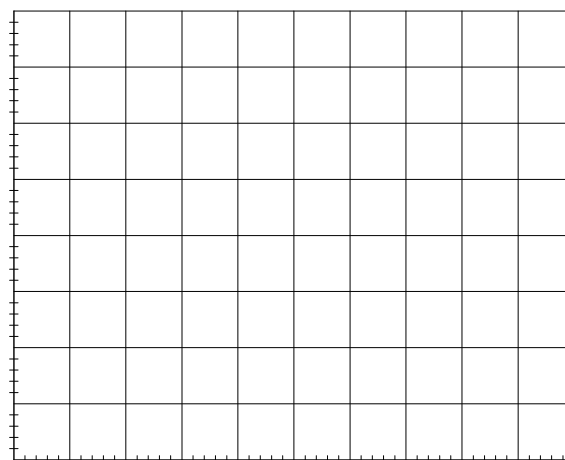


Slika 4.2. $D(v_{TP2})$

D.2. Integralni regulator

D.2.1. Integralni regulator sa 10 nF.

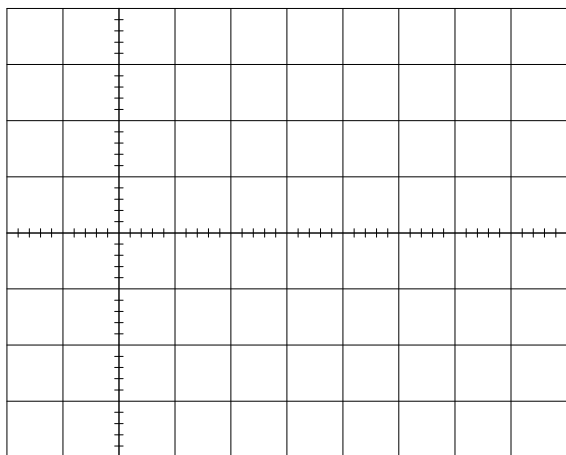


Slika 4.3. Struja kalema, $R_L = 100 \Omega$

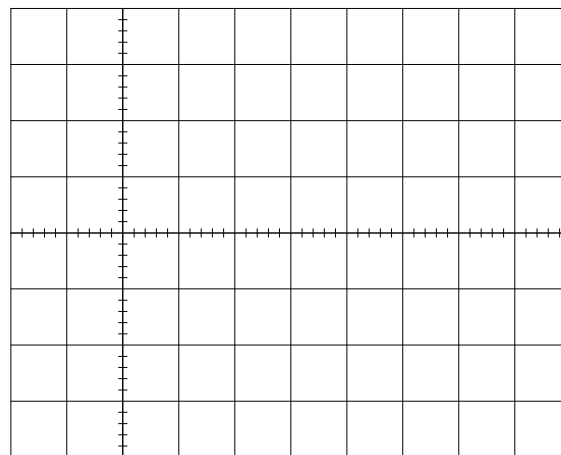


Slika 4.4. Izlazni napon regulatora,
 $R_L = 100 \Omega$


$$I_{OUT \text{ stable / unstable}} = \underline{\hspace{2cm}} \text{ mA}$$

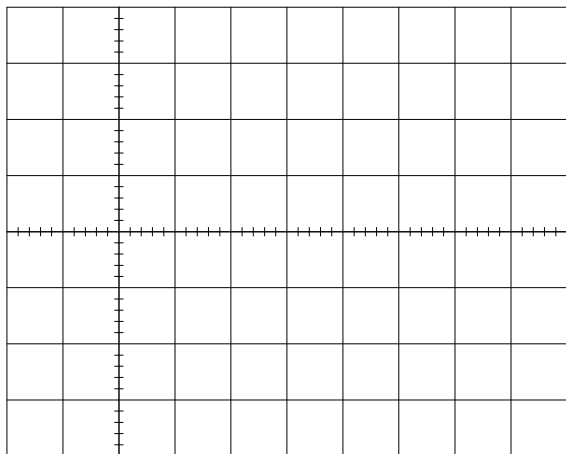

Slika 4.5. Struja kalema, $R_L = 16,5 \Omega$

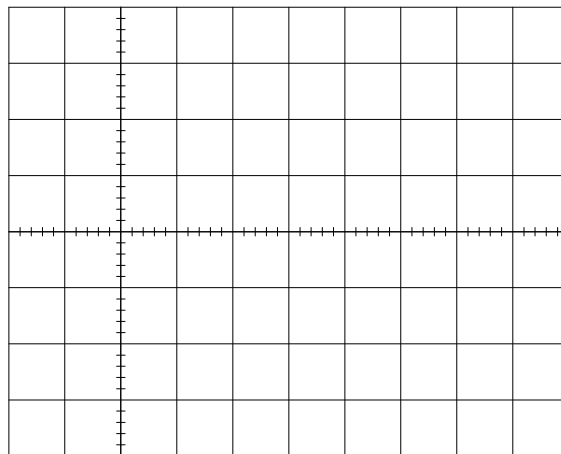


Slika 4.6. Izlazni napon regulatora,
 $R_L = 16,5 \Omega$

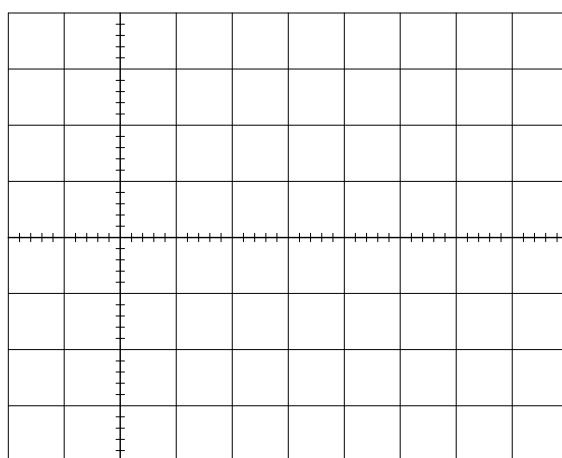


Slika 4.7. Izlazni napon konvertora, $R_L = 16,5 \Omega$

$V_{out\ p-p} = \underline{\hspace{2cm}}$ mV

D.2.2. Integralni regulator sa 47 nF.

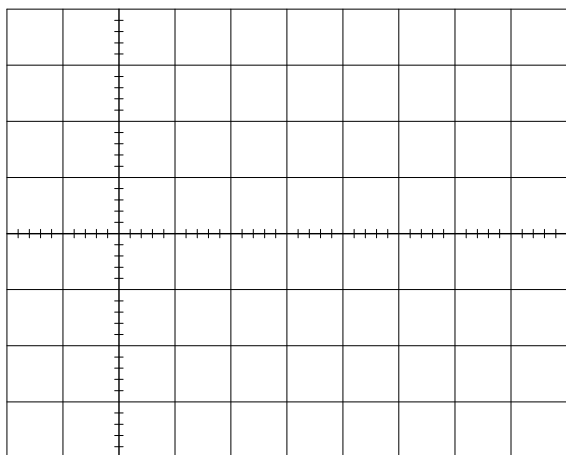


Slika 4.8. Struja kalema, $R_L = 100 \Omega$

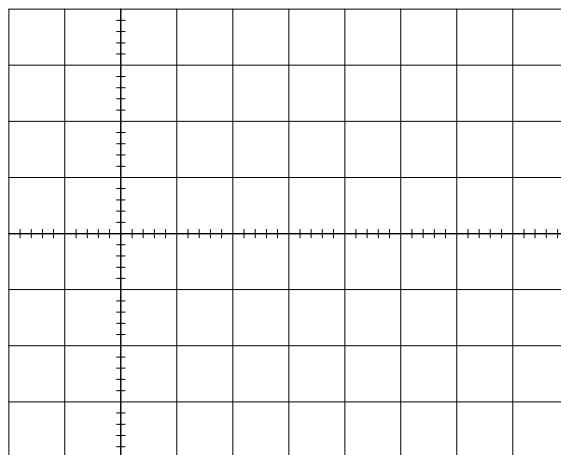


Slika 4.9. Izlazni napon regulatora,
 $R_L = 100 \Omega$


$I_{OUT\ stable / unstable} = \underline{\hspace{2cm}}$ mA

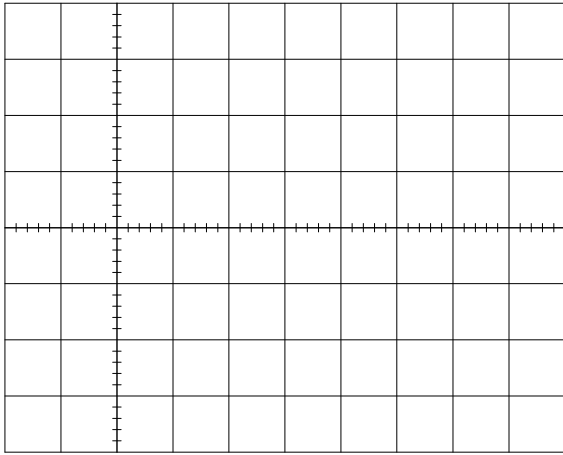

Slika 4.10. Struja kalema, $R_L = 16,5 \, \Omega$

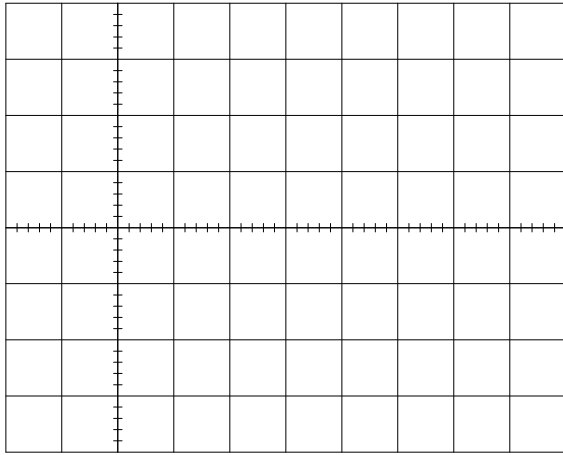

Slika 4.11. Izlazni napon regulatora,
 $R_L = 16,5 \, \Omega$

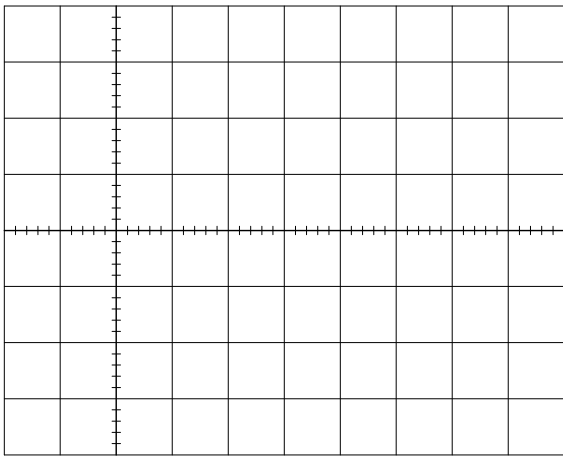


Slika 4.12. Izlazni napon konvertora, $R_L = 16,5 \, \Omega$

$V_{out \, p-p} = \text{_____} \, \text{mV}$

D.2.3. Integralni regulator sa 100 nF.

Tabela 4.2.

$I_{OUT} \, [\text{mA}]$	$V_{OUT} \, [\text{V}]$

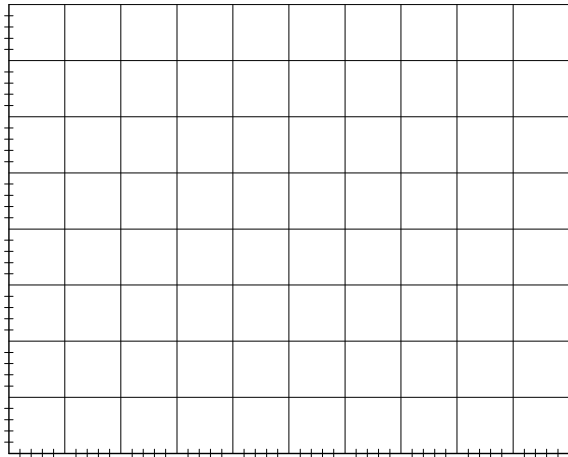

Slika 4.13. $V_{OUT}(I_{OUT})$


Zaključak:

D.3. Proporcionalni regulator

D.3.1. Proporcionalni regulator sa 100 kΩ.

Tabela 4.3.

I_{OUT} [mA]	V_{OUT} [V]

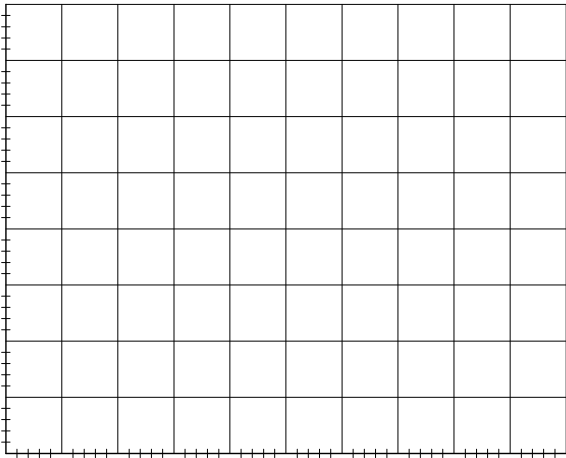


Slika 4.14. $V_{OUT}(I_{OUT})$


D.3.2. Proporcionalni regulator sa 470 kΩ.

Tabela 4.4.


I_{OUT} [mA]	V_{OUT} [V]

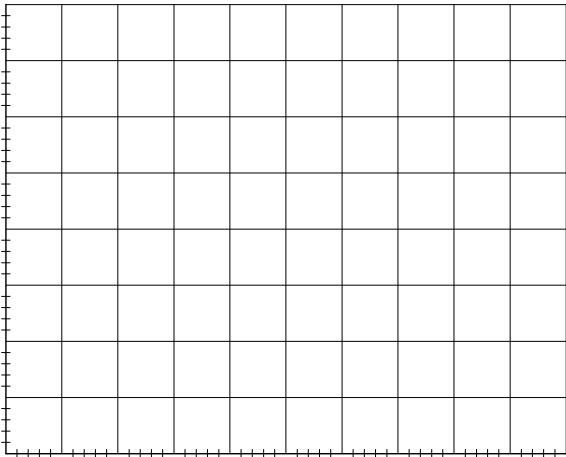


Slika 4.15. $V_{OUT}(I_{OUT})$

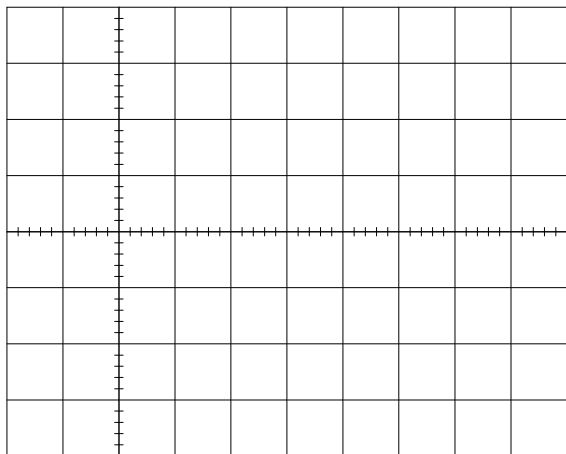

Slika 4.16. Struja kalema, $I_{OUT} = 500 \text{ mA}$

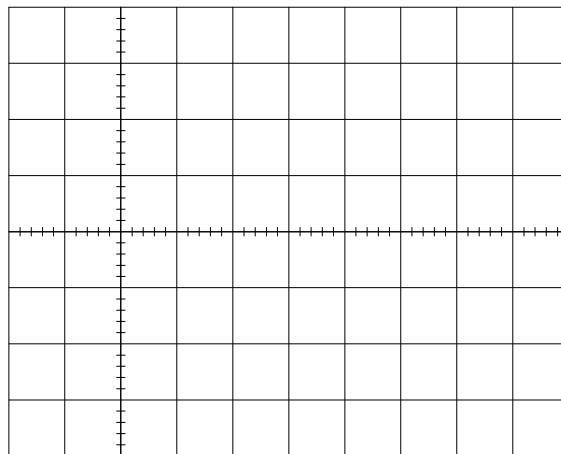


Slika 4.17. Izlazni napon regulatora,
 $I_{OUT} = 500 \text{ mA}$

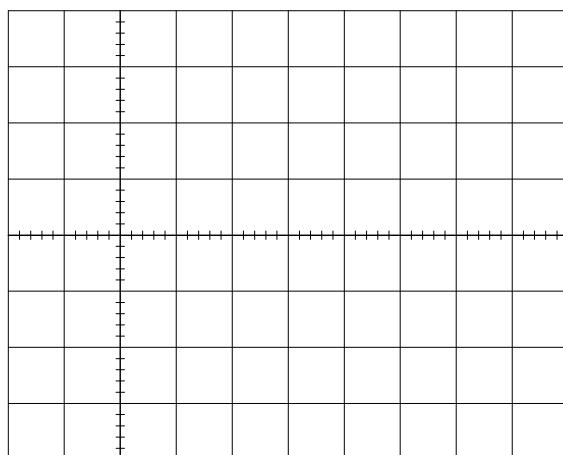


Slika 4.18. Naizmenična komponenta izlaznog napona konvertora, $I_{OUT} = 500 \text{ mA}$
Zaključak:


D.4. Proporcionalno-integralni regulator

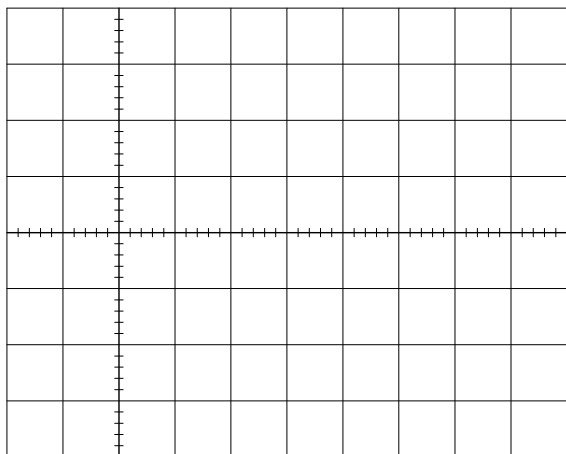


Slika 4.19. Struja kalema, $R_L = 16,5 \Omega$

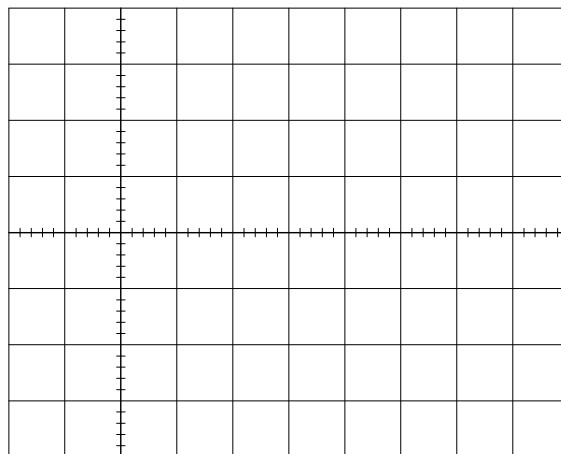


Slika 4.20. Izlazni napon regulatora,
 $R_L = 16,5 \Omega$

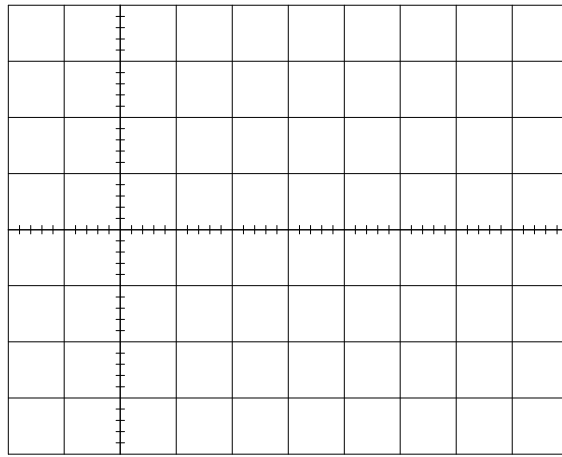


Slika 4.21. Naizmenična komponenta izlaznog napona konvertora, $R_L = 16,5 \, \Omega$

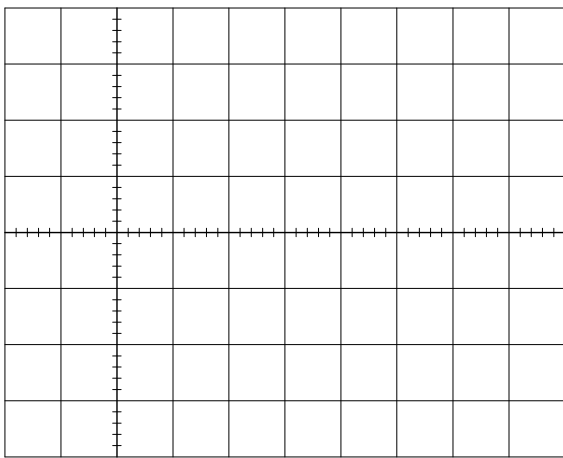

Slika 4.22. Struja kalema

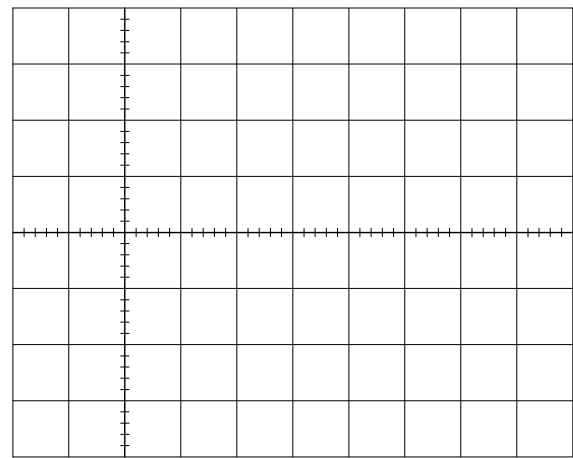


Slika 4.23. Izlazni napon regulatora

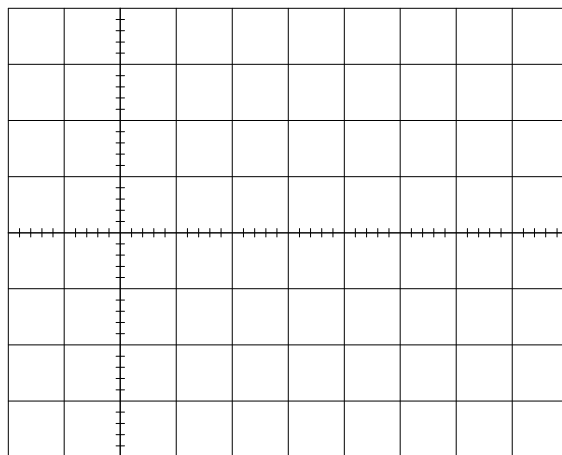


Slika 4.24. Izlazni napon konvetora

D5. Dinamički odziv konvertora


D.5.1. Proporcionalni regulator sa 100 k Ω

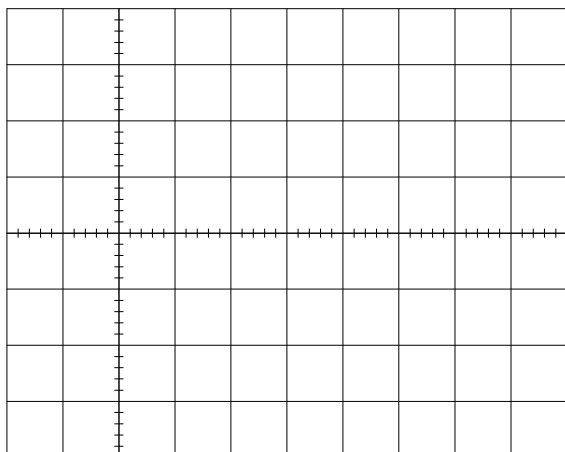


Slika 4.25. Struja kalema, $R_L = 16,5 \, \Omega$,
 $R_{L2} = 8,2 \, \Omega$

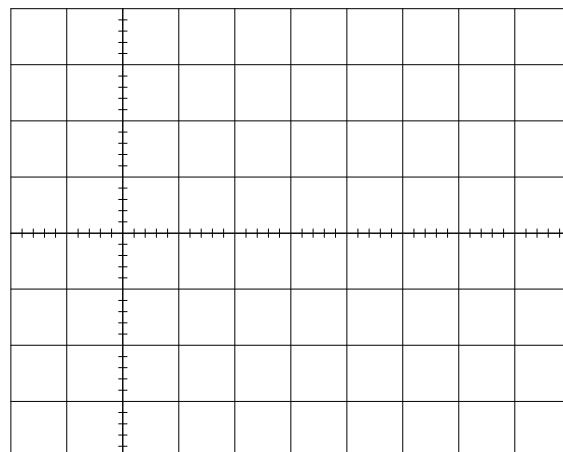

Slika 4.26. Naizmenična komponenta
izlaznog napona, isto

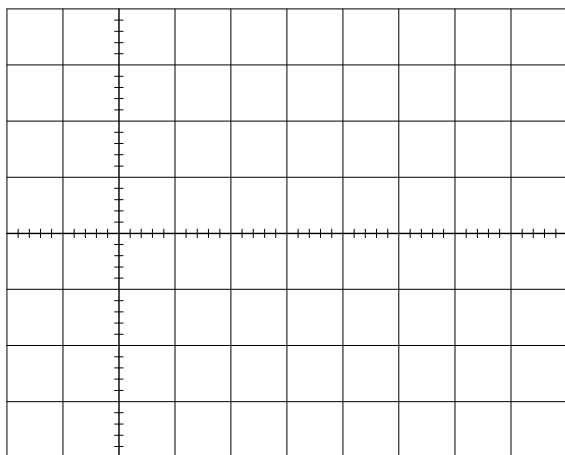


Slika 4.27. Struja kalema, $R_L = 47 \, \Omega$,
 $R_{L2} = 8,2 \, \Omega$

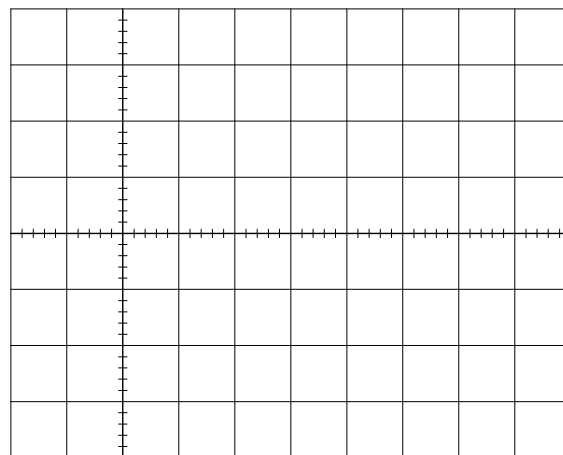


Slika 4.28. Naizmenična komponenta
izlaznog napona, isto

Zaključak:


D.5.2. Proporcionalni regulator sa 470 k Ω .

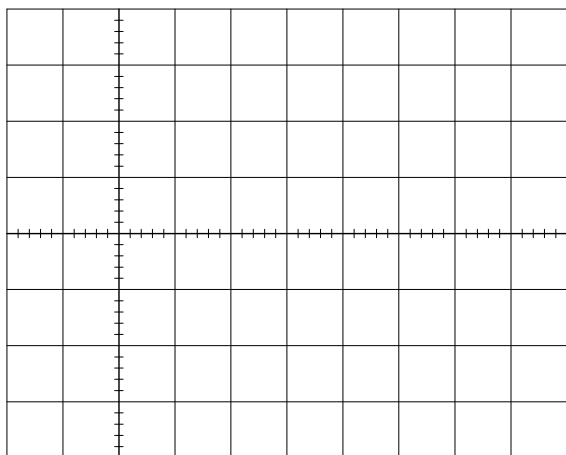


Slika 4.29. Struja kalema, $R_L = 16,5 \, \Omega$,
 $R_{L2} = 8,2 \, \Omega$

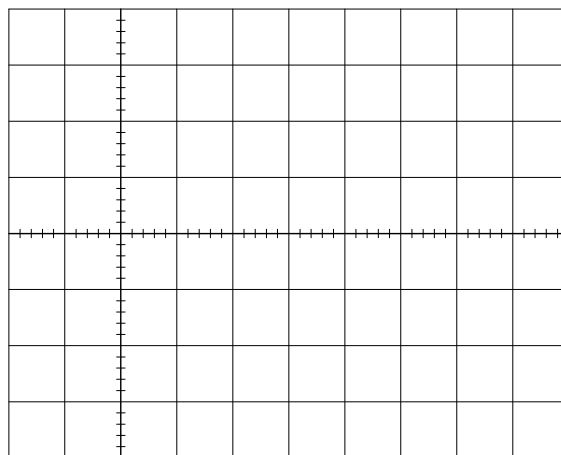

Slika 4.30. Naizmenična komponenta
izlaznog napona, isto

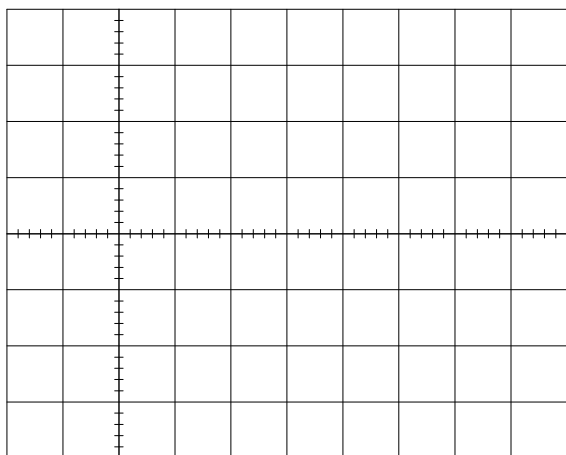


Slika 4.31. Struja kalema, $R_L = 47 \, \Omega$,
 $R_{L2} = 8,2 \, \Omega$

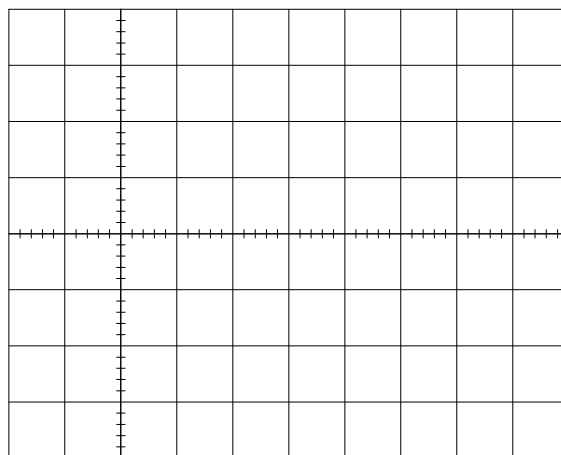


Slika 4.32. Naizmenična komponenta
izlaznog napona, isto

Zaključak:


D.5.3. Integralni regulator sa 100 nF.

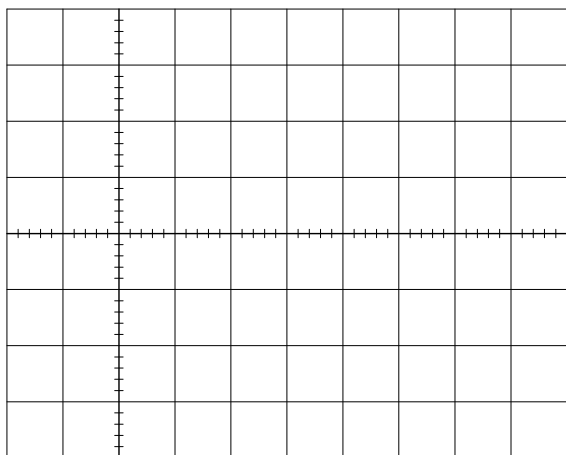


Slika 4.33. Struja kalema, $R_L = 16,5 \, \Omega$,
 $R_{L2} = 8,2 \, \Omega$

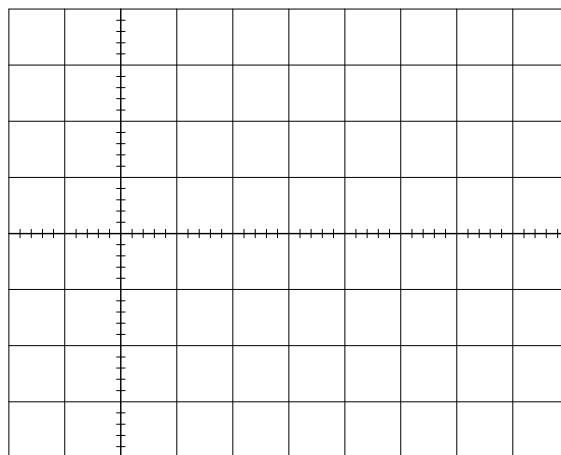

Slika 4.34. Naizmenična komponenta
izlaznog napona, isto

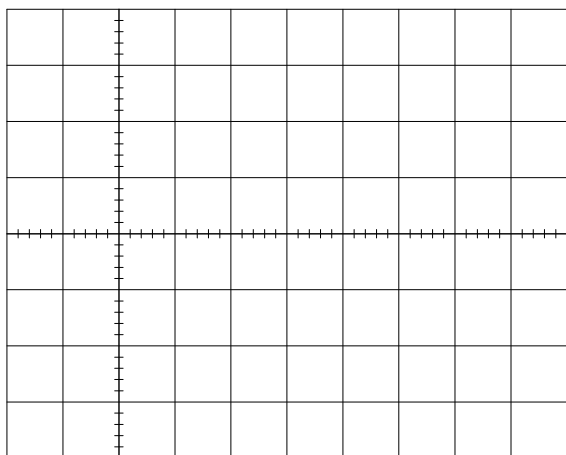


Slika 4.35. Struja kalema, $R_L = 47 \, \Omega$,
 $R_{L2} = 8,2 \, \Omega$

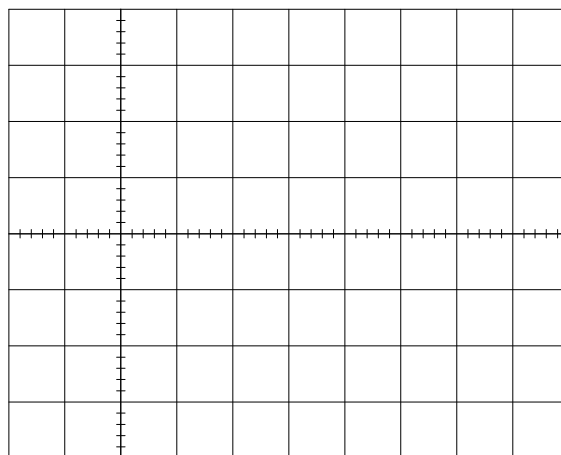


Slika 4.36. Naizmenična komponenta
izlaznog napona, isto

Zaključak:


D.5.4. Proporcionalno-integralni regulator.

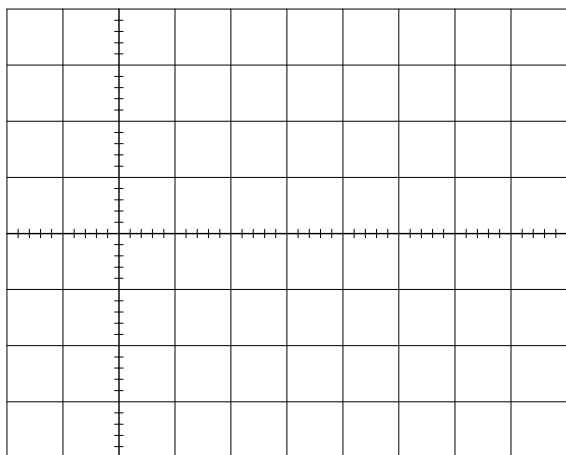


Slika 4.37. Struja kalema, $R_L = 16,5 \, \Omega$,
 $R_{L2} = 8,2 \, \Omega$

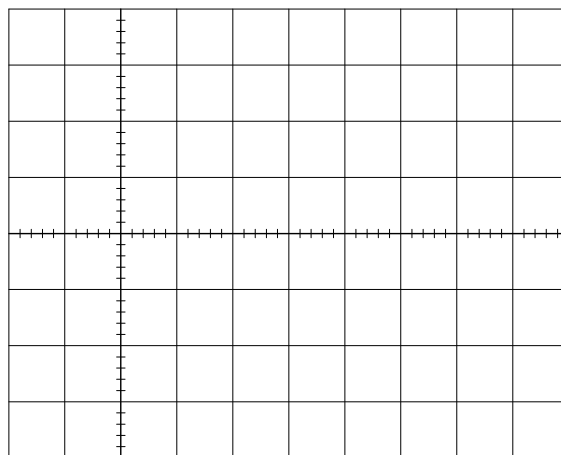


Slika 4.38. Naizmenična komponenta
izlaznog napona, isto

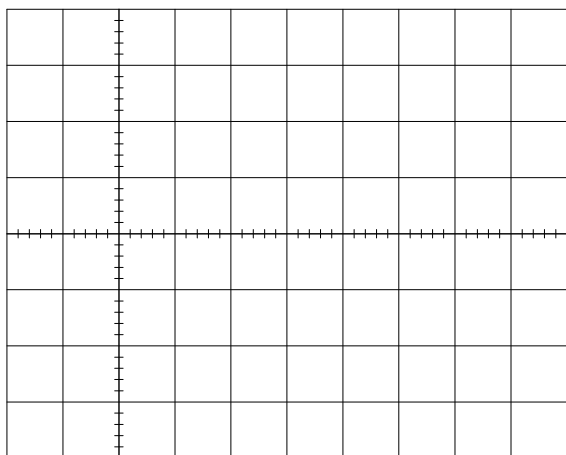


Slika 4.39. Struja kalema

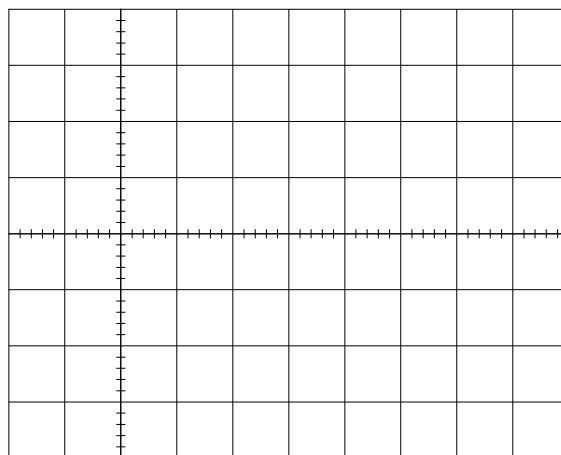


Slika 4.40. Naizmenična komponenta
izlaznog napona

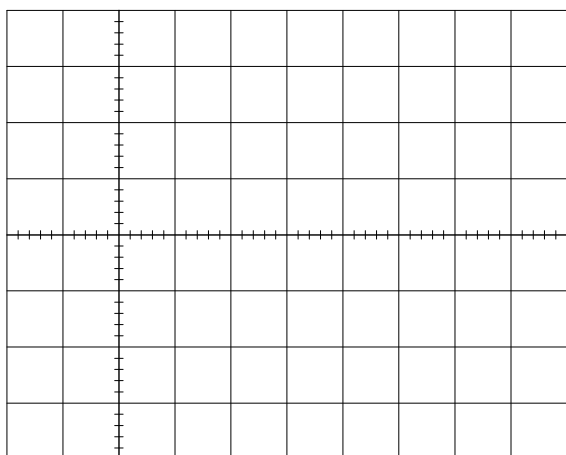


Slika 4.41. Struja kalema, 2 kHz

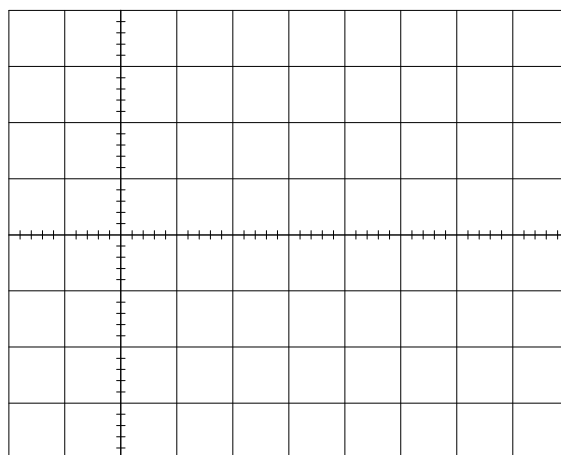


Slika 4.42. Naizmenična komponenta
izlaznog napona, 2 kHz

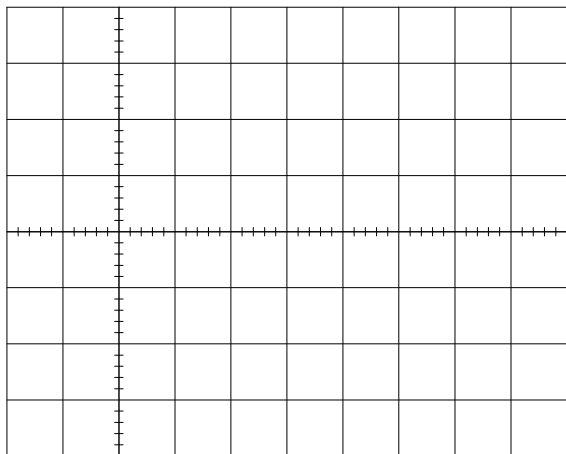


Slika 4.43. Struja kalema, $R_L = 47 \, \Omega$,
 $R_{L2} = 8,2 \, \Omega$

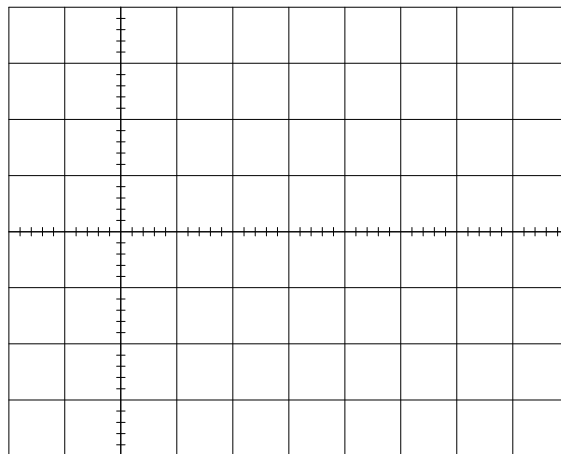


Slika 4.44. Naizmjenična komponenta
izlaznog napona, isto

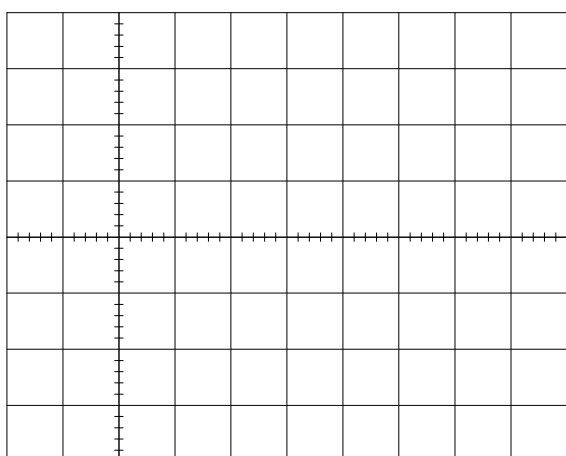


Slika 4.45. Struja kalema

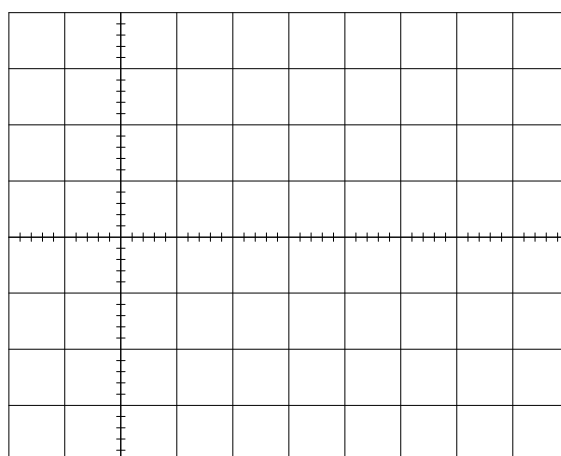

Slika 4.46. Naizmjenična komponenta
izlaznog napona

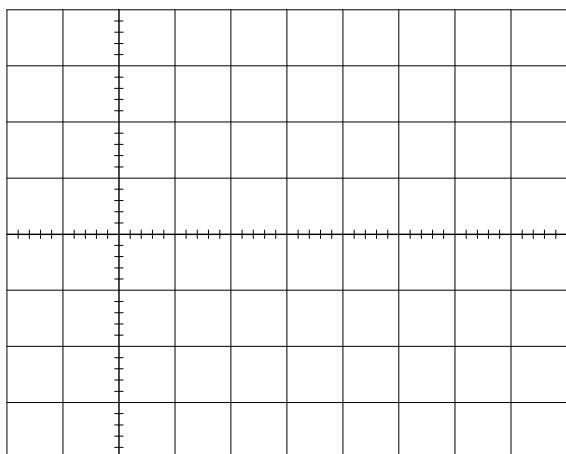

Slika 4.47. Struja kalema, 2 kHz

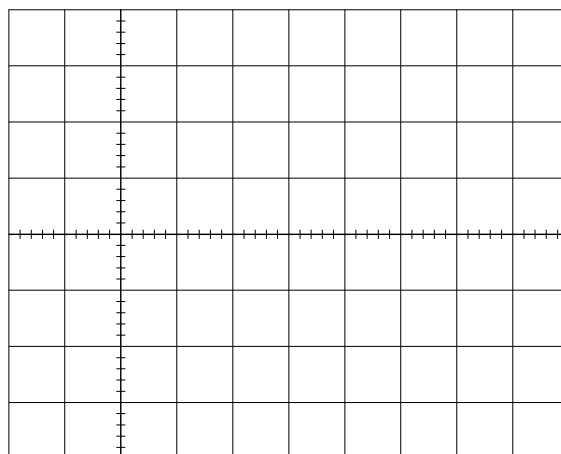

Slika 4.48. Naizmjenična komponenta
izlaznog napona, 2 kHz

Zaključak:


D.6. Prenosna karakteristika konvertora i kružno pojačanje

$V_{TP2} = \text{_____ V}$


D.6.1. Prenosna karakteristika konvertora

Tabela 4.5.

$f \text{ [Hz]}$	$V_{out\ p-p} \text{ [mV]}$	$ H_1(s) $	$\arg(H_1(s))$

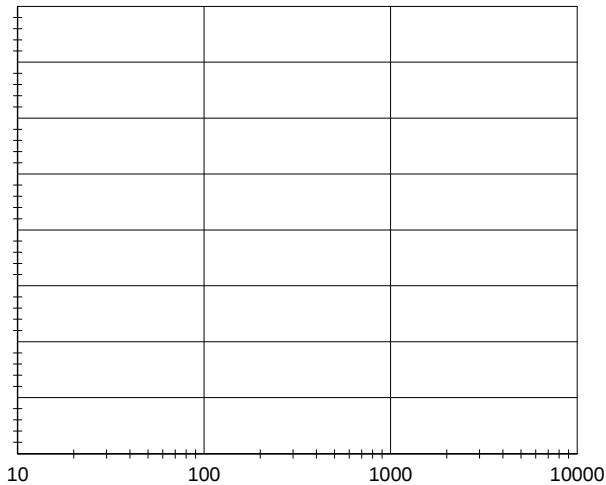

Slika 4.49. $|H_1(s)|$

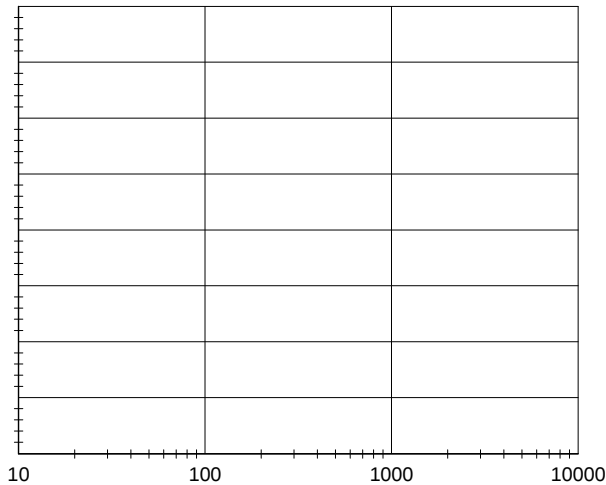


Slika 4.50. $\arg(H_1(s))$


D.6.2. Kružno pojačanje

Tabela 4.6.

f [Hz]	$V_{TP2\,p-p}$ [mV]	$ H_2(s) $	$\arg(H_2(s))$

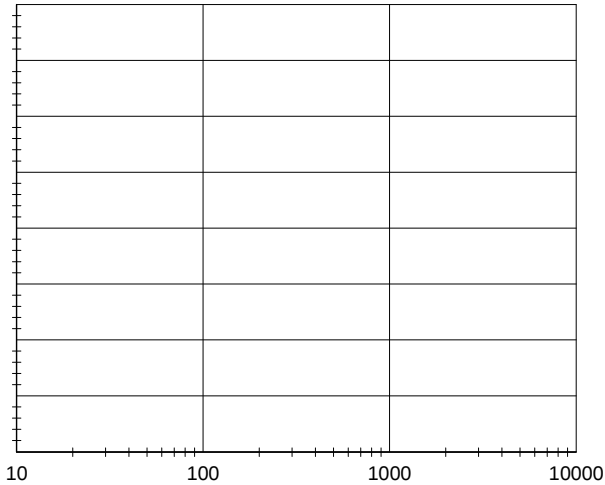

Slika 4.51. $|H_2(s)|$

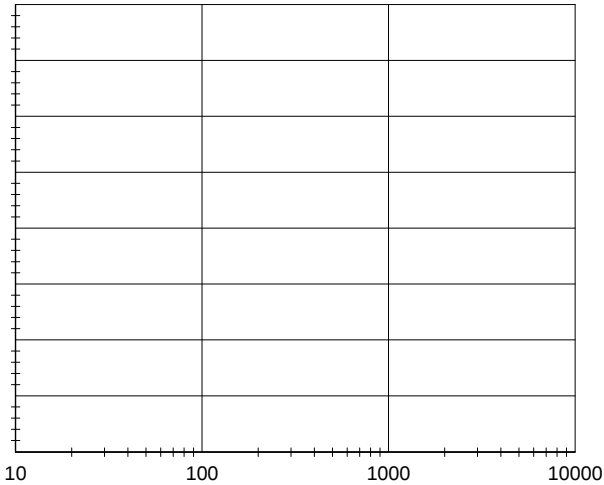

Slika 4.52. $\arg(H_2(s))$