

Osnovi analogue elektronike

19E042OAE

5.12.2021.

Osnovi elektronike


19E042OE

Elementi elektronike (2013)

13E042EE i 13E042EEG

## Kolokvijum – rešenja

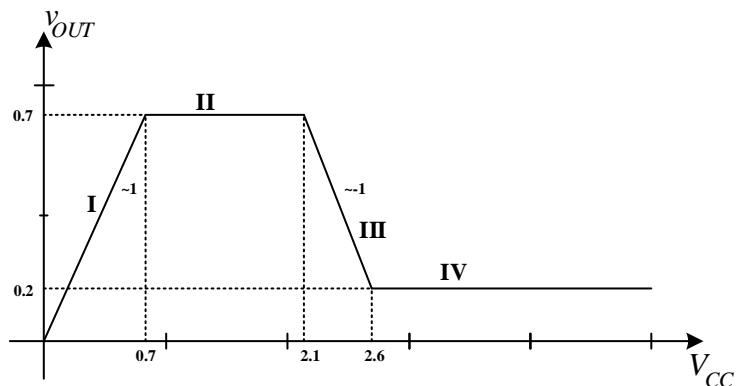1.  $I_D \approx 3.94\text{mA}$ ,  $a_v \approx 0.98$ ,  $R_u \approx 2.28\text{M}\Omega$ ,  $a_i \approx 22.30$



2.

$$\text{I: } v_{OUT} = V_{CC}; D \rightarrow OFF, Q \rightarrow OFF$$

$$\text{II: } v_{OUT} = V_D = 0.7V; D \rightarrow ON, Q \rightarrow OFF$$

$$\text{III: } v_{OUT} = V_{CC} \left( \frac{1}{R_3} - \frac{\beta}{2R_T} \right) + \frac{\beta V_{BE}}{R_T} - \frac{V_D}{R_3} = -0.05s V_{CC} + 0.105; D \rightarrow ON, Q \rightarrow ON_{DAR}$$

$$\text{III: } v_{OUT} = V_{CES} = 0.2V; D \rightarrow ON, Q \rightarrow ON_{ZAS}$$