

Osnovi analogue elektronike – februar 2022 - resenja

- 3.** a) $R_2 = (V_G - 2V_D)/I_{D1} = R_3 = 180\Omega$
 b) $v_I = 0.6V + 6.37\mu V \sin(\omega t)$


- 4.** a) $R_B = 721.6\Omega$
 b) $A_v = -g_m R_C$, $R_{ul} = R_B \parallel r_\pi$, $R_{izl} = R_c$
 c) $A_v = -121.1$, $R_{ul} = 82\Omega$, $R_{izl} = 2k\Omega$

7. zadatak

- a) $R_0 = 400\Omega$
 b) $a_v = \underbrace{-g_{m1} \left(R_0 \parallel \frac{1}{g_{m2}} \right)}_{\text{Prvi stepen}} \cdot \underbrace{\frac{g_{m2} R_S}{R_i}}_{\text{Drugi stepen}}, R_i = R_S$
 c) $a_v = -4, R_i = 7k\Omega$

8. zadatak

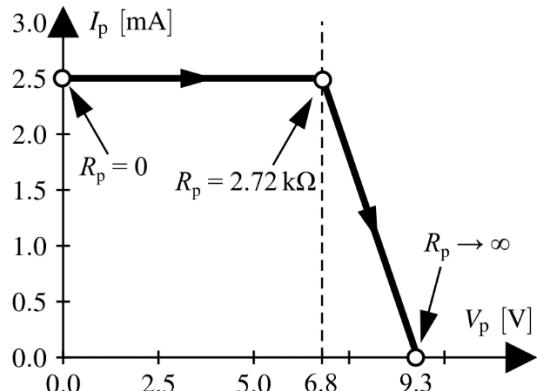- a) $I_{KS} = 5x \text{ mA}$.
 b) Traženi dijagram je na slici



- c) $R_{p,max} = 860 \Omega$.