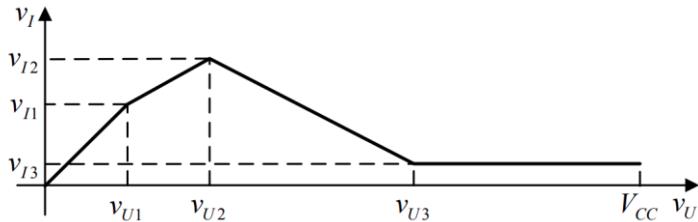


3. rešenje

Izrazi koji opisuju funkcije prenosa kola:

$$v_I = \begin{cases} v_U & 0 \text{ V} \leq v_U \leq 0.7 \text{ V} \\ \frac{v_U}{2} + 0.35 \text{ V} & 0.7 \text{ V} \leq v_U \leq 1.4 \text{ V} \\ -\frac{v_U}{2} + 1.75 \text{ V} & 1.4 \text{ V} \leq v_U \leq 3.1 \text{ V} \\ 0.2 \text{ V} & 3.1 \text{ V} \leq v_U \leq 5 \text{ V} \end{cases}$$

Grafički prikaz je dat:



gde je:


$$v_{II} = v_{U1} = 0.7 \text{ V}$$

$$v_{U2} = 1.4 \text{ V}, v_{I2} = 1.05 \text{ V}$$

$$v_{U3} = 3.1 \text{ V}, v_{I3} = 0.2 \text{ V}$$

4. rešenje

a) $I_D = 2mA$

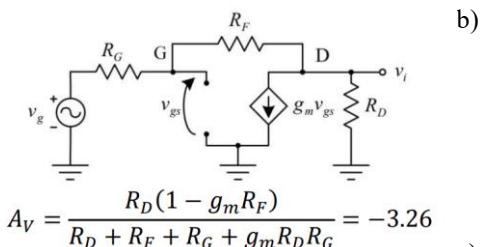


$$A_V = \frac{R_D(1 - g_m R_F)}{R_D + R_F + R_G + g_m R_D R_G} = -3.26$$

b)

$$i_g = \frac{v_g - v_i}{R_G + R_F} = \frac{v_g - A_V v_g}{R_G + R_F}$$

$$R_U = \frac{v_g}{i_g} = \frac{R_G + R_F}{1 - A_V} \approx 14.1k\Omega$$

c)

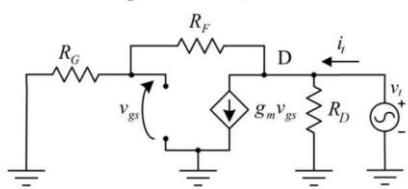

$$i_t = g_m v_{gs} + \frac{v_t}{R_F + R_G} + \frac{v_t}{R_D}$$

$$v_{gs} = v_t \frac{R_G}{R_G + R_F}$$


$$R_i = \frac{v_t}{i_t} = \frac{1}{\frac{g_m R_G}{R_G + R_F} + \frac{1}{R_F + R_G} + \frac{1}{R_D}} \approx 983\Omega$$

7. rešenje

(a)

$$v_I = \begin{cases} -\frac{2}{3}v_{IN} + 12 \text{ V} & , \quad 0 \leq v_{IN} \leq 4,5 \text{ V} \\ -2v_{IN} + 18 \text{ V} & , \quad 4,5 \text{ V} \leq v_{IN} \leq 6,5 \text{ V} \\ -\frac{2}{3}v_{IN} + \frac{28}{3} \text{ V} & , \quad 6,5 \text{ V} \leq v_{IN} \leq 12 \text{ V} \end{cases}$$
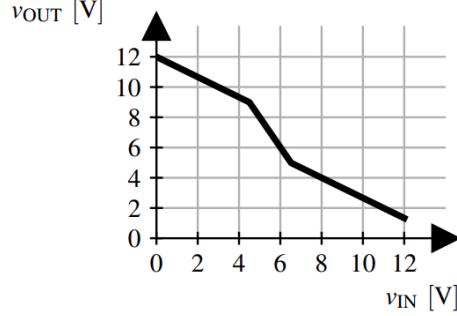
$$(5) v_{OUT} = 7 \text{ V} - 0,2 \text{ V} \sin(\omega t).$$



8. rešenje

a) Otpornost R_0 je:

$$R_0 = \frac{V_{CC} - V_{BE}}{I_3} = 1.72 \text{ k}\Omega$$

b) Transkonduktansa tranzistora u mirnoj radnoj tački iznosi

$$g_{m2} = g_m = \frac{I_{C1/2}}{V_T} = 0.05 \text{ S},$$

te je diferencijalno pojačanje pojačavača

$$A_d = \frac{v_i}{v_d} = \frac{g_m R_C}{2} = 25$$