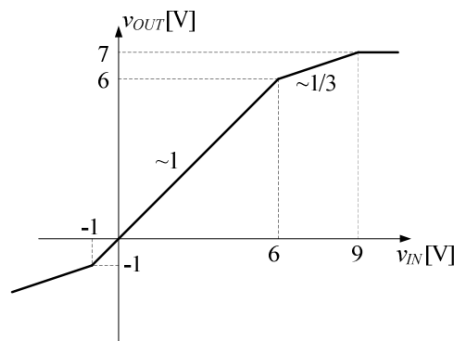


OSNOVI ANALOGNE ELEKTRONIKE – JUL 24 – REŠENJA

3. rešenje

$$v_{OUT} = \begin{cases} \frac{R_2}{R_1 + R_2} v_{IN} - \frac{R_1}{R_1 + R_2} V_D & v_{IN} \leq -V_D \\ v_{IN} & -V_D \leq v_{IN} \leq V_Z \\ \frac{R_2}{R_1 + R_2} v_{IN} + \frac{R_1}{R_1 + R_2} V_Z & V_Z \leq v_{IN} \leq V_Z + 3V_D \\ V_Z + V_D & v_{IN} \geq V_Z + 3V_D \end{cases} = \begin{cases} 0.33v_{IN} - 0.67 \text{ V} & v_{IN} \leq -1 \text{ V} \\ v_{IN} & -1 \text{ V} \leq v_{IN} \leq 6 \text{ V} \\ 0.33v_{IN} + 4 \text{ V} & 6 \text{ V} \leq v_{IN} \leq 9 \text{ V} \\ 7 \text{ V} & v_{IN} \geq 9 \text{ V} \end{cases}$$




4. rešenje

Izrazi koji opisuju funkcije prenosa kola:

$$v_I = \begin{cases} v_U & 0 \text{ V} \leq v_U \leq 0.7 \text{ V} \\ \frac{v_U}{2} + 0.35 \text{ V} & 0.7 \text{ V} \leq v_U \leq 1.4 \text{ V} \\ -\frac{v_U}{2} + 1.75 \text{ V} & 1.4 \text{ V} \leq v_U \leq 3.1 \text{ V} \\ 0.2 \text{ V} & 3.1 \text{ V} \leq v_U \leq 5 \text{ V} \end{cases}$$

Grafički prikaz je dat:

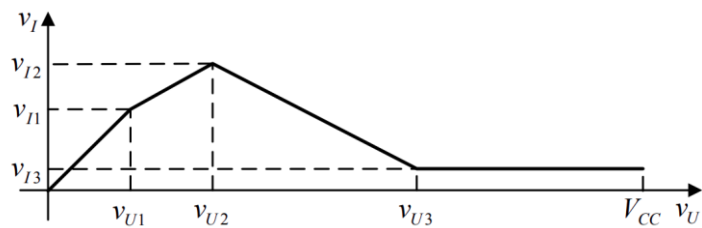

gde je:

$$v_{U1} = v_{U1} = 0.7 \text{ V}$$


$$v_{U2} = 1.4 \text{ V}, v_{I2} = 1.05 \text{ V}$$

$$v_{U3} = 3.1 \text{ V}, v_{I3} = 0.2 \text{ V}$$

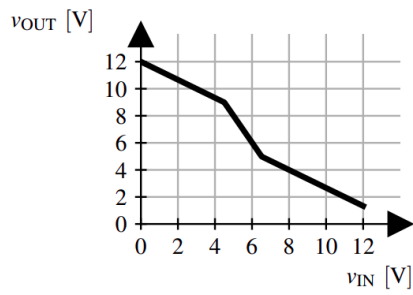7. Resenje

(a)


$$v_I = \begin{cases} -\frac{2}{3}v_{IN} + 12 \text{ V} & , 0 \leq v_{IN} \leq 4,5 \text{ V} \\ -2v_{IN} + 18 \text{ V} & , 4,5 \text{ V} \leq v_{IN} \leq 6,5 \text{ V} \\ -\frac{2}{3}v_{IN} + \frac{28}{3} \text{ V} & , 6,5 \text{ V} \leq v_{IN} \leq 12 \text{ V} \end{cases}$$




(b) $v_{OUT} = 7 \text{ V} - 0,2 \text{ V} \sin(\omega t)$.

8.

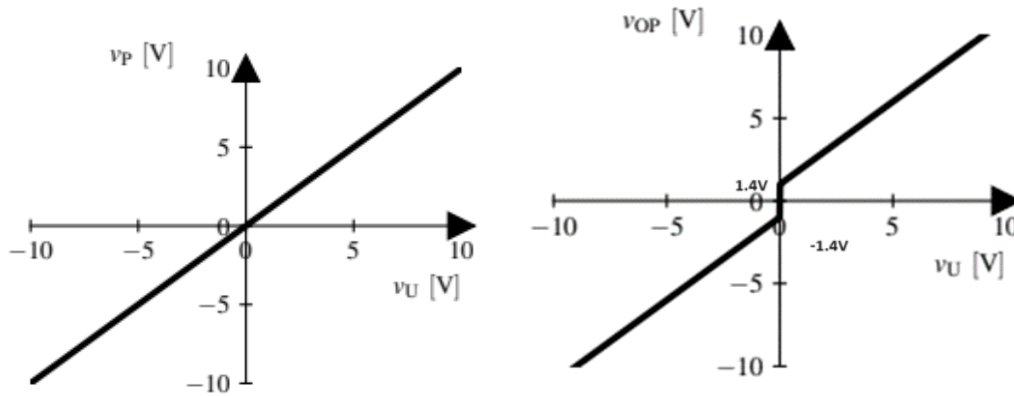a) Tražene statičke karakteristike prikazane su na slikama.



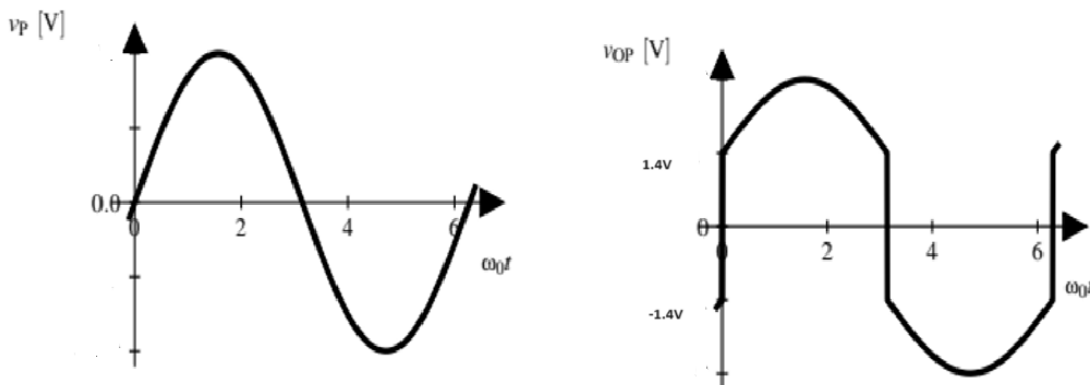b) Traženi dijagrami prikazani su na slikama:



d) Tražena otpornost je $R_{p,\min} = 02.26 \Omega$