
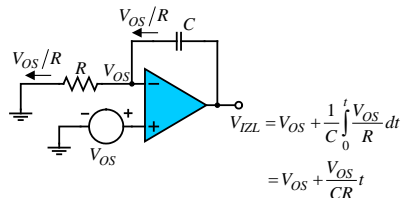




REŠENJA:

1. Beleške za predavanja, 9_Izlazni_pojacavacki_stepeni.pdf, slajdovi 3-5 (+ 6-8).

2. a)

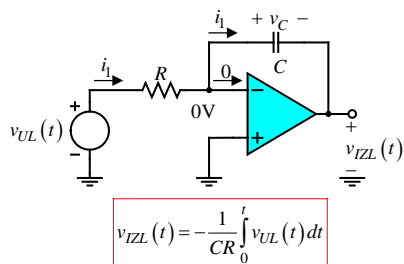

b)


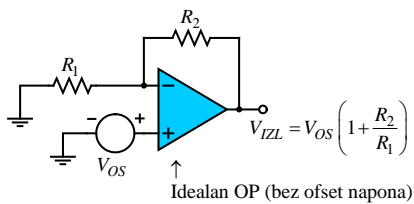
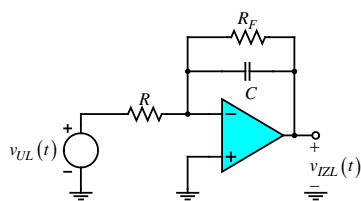


Ako se paralelno kondenzatoru veže R_F :

$$1V = 5mV \left(1 + \frac{R_F}{R} \right)$$

$$R_F = 199R$$

c)

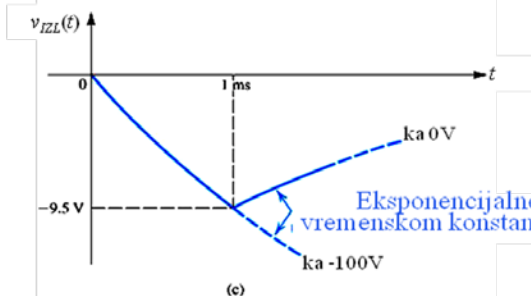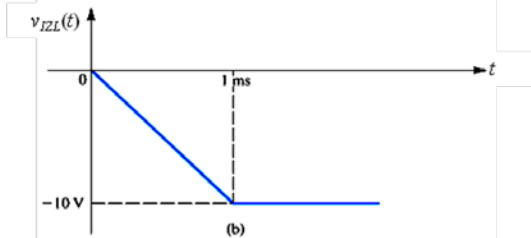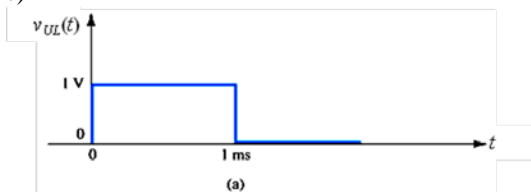

(a) Ulazni impuls. (b) Izlazni linearno-promenljivi napon idealnog integratora sa vremenskom konstantom 0,1 ms. (c) Izlazni eksponencijalni napon kada je otpornik R_F priključen paralelno sa kondenzatorom integratora.

3. Beleške za predavanja, 13_Regulator_(stabilizator)_napona.pdf, slajd 2, 3.

4. a) $v_{BE3} = v_{BE4} \Rightarrow I_{C3} = I_{C4}$

$$\left. \begin{aligned} I_{C4} &= \frac{V_{CC} - V_{BE} - V_{EE}}{R_1} = 4\text{mA} = I_{C3} \\ I_{C1} + I_{C2} &= I_{C3} \\ I_{C1} &= I_{C2} \end{aligned} \right\} \Rightarrow I_{C1} = I_{C2} = \frac{I_{C3}}{2} = 2\text{mA}$$

b) $r_{\pi 1} = r_{\pi 2} = \frac{\beta_0 V_T}{I_{C1}} = 1.25\text{k}\Omega$



$$\frac{v_p}{2} = (R_C \parallel \frac{R_P}{2}) \beta_0 \frac{\frac{v_d}{2}}{r_{\pi} + (1 + \beta_0) R_E} \Rightarrow a_d = \frac{v_p}{v_d} = \beta_0 \frac{R_C \parallel \frac{R_P}{2}}{r_{\pi} + (1 + \beta_0) R_E} = 5 \Rightarrow R_C = 5.36\text{k}\Omega$$

c) V_{\min} - određeno zasićenjem tranzistora Q_3

$$V - V_{BE} - I_{C1} R_E - V_{EE} \geq V_{CES} \Rightarrow V \geq V_{BE} + I_{C1} R_E + V_{EE} + V_{CES} \Rightarrow V_{\min} = -10.2\text{V}$$

V_{\max} - određeno zasićenjem tranzistora Q_1

$$V_{CC} - I_{C1} R_C - V + V_{BE} \geq V_{CES} \Rightarrow V \leq V_{CC} - I_{C1} R_C + V_{BE} - V_{CES} \Rightarrow V_{\max} = 1.68\text{V}$$

5.

a)

$$v_r = - \frac{(R_1 \parallel R_u + R_2) \parallel R_3}{(R_1 \parallel R_u + R_2) \parallel R_3 + R_4 + R_i} \frac{R_1 \parallel R_u}{R_1 \parallel R_u + R_2} v_t \Rightarrow$$

$$A_{inv} = \frac{v_r}{v_t} = - \frac{(R_1 \parallel R_u + R_2) \parallel R_3}{(R_1 \parallel R_u + R_2) \parallel R_3 + R_4 + R_i} \frac{R_1 \parallel R_u}{R_1 \parallel R_u + R_2} = -0.0832 \Rightarrow T = -a_{inv} = 8.32$$

b)

$$a_{r\infty} = a_r (a \rightarrow \infty) \Rightarrow v_u = 0 \Rightarrow v_x = -R_2 \frac{v_g}{R_1} \Rightarrow v_i = v_x - R_4 \left(\frac{v_g}{R_1} - \frac{v_x}{R_3} \right)$$

$$v_i = - \frac{v_g}{R_1} \left(R_2 + R_4 + \frac{R_2 R_4}{R_3} \right) \Rightarrow a_{r\infty} = - \frac{R_2 + R_4 + \frac{R_2 R_4}{R_3}}{R_1} = -8$$

$$a_{r0} = a_r (a = 0) \Rightarrow$$

$$c) v_i = \frac{R_u \parallel (R_2 + R_3 \parallel (R_4 + R_i))}{R_u \parallel (R_2 + R_3 \parallel (R_4 + R_i)) + R_1} \frac{R_3 \parallel (R_4 + R_i)}{R_3 \parallel (R_4 + R_i) + R_2} \frac{R_i}{R_i + R_4} v_g \Rightarrow a_{r0} = 0.017$$

$$d) a_r = a_{r\infty} \frac{T}{1+T} + a_{r0} \frac{1}{1+T} = -7.14$$

e) $R_{ir} = R_{i0} \frac{1+T_{ks}}{1+T_{ov}}$

$$R_{i0} = R_i \parallel (R_4 + R_3 \parallel (R_2 + R_u \parallel R_1)) = 932\Omega, T_{ks} = 0, T_{ov} = T = 8.32$$

$$R_{ir} = 100\Omega$$