

## REŠENJA:

1.

a)  $V_Z = 5,6V$

b)  $I = 0,2W/5,6V = 35,7mA$ ;  $I_{Zmax} = I = 35,7mA$ ;  $I_{Rp}|_{max} = 10I = 3,6A$ ;  $I_{Rp}|_{Rp=0} = 3,6A$

2.

a)  $a_d = \frac{v_i}{v_{u1} - v_{u2}} = \frac{g_{m2}R_2}{2}$ ;  $a_s \cong -\frac{R_2}{2r_{ds4}}$ ;  $\rho = \left| \frac{a_d}{a_s} \right| \cong g_{m2}r_{ds4}$

b)  $\rho = 100\sqrt{2} \cong g_{m2}r_{ds4} = \sqrt{2I_2B} \times \frac{V_{DS4} + V_{A4}}{I_4} \cong \sqrt{I_4B} \times \frac{V_{A4}}{I_4} \Leftrightarrow (V_{DS4} \square V_{A4})$

$$\rho = 100\sqrt{2} \cong \sqrt{\frac{B}{I_4}} \times V_{A4} \Rightarrow I_4 = 1mA = I_3$$

$$I_3 = 1mA = \frac{B}{2}(V_{GS3} - V_t)^2 \Rightarrow V_{GS3} = 2V \quad R_1 I_3 + V_{GS3} = V_{DD} - V_{SS} \Rightarrow R_1 = 8k\Omega$$

$$I_1 = I_2 = I_4/2 = 0,5mA \quad V_{IQ} = V_{SS} + R_2 I_2 = -2,5V \Rightarrow R_2 = (-V_{SS} - 2,5V)/I_2 = 5k\Omega$$

3. Beleške za predavanja, 9\_Izlazni\_pojacavacki\_stepeni.pdf, slajdovi 6-8 (+ 3-5).

4. a) i b)  $V_E = (R_{E1} + R_{E2})I_C = 5V$


$$V_C = V_{CC} - R_C I_C = 9.5V, \quad V_{CE} = 4.5V > V_{CES} \text{ dakle tranzistor radi u DAR-u}$$

$$V_B = V_E + V_{BE} = 5.6V$$

$$V_B = \frac{R_2}{R_1 + R_2} V_{CC} \Rightarrow R_2 = \frac{R_1}{\frac{V_{CC}}{V_B} - 1} = 87.5k\Omega$$

$$V_P = 0$$

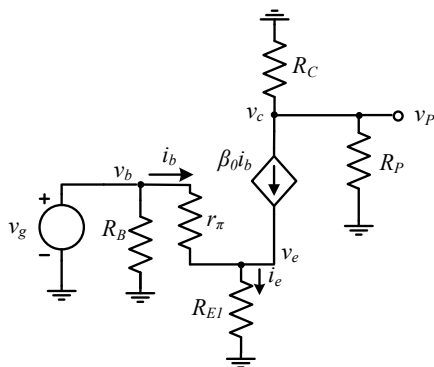c)  $r_\pi = \frac{\beta_0 V_T}{I_C} = 5k\Omega, \quad R_B = R_1 \parallel R_2 = 46.67k\Omega$



$$\left. \begin{aligned} v_p &= -\beta_0 i_b (R_C \parallel R_P) \\ i_b &= \frac{v_g}{r_\pi + (1 + \beta_0) R_{E1}} \end{aligned} \right\} \Rightarrow v_p = -\frac{\beta_0 (R_C \parallel R_P)}{r_\pi + (1 + \beta_0) R_{E1}} v_g \Rightarrow a_v = \frac{v_p}{v_g} = -\frac{\beta_0 (R_C \parallel R_P)}{r_\pi + (1 + \beta_0) R_{E1}} = -6$$

$$R_i = R_C = 5k\Omega$$

$$R_u = R_B \parallel (r_\pi + (1 + \beta_0) R_{E1}) = 25.35k\Omega$$

$$\left. \begin{aligned} i_p &= \frac{v_p}{R_P} \\ i_g &= \frac{v_g}{R_u} \end{aligned} \right\} \Rightarrow a_i = \frac{i_p}{i_g} = \frac{R_u}{R_P} \frac{v_p}{v_g} = -15.2$$

d)  $v_B(t) = V_B + v_b(t) = V_B + v_g(t) = (5.6 + 0.5 \sin(2\pi ft))V$

$$v_C(t) = V_C + v_c(t) = V_C + a_v v_g(t) = (9.5 - 3 \sin(2\pi ft))V$$

$$v_P(t) = V_P + v_p(t) = a_v v_g(t) = -3V \sin(2\pi ft)$$

$$v_E(t) = V_E + v_e(t) = V_E + (1 + \beta_0) R_{E1} i_b(t) = V_E + \frac{(1 + \beta_0) R_{E1}}{r_\pi + (1 + \beta_0) R_{E1}} v_g(t) = (5 + 0.45 \sin(2\pi ft))V$$

5.

a)

$$\left. \begin{aligned} V_{I1} &= -\frac{R_2}{R_1} V_R + \left(1 + \frac{R_2}{R_1}\right) V \\ V_I &= -\frac{R_1}{R_2} V_{I1} + \left(1 + \frac{R_1}{R_2}\right) V \end{aligned} \right\} \Rightarrow V_I = V_R$$

b)

$$v_i = \left(1 + \frac{R_2}{R_1}\right) \cdot -\frac{R_1}{R_2} v_1 + \left(1 + \frac{R_1}{R_2}\right) v_2 = \left(1 + \frac{R_1}{R_2}\right) (v_2 - v_1) = 2 \left(1 + \frac{R_1}{R_2}\right) v_2$$

$$a_1 = 2 \left(1 + \frac{R_1}{R_2}\right) = 20$$

c) Za  $v_1 = v_2$  iz prethodnog izraza se dobija  $v_i = 0 \Rightarrow a_2 = 0$

$$\text{d) Za } v_1 = v_2 = V, V_I = V_R, \quad V_{I1} = -\frac{R_2}{R_1} V_R + \left(1 + \frac{R_2}{R_1}\right) V = \frac{10V - V_R}{9}$$

$$\frac{10V_{\min} - V_R}{9} = V_{OL} \Rightarrow V_{\min} = \frac{9V_{OL} + V_R}{10} = 0.34V$$

$$V_{\max} = \frac{9V_{OH} + V_R}{10} = 4.66V$$