

## REŠENJA:

1. a)  $V_G = R_G I_G = 5\text{k}\Omega \times 0,5\text{mA} = 2,5\text{V}$  Ako se zanemari amplituda napona  $v_g$ , minimalni napon drejna je  $V_G - V_t = 1,5\text{V}$ .  
 $V_{CC} - 1,5\text{V} - R_{Dopt} I_G = 2 I R_{Dopt} \Rightarrow R_{Dopt} = 8,5\text{V} / 2,5\text{mA} = 3,4\text{k}\Omega$ .


b)  $a_v = -v_d / v_g = -g_m R_D = -\sqrt{2 I_B} \times R_D = -2\text{mS} \times 7\text{k}\Omega = -14$ .

2. Beleške za predavanja, „7\_Strujni\_izvori\_i\_aktivno\_opterecenje.pdf“, slajd 4.

$$I_{IZL} R_E = V_T \ln \left( \frac{I_{REF}}{I_{IZL}} \right) \Rightarrow I_{REF} = I_{IZL} e^{I_{IZL} R_E / V_T} = 10\mu\text{A} e^{10\mu\text{A} \cdot 5\text{k}\Omega / 25\text{mV}} = 10\mu\text{A} e^2 = 73,89\mu\text{A}$$

3. Beleške za predavanja, 13\_Regulator\_(stabilizator)\_napona.pdf, slajdovi 4, 5, 6.

4. a) i b)

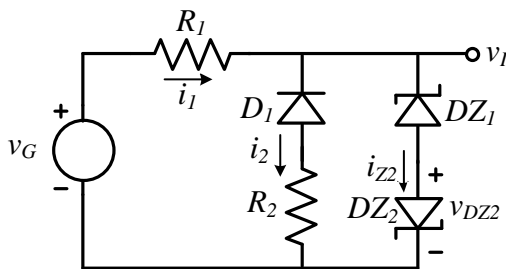

I  $-15\text{V} \leq v_G < V_1$ , DZ1 i D1 direktno polarisane, DZ2 inverzno polarisana

$$v_I = -V_Z - V_D = -5,4\text{V}$$

$$\left. \begin{aligned} i_1 &= \frac{v_G + V_Z + V_D}{R_1} \\ i_2 &= \frac{-V_Z - V_D + V_D}{R_2} = -\frac{V_Z}{R} \end{aligned} \right\} \Rightarrow P_{Z2} = v_{DZ2} \cdot i_{Z2} = -\frac{V_Z}{R} (v_G + 2V_Z + V_D)$$

$$i_{Z2} = i_1 - i_2 = \frac{v_G + 2V_Z + V_D}{R} \quad v_{DZ2} = -V_Z$$

Zener diode su polarisane na ovaj način dok god je  $i_{Z2} < 0$ . Pri ulaznom naponu  $V_1$  struja  $i_{Z2}$  pada na 0 i dolazi do gašenja zener dioda.

$$i_{Z2}(V_1) = 0 \Rightarrow \frac{V_1 + 2V_Z + V_D}{R} = 0 \Rightarrow V_1 = -(2V_Z + V_D) = -10,1\text{V}$$

II  $V_1 \leq v_G < -V_D$ , D1 direktno polarisana, DZ1 i DZ2 isključene

$$i_{Z2} = 0 \Rightarrow P_{Z2} = 0$$

$$v_I = R_2 \frac{v_G + V_D}{R_1 + R_2} - V_D = \frac{v_G - V_D}{2}$$

III  $-V_D \leq v_G < V_Z + V_D$ , D1, DZ1 i DZ2 isključene

$$i_{Z2} = 0 \Rightarrow P_{Z2} = 0$$

$$v_I = v_G$$

IV  $V_Z + V_D \leq v_G \leq 15\text{V}$ , D1 isključena, DZ1 inverzno polarisana, DZ2 direktno polarisana

$$\left. \begin{aligned} i_{Z2} &= \frac{v_G - V_Z - V_D}{R_1} \\ v_{DZ2} &= V_D \end{aligned} \right\} \Rightarrow P_{Z2} = \frac{V_D}{R} (v_G - V_Z - V_D)$$

$$v_I = V_Z + V_D = 5,4\text{V}$$

5.

a)

$$v_X = v_A - R \frac{v_B - v_A}{R} = 2v_A - v_B$$

$$v_I = v_X - \left( \frac{v_B - v_A}{R} - \frac{v_X}{R_X} \right) R = \left( 3 + \frac{2R}{R_X} \right) v_A - \left( 2 + \frac{R}{R_X} \right) v_B$$

b)  $v_B = V_m \sin(2\pi ft + \pi) = -V_m \sin(2\pi ft) = -v_A$

$$v_I = \left( 5 + \frac{3R}{R_X} \right) v_A = \left( 5 + \frac{3R}{R_X} \right) V_m \sin(2\pi ft) \leq V_{CC} \Rightarrow R_X \geq \frac{3R}{\frac{V_{CC}}{V_m} - 5} = 15\text{k}\Omega$$