

1. Beleške za predavanja, „Dioda.pdf“, slajdovi 29 i 30.

2. Beleške za predavanja, „4\_Pojacavacke\_sprege\_sa\_bipolarnim\_tranzistorima.pdf“, slajdovi 5, 6 i 9.

3. Beleške za predavanja, „6\_Pojacavacke\_sprege\_sa\_MOS\_tranzistorima.pdf“, slajd 10 i „7\_Strujni\_izvori\_i\_aktivno\_opterecenje.pdf“, slajd 3.

4.

a), b)

$-12V \leq v_G < V_1$ , D1 – ON, DZ – na granici provođenja, sa nultom strujom

$$v_P = -V_D = -0.7V, i_Z = 0 \Rightarrow P_Z = 0$$

Dioda D1 se koči pri povećanju napona generatora preko vrednosti  $V_1$ . Na granici zakočenja važi:

$$\frac{R_P}{R_G + R_P} V_1 = -V_D \Rightarrow V_1 = -(1 + \frac{R_G}{R_P}) V_D = -2V_D = -1.4V$$

$V_1 \leq v_G < V_2$ , D1 – OFF, DZ – OFF

$$v_P = -\frac{R_P}{R_G + R_P} v_G = -\frac{v_G}{2}, i_Z = 0 \Rightarrow P_Z = 0$$

Pri naponu generatora  $V_2$  počinje da vodi dioda DZ. Na granici provođenja važi:

$$\frac{R_P}{R_G + R_P} V_2 = V_Z \Rightarrow V_2 = (1 + \frac{R_G}{R_P}) V_Z = 2V_Z = 9.4V$$

$V_2 \leq v_G \leq 12V$ , D1 – OFF, DZ – ON

$$\frac{v_G - v_P}{R_G} = \frac{v_P - V_Z}{R} + \frac{v_P}{R_P} \Rightarrow v_P = \frac{\frac{v_G}{R_G} + \frac{V_Z}{R}}{\frac{1}{R_G} + \frac{1}{R} + \frac{1}{R_P}} = \frac{v_G + V_Z}{3}$$

$$i_Z = \frac{v_P - V_Z}{R} = \frac{v_G - 2V_Z}{3R} \Rightarrow P_Z = V_Z i_Z = \frac{V_Z}{3R} v_G - \frac{2V_Z^2}{3R}$$

c)

$0 < R_P < R_{P1}$ , DZ – OFF, D1 – OFF

$$v_P = \frac{R_P}{R_G + R_P} V_G = \frac{1}{1 + \frac{R_G}{R_P}} V_G$$

Pri otpornosti  $R_{P1}$  dioda DZ počinje da vodi. Na granici provođenja važi:

$$\frac{1}{1 + \frac{R_G}{R_{P1}}} V_G = V_Z \Rightarrow R_{P1} = \frac{R_G}{\frac{V_G}{V_Z} - 1} = 887\Omega$$

$R_{P1} \leq R_P < \infty$ , DZ – ON, D1 – OFF

$$\frac{V_G - v_P}{R_G} = \frac{v_P - V_Z}{R} + \frac{v_P}{R_P} \Rightarrow v_P = \frac{\frac{V_G}{R_G} + \frac{V_Z}{R}}{\frac{1}{R_G} + \frac{1}{R} + \frac{1}{R_P}}$$

$$v_{P\max} = v_P(R_P \rightarrow \infty) = \frac{\frac{V_G}{R_G} + \frac{V_Z}{R}}{\frac{1}{R_G} + \frac{1}{R}} = \frac{V_G + V_Z}{2} = 7.35V$$

5.

$$a) -\frac{I_C}{\beta_F} R_B - V_{BE} - \frac{\beta_F + 1}{\beta_F} I_C R_E = V_{EE} \Rightarrow R_E = -\frac{\beta_F}{(\beta_F + 1) I_C} \left( \frac{I_C}{\beta_F} R_B + V_{BE} + V_{EE} \right) = 11.2 \text{ k}\Omega$$

$$b) r_{ce} = \frac{V_A}{I_C} = 75 \text{ k}\Omega, r_{\pi} = \frac{\beta_0 V_T}{I_C} = 2.5 \text{ k}\Omega$$

$$\left. \begin{aligned} v_p &= (\beta_0 + 1) i_b (r_{ce} \parallel R_E \parallel R_P) \\ i_b &= \frac{v_u}{r_{\pi} + (\beta_0 + 1)(r_{ce} \parallel R_E \parallel R_P)} \end{aligned} \right\} \Rightarrow a_v = \frac{v_p}{v_u} = \frac{(\beta_0 + 1)(r_{ce} \parallel R_E \parallel R_P)}{r_{\pi} + (\beta_0 + 1)(r_{ce} \parallel R_E \parallel R_P)} = 0.995$$

$$\left. \begin{aligned} i_u &= \frac{v_u}{r_{\pi} + (1 + \beta_0)(r_{ce} \parallel R_E \parallel R_P)} \\ i_p &= \frac{v_p}{R_P} \end{aligned} \right\} \Rightarrow a_i = \frac{i_p}{i_u} = \frac{r_{\pi} + (1 + \beta_0)(r_{ce} \parallel R_E \parallel R_P)}{R_P} \frac{v_p}{v_u} = \frac{(1 + \beta_0)(r_{ce} \parallel R_E \parallel R_P)}{R_P} = 49.85$$

c)

Otpornost koja se vidi iz baze tranzistora je  $R_X = r_{\pi} + (1 + \beta_0)(r_{ce} \parallel R_E \parallel R_P) = 500 \text{ k}\Omega$ .

$$v_u = \frac{R_B \parallel R_X}{R_g + R_B \parallel R_X} v_g = 0.91 v_g \Rightarrow a_{vuk} = \frac{v_p}{v_g} = a_v \frac{v_u}{v_g} = 0.91 a_v = 0.905$$

$$i_u = \frac{R_B}{R_X + R_B} i_g = 0.98 i_g \Rightarrow a_{iuk} = \frac{i_p}{i_g} = a_i \frac{i_u}{i_g} = 0.98 a_i = 48.85$$

$$d) R_u = R_g + R_B \parallel R_X = 10.8 \text{ k}\Omega$$

$$e) R_i = r_{ce} \parallel R_E \parallel \frac{r_{\pi} + R_B \parallel R_g}{1 + \beta_0} = 33.6 \Omega$$