

1. Beleške za predavanja, „2\_Dioda.pdf“, slajdovi 35, 37 i 39.

a)  $v_{p\text{eff}} = (240 \cdot \sqrt{2}/10) - V_D = 240 \cdot \sqrt{2}/10;$

b)  $v_{p\text{eff}} = 24V .$

2. Beleške za predavanja, „3\_Bipolarni\_tranzistor.pdf“, slajdovi 18 i 25.

3.

a)

$$V_{GS2} = V_{GS1} \Rightarrow I_{M2} = I_{M1} \Rightarrow I_{IZL} = I_{REF} = 20\mu A$$

$$V_{I\text{min}} = 2\sqrt{2I_{IZL}/B} + V_T = 2V$$

b)

$$v_{g4} = -g_{m1}r_{ds1}v_{gs1} \quad v_{s4} = v_{gs1} \quad v_{gs4} = -(1 + g_{m1}r_{ds1})v_{gs1}$$

$$v_{gs1} = \left( \frac{1}{g_{m2}} \parallel r_{ds2} \right) i_t$$


$$v_t = v_{gs1} - g_{m4}r_{ds4}v_{gs4} + r_{ds4}i_t$$

$$v_t = \left( \frac{1}{g_{m2}} \parallel r_{ds2} \right) i_t + g_{m4}r_{ds4} (1 + g_{m1}r_{ds1}) \left( \frac{1}{g_{m2}} \parallel r_{ds2} \right) i_t + r_{ds4}i_t$$

$$R_{izl} = \frac{v_t}{i_t} = \left[ 1 + g_{m4}r_{ds4} (1 + g_{m1}r_{ds1}) \right] \left( \frac{1}{g_{m2}} \parallel r_{ds2} \right) + r_{ds4}$$

$$g_m = \sqrt{2I_{IZL}B} = 80\mu S \quad g_m r_{ds} = 8$$
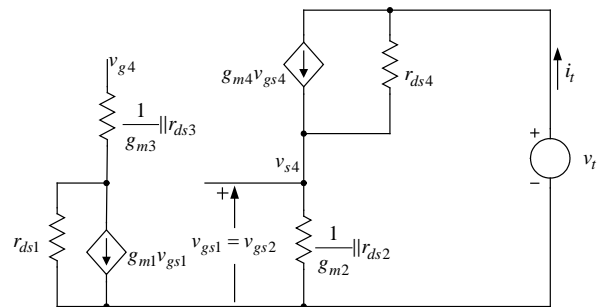
$$R_{izl} = 73 \times 11,1k\Omega + 100k\Omega = 911,1k\Omega$$



4.

I  $-10V \leq v_U < -V_D$ , DZ direktno polarisana, M1 isključen

$$i_Z = \frac{v_U + V_D}{R_G}$$

$$i_D = 0$$

$$v_I = V_{DD}$$

II  $-V_D \leq v_U < V_T$ , DZ je isključena, M1 isključen

$$i_Z = 0$$

$$i_D = 0$$

$$v_I = V_{DD}$$

III  $V_T \leq v_U < V_Z$ , DZ je isključena, M1 vodi u zasićenju (po uslovu zadatka)

$$i_Z = 0$$

$$i_D = \frac{B}{2}(v_U - V_T)^2, \quad i_D(V_Z) = 4mA$$

$$v_I = V_{DD} - i_D R_D$$

IV  $V_Z < v_U \leq 10V$ , DZ inverzno polarisana i vodi u probuju, M1 vodi u zasićenju (po uslovu zadatka)

$$i_Z = \frac{v_U - V_Z}{R_G}$$

$$i_D = \frac{B}{2}(V_Z - V_T)^2 = 4mA$$


$$v_I = V_{DD} - i_D R_D$$

Potrebno je obezbediti da tranzistor ne ulazi u triodnu oblast odnosno da važi:

$$v_{DG1} \geq -V_T \Rightarrow V_{DD} - i_D R_D - V_Z \geq -V_T$$

$$R_D \leq \frac{V_{DD} + V_T - V_Z}{i_D} = 1.425 \text{ k}\Omega$$

5.

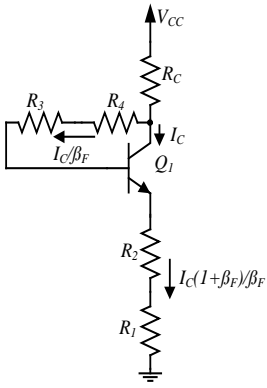

$$\text{a) } I_C = \frac{V_{CC} - V_{BE}}{\left(1 + \frac{1}{\beta_F}\right) R_C + (R_3 + R_4) \frac{1}{\beta_F} + \frac{(1 + \beta_F)}{\beta_F} (R_2 + R_1)} = 937 \mu\text{A}$$


$$V_{CE} = V_{BE} + (R_3 + R_4) \frac{I_C}{\beta_F} = 1.07 \text{ V} > V_{CES}$$

$$\text{b) } r_\pi = \frac{\beta_0 V_T}{I_C} = 5.34 \text{ k}\Omega$$

$$v_P = -\beta_0 i_b (R_C \parallel R_4 \parallel R_P)$$

$$i_b = \frac{v_g}{r_\pi + (1 + \beta_0) R_2}$$
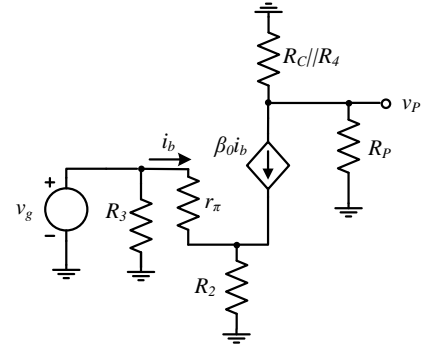
$$a_v = \frac{v_P}{v_g} = -\frac{\beta_0 (R_C \parallel R_4 \parallel R_P)}{r_\pi + (1 + \beta_0) R_2} = -16.5$$



$$a_i = \frac{i_P}{i_g} = \frac{v_P}{R_P} \frac{R_3 \parallel (r_\pi + (1 + \beta_0) R_2)}{v_g}$$

$$a_i = a_v \frac{R_3 \parallel (r_\pi + (1 + \beta_0) R_2)}{R_P} = -15.5$$

$$\text{c) } R_u = R_3 \parallel (r_\pi + (1 + \beta_0) R_2) = 11.76 \text{ k}\Omega$$

$$\text{d) } R_i = R_C \parallel R_4 = 1.46 \text{ k}\Omega$$