


1.

$$I_{D1} = I; \quad I_{D2} = I_1 - I; \quad r_{D1} = \frac{V_T}{I_{D1}} = \frac{V_T}{I}; \quad r_{D2} = \frac{V_T}{I_{D2}} = \frac{V_T}{I_1 - I};$$

$$\frac{v_i}{v_u} = \frac{r_{D2}}{r_{D1} + r_{D2}} = \frac{\frac{V_T}{I_1 - I}}{\frac{V_T}{I} + \frac{V_T}{I_1 - I}} = \frac{I}{I_1};$$

$$I_1 = 1 \text{ mA}$$
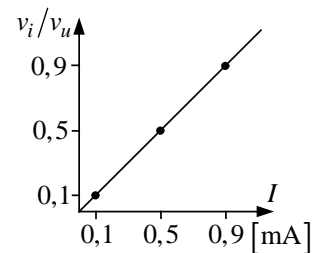
$$I = 0,1 \text{ mA} \Rightarrow v_i/v_u = 0,1; \quad I = 0,5 \text{ mA} \Rightarrow v_i/v_u = 0,5; \quad I = 0,9 \text{ mA} \Rightarrow v_i/v_u = 0,9$$



2. a) Na karakteristici za  $v_{GS} = V_t + 1\text{V}$  u zasićenju je  $i_D = 0,5 \text{ mA}$ .

$$i_D = \frac{B}{2}(v_{GS} - V_t)^2 \Rightarrow B = \frac{2i_D}{(v_{GS} - V_t)^2} = \frac{1 \text{ mA}}{(1\text{V})^2} = 1 \frac{\text{mA}}{\text{V}^2}.$$

b) Sa Slike 2 se vidi da u datoj radnoj tački tranzistor radi u zasićenju.

$$V_t = V_{GS} - \sqrt{2I_D/B} = 3\text{V} - \sqrt{3\text{V}} = 1,268\text{V}.$$

3. Beleške za predavanja, „7\_Strujni\_izvori\_i\_aktivno\_opterecenje.pdf“, slajd 5.

4. a) Za  $v_G < V_{BE}$  Q je zakočen  $\Rightarrow v_B = v_G, v_C = V_{CC}$

Za  $V_{BE} \leq v_G < V_1$  Q je u DAR-u  $\Rightarrow v_B = V_{BE}$


$$i_B = \frac{v_G - V_{BE}}{R_B} \Rightarrow v_C = V_{CC} - R_C \beta_F \frac{v_G - V_{BE}}{R_B}, \quad V_1 \text{ je napon generatora pri kojem dioda počinje da vodi}$$

$$v_G = V_1 \Rightarrow v_{BC} = V_D \Rightarrow V_{BE} - V_{CC} + \beta_F \frac{R_C}{R_B} (V_1 - V_{BE}) = V_D$$

$$V_1 = V_{BE} + \frac{R_B}{\beta_F R_C} (V_{CC} + V_D - V_{BE}) = 0,96\text{V}$$

Za  $v_G > V_1$  dioda vodi  $\Rightarrow v_C = V_{BE} - V_D = 0,4\text{V} \Rightarrow$  Q i dalje u DAR-u  $\Rightarrow v_{BE} = V_{BE}$

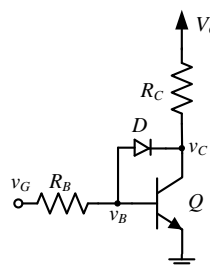b) Za  $v_G \leq V_1$  dioda je zakočena  $\Rightarrow P_D = 0$



Za  $v_G > V_1$  dioda vodi i transistor vodi u DAR-u pa prema tome važi

$$\left. \begin{aligned} \frac{v_G - V_{BE}}{R_B} &= i_B + i_D \\ i_D + \frac{V_{CC} - V_{BE} + V_D}{R_C} &= \beta_F i_B \end{aligned} \right\} \Rightarrow i_D = \frac{\beta_F}{1 + \beta_F} \frac{v_G}{R_B} - \frac{1}{1 + \beta_F} \left( \frac{\beta_F V_{BE}}{R_B} + \frac{V_{CC} - V_{BE} + V_D}{R_C} \right)$$

$$P_D = \begin{cases} 0, & v_G \leq V_1 \\ V_D \left[ \frac{\beta_F}{1 + \beta_F} \frac{v_G}{R_B} - \frac{1}{1 + \beta_F} \left( \frac{\beta_F V_{BE}}{R_B} + \frac{V_{CC} - V_{BE} + V_D}{R_C} \right) \right], & v_G > V_1 \end{cases}$$

5. a)  $V_D = V_{DD} = 12V$

$$V_G = \frac{R_1}{R_1 + R_2} V_{DD} = 8V$$


$$V_{GS} = V_T + \sqrt{\frac{2I_D}{B}} = 2V$$

$$V_G - V_{GS} = I_D R_S \Rightarrow R_S = \frac{V_G - V_{GS}}{I_D} = 6k\Omega$$

$$V_S = V_G - V_{GS} = 6V$$

$$I_D = \frac{B}{2}(V_{GS} - V_T)^2 = 1mA \Rightarrow g_m = \sqrt{2BI_D} = 2mS, r_{ds} = \frac{1}{\lambda I_D} = 100k\Omega$$

b)

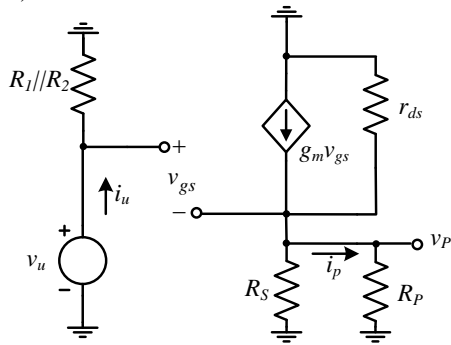

$$\left. \begin{aligned} v_p &= g_m v_{gs} (R_S \parallel R_P \parallel r_{ds}) \\ v_{gs} &= v_g - v_s = v_u - v_p \end{aligned} \right\} \Rightarrow a_v = \frac{v_p}{v_u} = \frac{g_m (R_S \parallel R_P \parallel r_{ds})}{1 + g_m (R_S \parallel R_P \parallel r_{ds})} = 0.88$$

$$\left. \begin{aligned} i_p &= \frac{v_p}{R_P} \\ i_u &= \frac{v_u}{R_1 \parallel R_2} \end{aligned} \right\} \Rightarrow a_i = \frac{i_p}{i_u} = \frac{R_1 \parallel R_2}{R_P} \frac{v_p}{v_u} = \frac{R_1 \parallel R_2}{R_P} a_v = 58.67$$


c)  $v_G(t) = V_G + v_g(t) = V_G + v_u(t) = (8 + 0.1 \sin(2\pi ft))V$

$$v_D(t) = V_D + v_d(t) = V_D = 12V$$

$$v_S(t) = V_S + v_s(t) = V_S + a_v v_u(t) = (6 + 0.088 \sin(2\pi ft))V$$

$$v_P(t) = V_P + v_p(t) = a_v v_u(t) = 0.088V \sin(2\pi ft)$$

d)

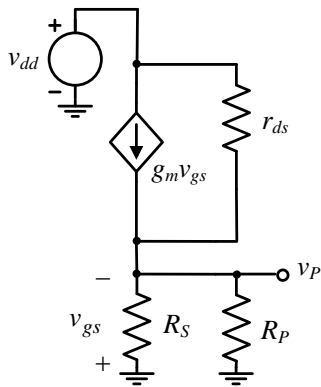

$$\left. \begin{aligned} v_p (G_S + G_P) &= (v_{dd} - v_p) g_{ds} + g_m v_{gs} \\ v_{gs} &= -v_p \end{aligned} \right\} \Rightarrow a_{dd} = \frac{v_p}{v_{dd}} = \frac{g_{ds}}{G_S + G_P + g_{ds} + g_m} = 0.0044$$