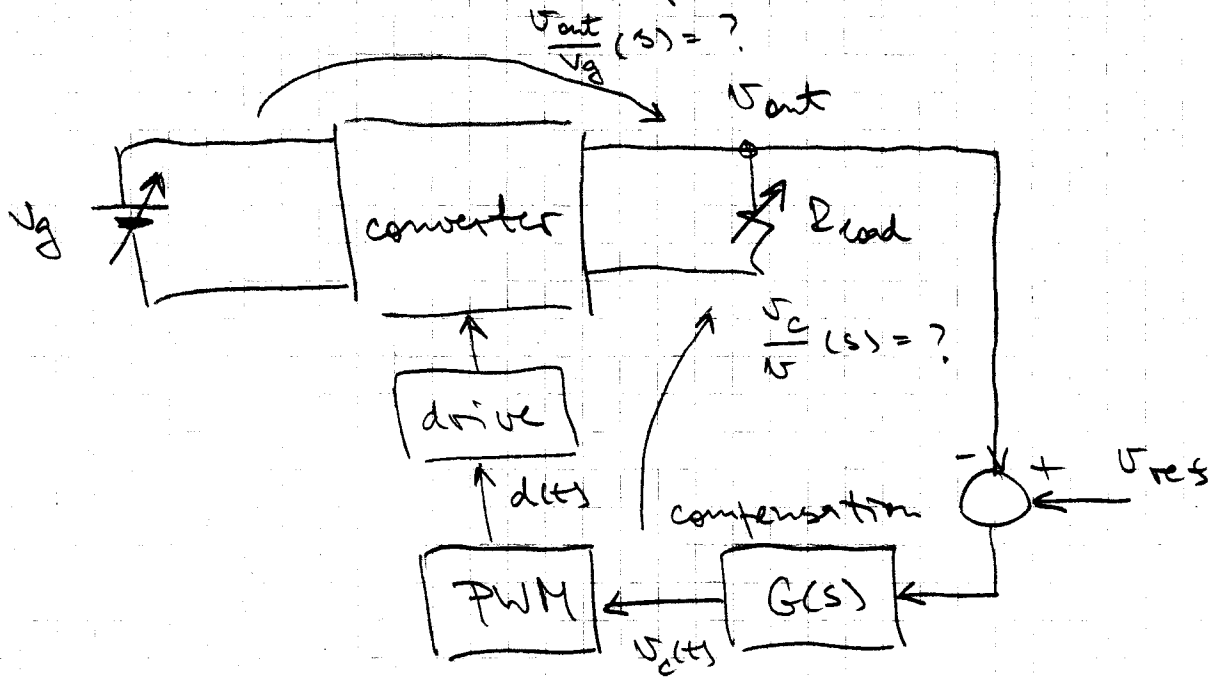


\*

# Yüqünlü DC-DC konverterlərinə

- Transient davranış



- 1 transient overshoot
- 2 setting time
- 3 steady-state regulation

- Crossin: təmizləyici / həyati mövqeyə


- Yüqünlü - cümləyici - tələb və dizayn, nəzərdə tutulan

- Avtomatik idarəetmə:


1) təmizləyici

$$\text{boost, } M(D) = \frac{1}{1-D}$$

- dərəcə  
steady-state

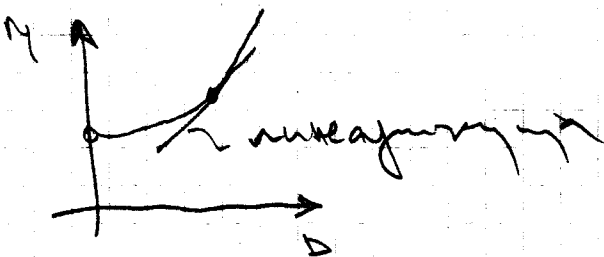

2) ripple (индуктивность и емкость)

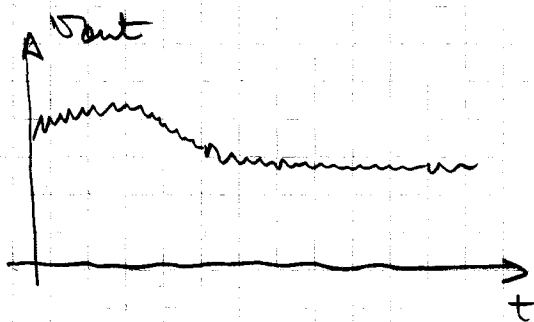


пенетра - neglect ripple

Примеры:

- 1) индуктивность
- 2) емкость


Пример: Buck-boost converter

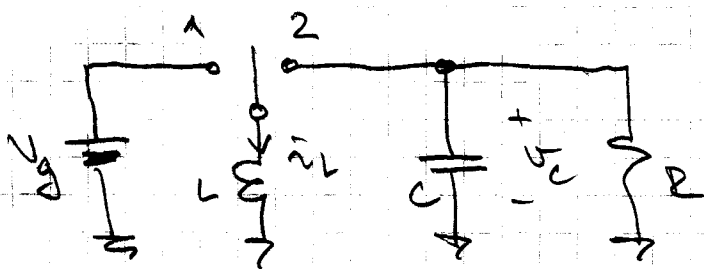

$T_s$  - switching period

$D$  - duty ratio

position 1

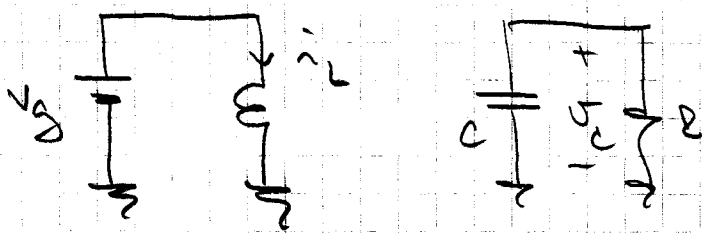


$D T_s$

$$V_L = L \frac{di_L}{dt} = V_g$$

$$i_C = C \frac{dv_C}{dt} = - \frac{V_g}{R}$$

## Position 2

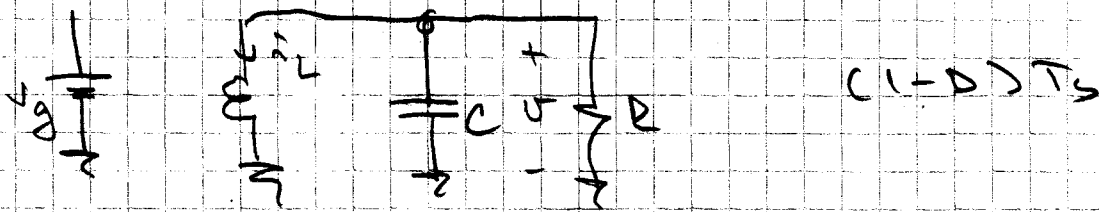

$$U_L = L \frac{di_L}{dt} = \sigma_C$$

$$\dot{\lambda}_C = C \frac{d\sigma_C}{dt} = -\dot{\lambda}_L - \frac{U_g}{R}$$

Integration in  $\lambda_L(T_s) \approx \sigma_C(T_s)$  and  $\phi - 17$  eq  
 $\lambda_L(0), \sigma_C(0) \approx \Delta$

$$\lambda_L(\Delta T_s) = \lambda_L(0) + \Delta T_s \frac{U_g}{L}$$

$$\lambda_C(T_s) = \lambda_C(\Delta T_s) + \Delta' T_s \frac{U_g}{L}$$

↪ due to symmetrical linear ripple approximation

$$\lambda_L(T_s) = \lambda_L(0) + \Delta T_s \frac{U_g}{L} + \Delta' T_s \frac{U_g}{L}$$

$$\lambda_L(T_s) = \lambda_L(0) + \frac{T_s}{L} \underbrace{(\Delta U_g + \Delta' U_g)}_{U_{g,eff}}$$

Roone n defnisaqa

$$\hat{i}_L(nT_s) = \hat{i}_L(nT_s) + \frac{T_s}{L} (D(nT_s) V_g(nT_s) + D'(nT_s) v_c(nT_s))$$

hjet awabwaleto qa ce  $V_g$  n  $v_c$  awajo (qawajetawo) mawajy (tam paxwajy)

Anjoxawajy n wabaja:

$$\frac{di_L}{dt} \approx \frac{\Delta i_L}{\Delta t} = \frac{i_L(n+1)T_s - i_L(nT_s)}{T_s}$$

awawo ce de awajo mawo  $nT_s \rightarrow t$ , wawajy n wabaja

$$\frac{di_L}{dt} \approx \frac{1}{L} (D(t) V_g(t) + D'(t) v_c(t))$$

awawo:

$$L \frac{di_L}{dt} = D V_g + D' v_c = \bar{v}_L$$

awawo n ce njet mawawo

Carilah  $v_c(t)$  :

$$v_c(DT_s) = v(0) - DT_s \frac{v_c}{RC}$$

$$v_c(T_s) = v_c(DT_s) - D' T_s \left( \frac{i_L}{C} + \frac{v_c}{RC} \right)$$

$$v_c(T_s) = v_c(0) - \frac{T_s}{C} \underbrace{\left( \frac{v}{R} + D' i_L \right)}_{= i_c}$$

atasnya jika  $0 < n < 1$ , artinya hanya  
waktu

$$\frac{dv_c}{dt} \approx \frac{\Delta v}{\Delta t} = \frac{v_c((n+1)T_s) - v_c(nT_s)}{T_s}$$

$$\frac{dv_c}{dt} = -\frac{1}{C} \left( \frac{v_c(t)}{R} + D'(t) i_L(t) \right)$$

sekarang

$$C \frac{dv_c}{dt} \approx -\frac{v_c}{R} - D' i_L = i_c$$

- Combine ~~last~~ large-signal dynamical model

$$L \frac{di_L}{dt} = D V_g + D' v_c$$

$$C \frac{dv_c}{dt} = -\frac{v_c}{R} - D' i_L$$

- Nonlinear: multiplication of time-varying quantities,  $D(t)$ ,  $v_c(t)$ ,  $i_L(t)$
- Low-frequency behavior of  $i_L(t)$  &  $v_c(t)$ , ripple filtered out
- Still nonlinear
- Next step: large signal DC and small signal AC models
- DC model bet. phases
- Quiescent operating point

$$v_g(t) = V_g + \hat{v}_g(t)$$

$$d(t) = D_0 + \hat{d}(t)$$

$$i_L(t) = I_{L0} + \hat{i}_L(t)$$

$$v_c(t) = V_{c0} + \hat{v}_c(t)$$

- DC model (large signal)  
transients died out

$$0 = D_0 V_g + D_0' V_c \quad \rightarrow \quad V_c = - \frac{D_0}{D_0'} V_g$$

$$0 = - \frac{V_c}{R} - D_0' I_L \quad \rightarrow \quad I_L = - \frac{V_c}{R D_0'}$$

↑

approx of  $\mu$  is  
 $\mu_{sec} \sim \mu_{sec} \text{ balance}$

- Obs by steady-state transfer functions,  
nonlinear, but who cares

- Perturbation of large-signal dynamical  
model ( $\neq$  large signal DC model)

$$L \frac{d(I_L + \hat{i}_L)}{dt} = (D_0 + \hat{d}) (V_g + \hat{v}_g) + (D_0' - \hat{d}) (V_c + \hat{v}_c)$$

$$L \left( \frac{dI_L}{dt} + \frac{d\hat{i}_L}{dt} \right) = \underbrace{(D_0 V_g + D_0' V_c)}_{\text{dc terms}} +$$

$$+ \underbrace{D_0 \hat{v}_g + \hat{d} V_g - \hat{d} V_c + D_0' \hat{v}_c}_{\text{1st order ac terms}} +$$

$$+ \underbrace{\hat{d} \hat{v}_g - \hat{d} \hat{v}_c}_{\text{2nd order ac terms}} \rightarrow \text{neglect}$$

$$L \frac{d\hat{i}_L}{dt} = D_0 \hat{v}_g + D_0' \hat{v}_c + \hat{d} (v_g - v_c)$$

- in case of convergence

$$C \frac{d(v_c + \hat{v}_c)}{dt} = - \frac{v_c + \hat{v}_c}{R} - (D_0' - \hat{d})(I_L + \hat{i}_L)$$

$$C \frac{d\hat{v}_c}{dt} = \underbrace{- \frac{v_c}{R} - D_0' I_L}_{DC}$$

$$\underbrace{- \frac{\hat{v}_c}{R} + \hat{d} I_L - D_0' \hat{i}_L}_{1st \text{ order ac}} + \underbrace{\hat{d} \hat{i}_L}_{2nd \text{ order ac} \rightarrow \text{neglect}}$$

$$C \frac{d\hat{v}_c}{dt} = - \frac{\hat{v}_c}{R} - D_0' \hat{i}_L + \hat{d} I_L$$

$$L \frac{d\hat{i}_L}{dt} = D_0 \hat{v}_g + D_0' \hat{v}_c + \hat{d} (v_g - v_c)$$

$$C \frac{d\hat{v}_c}{dt} = - \frac{\hat{v}_c}{R} - D_0' \hat{i}_L + \hat{d} I_L$$

small-signal ac model



## - Small signal ac models

1 integrator

2 delay element

3 transfer values of delay element zero in phase curve (response zero in time 2!)

4 because of study point

5 point is high or low, because of a system frequency

## - Summary of the models

- large signal dynamic model

- large signal DC model

- small signal AC model

## - Summary of Procedure

1° Measure  $i_L(T_s)$  and  $v_C(T_s)$  by observation of  $i_L(0)$ ,  $v_C(0)$  and  $D$

2° Approximation where  $\frac{di_L}{dt} \approx \frac{i_L(T_s) - i_L(0)}{T_s}$

$\frac{dv_C}{dt} \approx \frac{v_C(T_s) - v_C(0)}{T_s}$ ; result: nonlinear

state equations, nonlinear dynamic model

3° Perturbation and Linearization of nonlinear state equations - small signal ac model

- Cukciem paprsta je do najprijemljiva mreza  
 - stanovitaka - linear control theory za  
 neprotokabe perznavaja.

- Primer: njena funkcija  $\frac{\hat{V}_c(s)}{\hat{d}(s)}$

lativoda njena funkcija za small signal  
 ac model

$$sh \hat{i}_L(s) = D'_0 \hat{V}_c(s) + (V_g - V_c) \hat{d}(s) + D_0 \hat{V}_g(s)$$


$$sc \hat{V}_c(s) = -D'_0 \hat{i}_L(s) - \hat{V}_c(s)/R + I_L \hat{d}(s)$$

$\hat{V}_g(s) = 0$  - nena najprijemljiva mreza mreza,  
 mreza cimen, cyrcitovnja  
 emuliramo  $\hat{i}_L(s)$ , penalavo do  $\frac{\hat{V}_c(s)}{\hat{d}(s)}$

$$\frac{\hat{V}_c(s)}{\hat{d}(s)} = -\frac{V_g}{D'_0} \frac{(1 - s \frac{D_0 L}{D'_0 R})}{(1 + s \frac{L}{D'_0 R} + s^2 \frac{LC}{D'_0})}$$

Donatki rangkaian:

Apa saja Watkins - Johnson konfigurasi

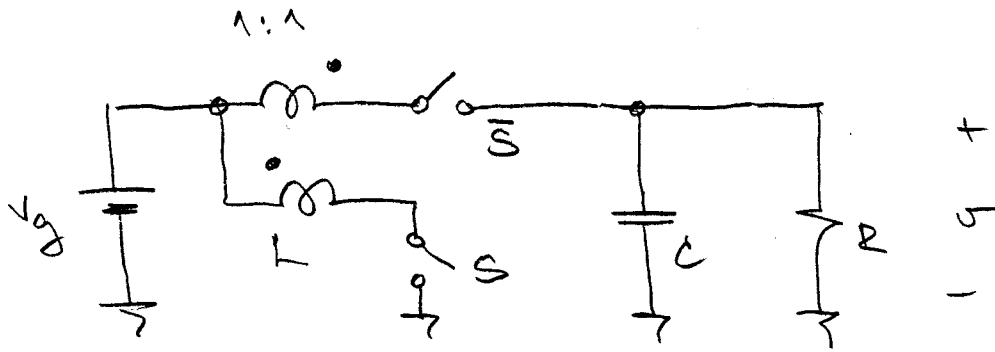

- 1) DC noise
- 2) AC (small signal) noise
- 3) pemrosesan  $S$  dan  $\bar{S}$  (cepat & baik dan  
tidak noise dan akurat)
- 4) noise frekuensi

$$\frac{\hat{V}}{\hat{d}} (S)$$

$$\frac{\hat{V}}{V_g} (S)$$

# The State-Space Averaging Method

- average method - perturbation method
- same terms as above, also in form of
- average method for AC converter

- Average model

- 1) point is "SP3", quasilinear average model  
in average in point is average
- 2) equivalent model for average (model is in  
line, not for average)

- Position 1:

$$\frac{dx}{dt} = A_1 x + B_1 u$$

$$y = C_1 x + E_1 u$$

- Position 2:

$$\frac{dx}{dt} = A_2 x + B_2 u$$

$$y = C_2 x + E_2 u$$

- natural frequencies of converter, regulator, line variations must be small of switching frequency

$$\left. \begin{aligned} \underline{0} &= \underline{A} \underline{x}_0 + \underline{B} \underline{u}_0 \\ \underline{y}_0 &= \underline{C} \underline{x}_0 + \underline{E} \underline{u}_0 \end{aligned} \right\} \text{steady state equations}$$

ifc ifc

$$\underline{A} = \underline{D}_0 \underline{A}_1 + \underline{D}_0' \underline{A}_2$$

$$\underline{B} = \underline{D}_0 \underline{B}_1 + \underline{D}_0' \underline{B}_2$$

$$\underline{C} = \underline{D}_0 \underline{C}_1 + \underline{D}_0' \underline{C}_2$$

$$\underline{E} = \underline{D}_0 \underline{E}_1 + \underline{D}_0' \underline{E}_2$$

$\underline{x}_0, \underline{u}_0, \underline{y}_0, \underline{D}_0$  - y mufraj jaghoj drom

- Ota je nasa nasachara dox nasayya  
 ujoy jaghoj nasa, nasa cy dbe  
 nasa aj nasa

- small signal ac model

$$\frac{d\hat{x}}{dt} = \underline{A} \hat{x} + \underline{B} \hat{u} + ((\underline{A}_1 - \underline{A}_2) \underline{x}_0 + (\underline{B}_1 - \underline{B}_2) \underline{u}_0) \hat{d}$$

$$\hat{y} = \underline{C} \hat{x} + \underline{E} \hat{u} + ((\underline{C}_1 - \underline{C}_2) \underline{x}_0 + (\underline{E}_1 - \underline{E}_2) \underline{u}_0) \hat{d}$$

-  $\hat{x}, \hat{y}, \hat{u}, \hat{d}$  - small signal variations

- ustatone facho, aj nasa, comm nasa  
 ac nasa, aj nasa 2<sup>nd</sup> order terms


- uzložna ce de uz nety kopre, nonlinear large-signal dynamic model

$$\frac{dx}{dt} = (DA_1 + D'A_2) \underline{x} + (DB_1 + D'B_2) \underline{u}$$

- Bendame (čaga u veržuy)

Koprecah state-space averaging u deca small-signal AC model za boost veržuy.

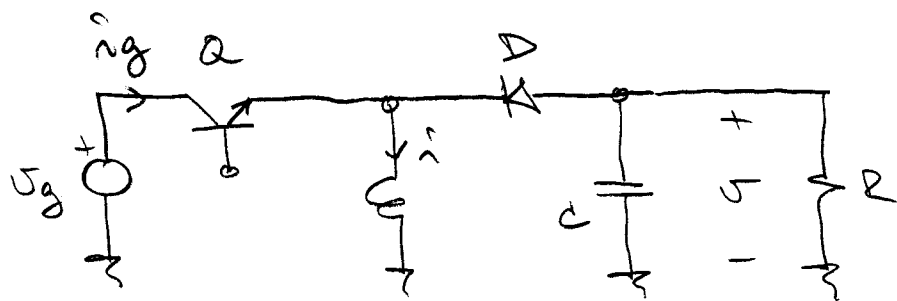- Upruq Buck-Boost veržuy a žyduyua, transistor and diode voltage drops  $V_T$  &  $V_D$




determine both output voltage  $v$  and the line current  $i_g$

output vector  $y(t) = \begin{bmatrix} v(t) \\ i_g(t) \end{bmatrix}$

state vector  $x(t) = \begin{bmatrix} i(t) \\ v(t) \end{bmatrix}$

input vector  $u(t) = \begin{bmatrix} V_g(t) \\ V_T \\ V_D \end{bmatrix}$

a on

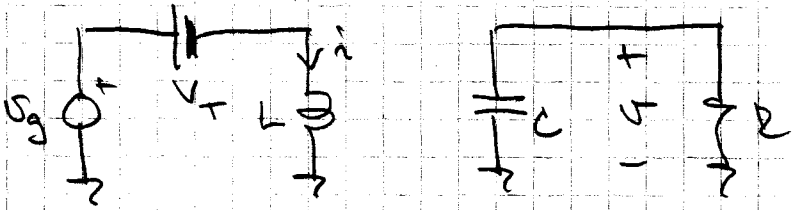

$$L \frac{di}{dt} = u_g - U_T \quad \rightarrow \quad \frac{di}{dt} = \frac{u_g}{L} - \frac{U_T}{L}$$

$$C \frac{dU_T}{dt} = -\frac{U_T}{R} \quad \rightarrow \quad \frac{dU_T}{dt} = -\frac{U_T}{RC}$$


$$\vec{i}_g = i$$

$$\frac{dx}{dt} = \frac{d}{dt} \begin{bmatrix} i \\ U_T \end{bmatrix} = \underbrace{\begin{bmatrix} 0 & 0 \\ 0 & -\frac{1}{RC} \end{bmatrix}}_{A_1} \begin{bmatrix} i \\ U_T \end{bmatrix} +$$

$$\underbrace{\begin{bmatrix} \frac{1}{L} & 0 \\ 0 & 0 \end{bmatrix}}_{B_1} \begin{bmatrix} u_g \\ U_T \end{bmatrix}$$

$$10s = \begin{bmatrix} s \\ \vec{i}_g \end{bmatrix} = \underbrace{\begin{bmatrix} 0 & 1 \\ 1 & 0 \end{bmatrix}}_C \begin{bmatrix} i \\ U_T \end{bmatrix} + \underbrace{\begin{bmatrix} 0 & 0 & 0 \\ 0 & 0 & 0 \end{bmatrix}}_{D_1} \begin{bmatrix} u_g \\ U_T \\ 0 \end{bmatrix}$$

Q of f

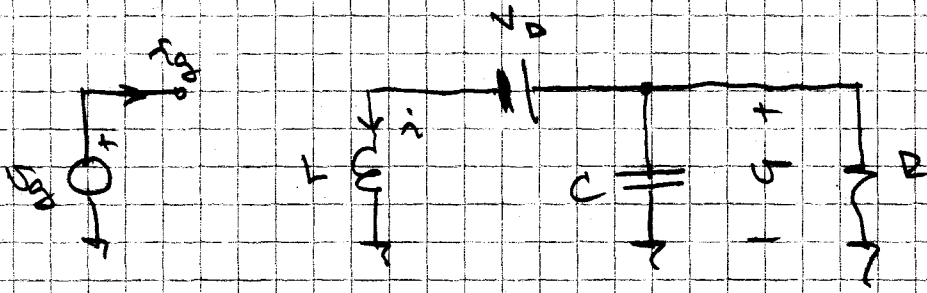

$$L \frac{di}{dt} = u - \Delta$$

$$\frac{di}{dt} = \frac{u}{L} - \frac{\Delta}{L}$$

$$C \frac{du}{dt} = \frac{u}{R} - i_c$$

$$\frac{du}{dt} = \frac{u}{RC} - \frac{i_c}{C}$$

$$i_c = 0$$

$$\frac{d}{dt} \begin{bmatrix} i \\ u \end{bmatrix} = \underbrace{\begin{bmatrix} 0 & 1 \\ -\frac{1}{RC} & -\frac{1}{L} \end{bmatrix}}_{A_2} \begin{bmatrix} i \\ u \end{bmatrix} + \underbrace{\begin{bmatrix} 0 & 0 \\ 0 & 0 \\ 0 & 1 \\ 0 & 0 \end{bmatrix}}_{B_2} \begin{bmatrix} i_s \\ \Delta \end{bmatrix}$$

$$\begin{bmatrix} i \\ u \end{bmatrix} = \underbrace{\begin{bmatrix} 0 & 1 \\ 0 & 0 \end{bmatrix}}_{C_2} \begin{bmatrix} i \\ u \end{bmatrix} + \underbrace{\begin{bmatrix} 0 & 0 \\ 0 & 0 \\ 0 & 1 \\ 0 & 0 \end{bmatrix}}_{E_2} \begin{bmatrix} i_s \\ \Delta \end{bmatrix}$$

Čaka samo izračunati matrice odgovarajuće u  
odgovarajuće matrike



DC Model

$$\underline{0} = \underline{A} \underline{x}_0 + \underline{B} \underline{u}_0$$

$$\underline{y}_0 = \underline{C} \underline{x}_0 + \underline{E} \underline{u}_0$$

AC Model

$$\frac{d\hat{x}}{dt} = \underline{A} \hat{x} + \underline{B} \hat{u} + ((\underline{A}_1 - \underline{A}_2) \underline{x}_0 + (\underline{B}_1 - \underline{B}_2) \underline{u}_0) \hat{d}$$

$$\hat{y} = \underline{C} \hat{x} + \underline{E} \hat{u} + ((\underline{C}_1 - \underline{C}_2) \underline{x}_0 + (\underline{E}_1 - \underline{E}_2) \underline{u}_0) \hat{d}$$

$$\underline{A} = \underline{D}_0 \underline{A}_1 + \underline{D}_0' \underline{A}_2$$

$$\underline{B} = \underline{D}_0 \underline{B}_1 + \underline{D}_0' \underline{B}_2$$

$$\underline{C} = \underline{D}_0 \underline{C}_1 + \underline{D}_0' \underline{C}_2$$

$$\underline{E} = \underline{D}_0 \underline{E}_1 + \underline{D}_0' \underline{E}_2$$

Superstition function:

$$\underline{A} = \begin{bmatrix} 0 & \underline{D}_0' \\ -\underline{C} \underline{D}_0 & -\underline{1} \\ & \underline{D}_0 \end{bmatrix}$$

$$\underline{B} = \begin{bmatrix} \underline{D}_0 \underline{B}_1 & -\underline{D}_0 \underline{B}_2 & -\underline{D}_0' \underline{B}_2 \\ 0 & 0 & 0 \end{bmatrix}$$

$$\underline{C} = \begin{bmatrix} 0 & \underline{1} \\ \underline{D}_0 & 0 \end{bmatrix}$$

$$\underline{A}_1 - \underline{A}_2 = \begin{bmatrix} 0 & -\underline{1} \\ \underline{C} & 0 \end{bmatrix}$$

$$\underline{B}_1 - \underline{B}_2 = \begin{bmatrix} \underline{D}_0 \underline{B}_1 & -\underline{D}_0 \underline{B}_2 & -\underline{D}_0' \underline{B}_2 \\ 0 & 0 & 0 \end{bmatrix}$$

$$A_1 - A_2 = \begin{bmatrix} 0 & 0 \\ 1 & 0 \end{bmatrix}$$

$$E_1 - E_2 = 0$$

$$\begin{aligned} (A_1 - A_2) \underline{x}_0 + (B_1 - B_2) \underline{u}_0 &= \\ &= \begin{bmatrix} -\frac{V_0}{L} \\ \frac{I_0}{C} \end{bmatrix} + \begin{bmatrix} \frac{V_g - V_T + V_D}{L} \\ 0 \end{bmatrix} = \begin{bmatrix} \frac{V_g - V_0 - V_T + V_D}{L} \\ \frac{I_0}{C} \end{bmatrix} \end{aligned}$$

$$(A_1 - A_2) \underline{x}_0 + (E_1 - E_2) \underline{u}_0 = \begin{bmatrix} 0 \\ I_0 \end{bmatrix}$$

problem:

dc model

$$\underline{0} = A \underline{x}_0 + B \underline{u}_0$$

$$\underline{y}_0 = C \underline{x}_0 + E \underline{u}_0$$

$$\begin{bmatrix} 0 \\ 0 \end{bmatrix} = \begin{bmatrix} 0 & \frac{D_1}{L} \\ -\frac{D_1}{C} & -\frac{1}{RC} \end{bmatrix} \begin{bmatrix} I_0 \\ V_0 \end{bmatrix} + \begin{bmatrix} \frac{D_1}{L} & -\frac{D_1}{L} \\ 0 & 0 \\ 0 & \frac{D_1}{L} \end{bmatrix} \begin{bmatrix} V_g \\ V_T \\ V_D \end{bmatrix}$$

$$\underline{y}_0 = \begin{bmatrix} V_0 \\ I_0 \end{bmatrix} = \begin{bmatrix} 0 & 1 \\ D_0 & 0 \end{bmatrix} \begin{bmatrix} I_0 \\ V_0 \end{bmatrix} + \underline{10}$$

facteur de

$$0 = \frac{D_0'}{L} V_0 + \frac{D_0}{L} V_g - \frac{D_0}{L} V_T - \frac{D_0'}{L} V_D$$


$$0 = D_0' V_0 + D_0 V_g - D_0 V_T - D_0' V_D \quad (1)$$

$$0 = -\frac{D_0'}{C} I_0 - \frac{V_0}{RC}$$


$$0 = D_0' I_0 + \frac{V_0}{R} \quad (2)$$

$$I_g = D_0 I_0 \quad (3)$$


Eq. (1) : Loop equation (KVL)

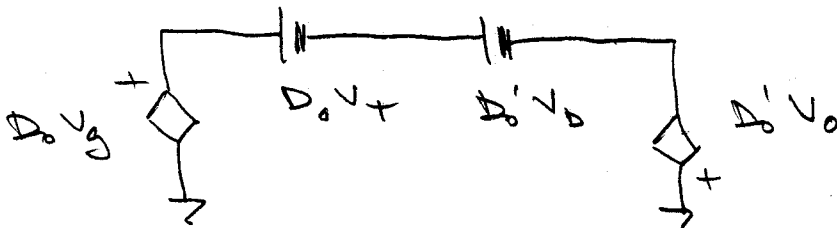



Eq. (2) : Node equation (KCL)

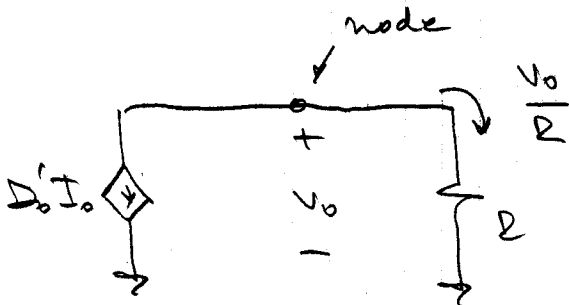

Eq. (3) : Node equation (K3C)

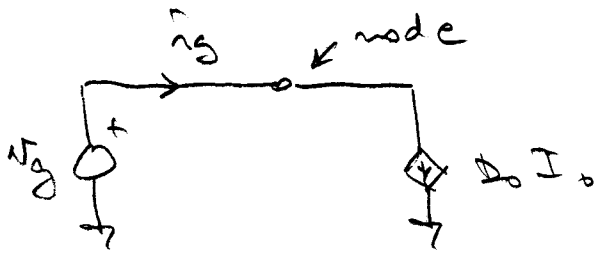

Combine all three circuits together

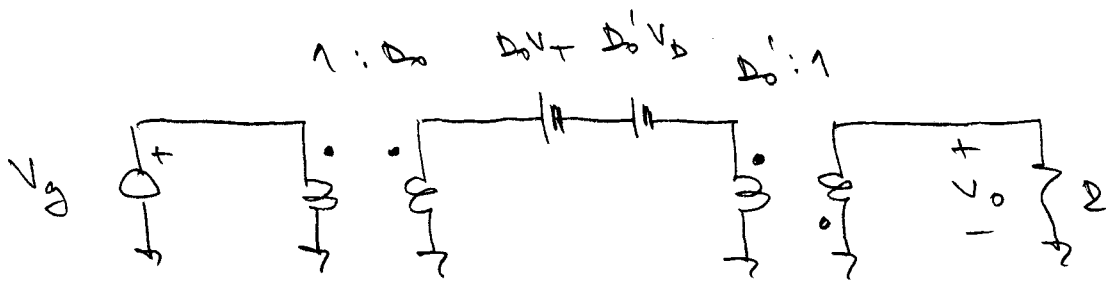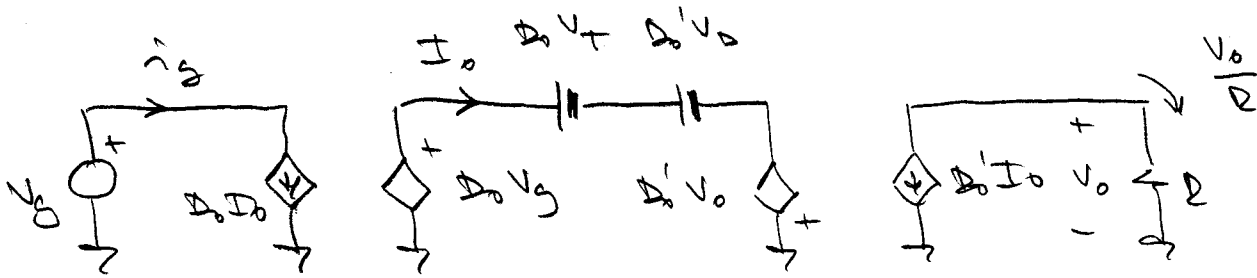

DC transformers

DC model for the Buck-Boost converter

AC Model

$$\frac{dx}{dt} = A \hat{x} + B \hat{u} + ((A_1 - A_2) \hat{x}_0 + (B_1 - B_2) \hat{u}_0) \hat{d}$$

$$\frac{d}{dt} \begin{bmatrix} \hat{i} \\ \hat{g} \end{bmatrix} = \begin{bmatrix} 0 & -\frac{r}{L} \\ -\frac{c}{L} & -\frac{r}{L} \end{bmatrix} \begin{bmatrix} \hat{i} \\ \hat{g} \end{bmatrix} + \begin{bmatrix} 0 & \frac{r}{L} \\ 0 & -\frac{r}{L} \\ 0 & \frac{c}{L} \end{bmatrix} \begin{bmatrix} \hat{g} \\ \hat{g} \\ \hat{g} \end{bmatrix} + \begin{bmatrix} \frac{v_g - v_o - v_T + v_o}{L} \\ \frac{c}{L} \end{bmatrix} \hat{d}$$

matrix notation

$$L \frac{d\hat{i}}{dt} = D_0' \hat{g} + D_0 \hat{g}_g + (v_g - v_o - v_T + v_o) \hat{d} \quad (4)$$


$$C \frac{d\hat{g}}{dt} = -D_0' \hat{i} - \frac{r}{L} \hat{g} + I_0 \hat{d} \quad (5)$$

output relations


$$\begin{bmatrix} \hat{v}_i \\ \hat{g}_g \end{bmatrix} = \begin{bmatrix} 0 & 1 \\ D_0 & 0 \end{bmatrix} \begin{bmatrix} \hat{i} \\ \hat{g} \end{bmatrix} + \begin{bmatrix} 0 \\ I_0 \end{bmatrix} \hat{d}$$

$$\hat{g}_g = D_0 \hat{i} + I_0 \hat{d} \quad (6)$$


Eq. (4): loop equation

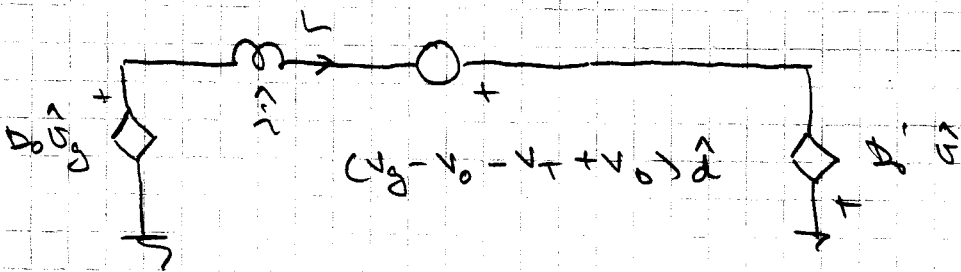




Eq. (5): Node equation

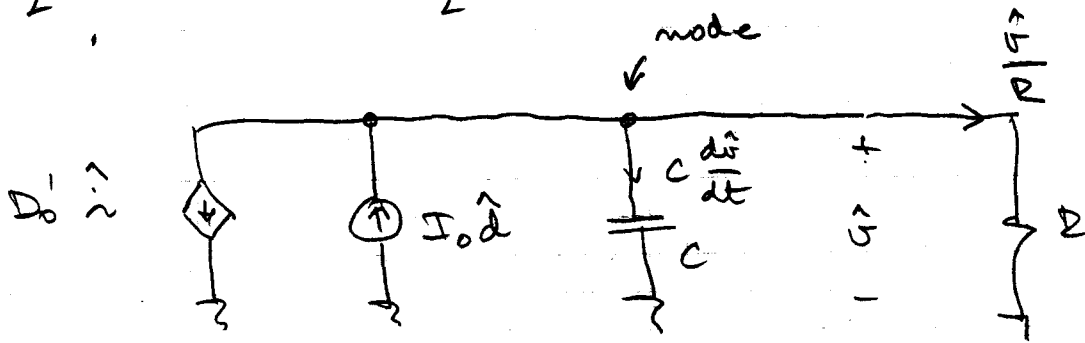

Eq. (6): Node equation

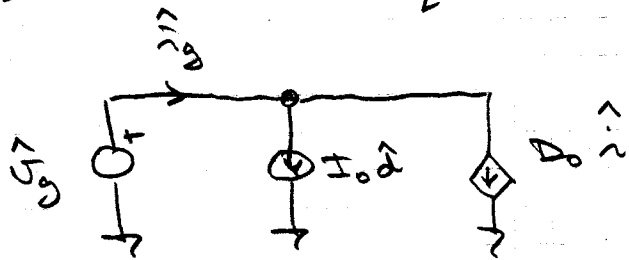

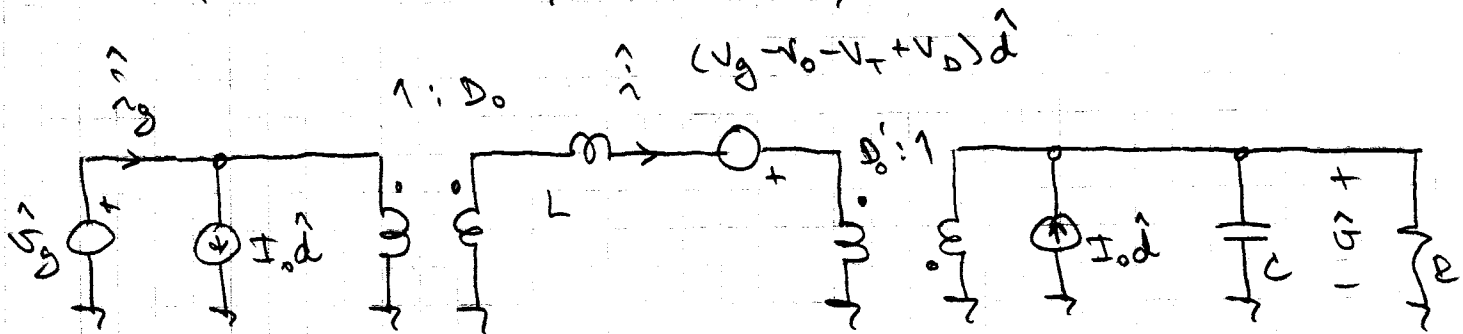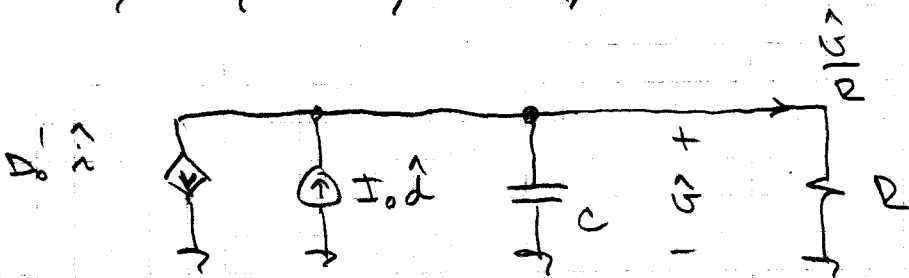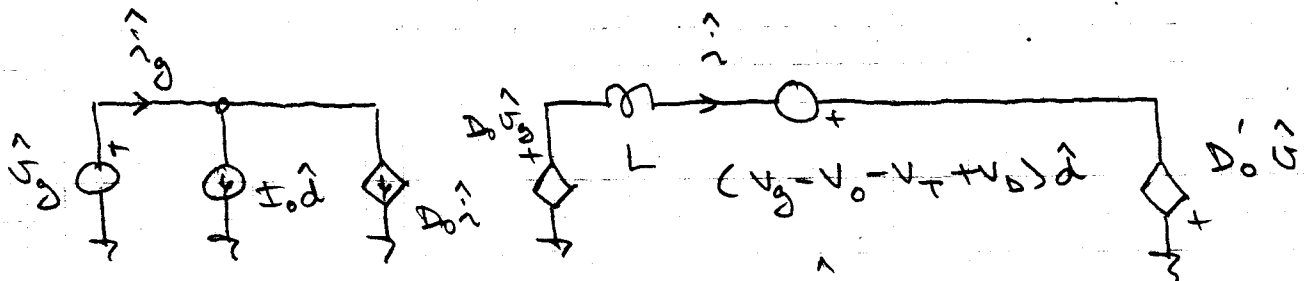Combination of all three ac circuit yields



↑ complete ac model

## Каноничен модел

- една фаза еквивалентна верига за на изход  
напрежение


- Чи напрежение може осъществява функцията:

1) Трансформацията на входната - изходната  
напрежение, идеално са  $\eta = 100\%$

2) Трансферентна функция

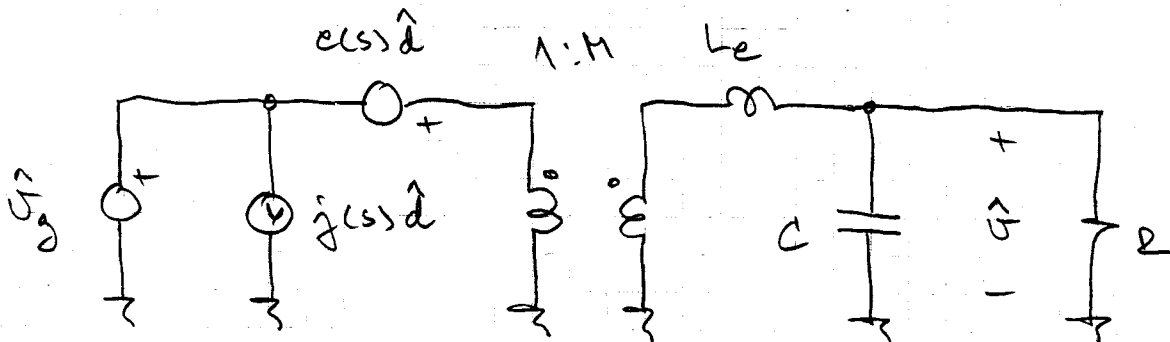3) Константа напрежение  $D$

Като  $\hat{v}$  и  $\hat{i}$  са средно еквивалентна верига




For some common ideal converters

converter	$M(D_0)$	$L_e$	$e(s)$	$\hat{i}(s)$
Buck	$D_0$	$L$	$V_0 / D_0^2$	$V_0 / R$
Boost	$1/D_0'$	$L / D_0'^2$	$V_0 (1 - s \frac{L_e}{R})$	$\frac{V_0}{D_0'^2 R}$
Buck-Boost	$-D_0 / D_0'$	$L / D_0'^2$	$-\frac{V_0}{D_0^2} (1 - s \frac{D_0 L_e}{R})$	$-\frac{V_0}{D_0'^2 R}$

# Circuit Averaging

- method of state-space averaging
- more physical insight
- can be used for non-linear systems and non-linear waveforms
- Example: Boost Converter

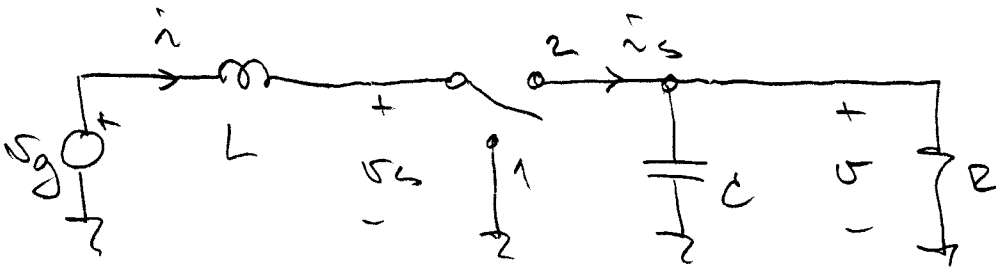

Position 1:  $v_s = 0$   
 $\hat{i}_s = 0$

Position 2:  $v_s = v$   
 $\hat{i}_s = \hat{i}$

- Averaging:

$$\bar{v}_s = \frac{1}{T_s} (0 \cdot DT_s + v \cdot D'T_s)$$


$$\bar{v}_s = D'v$$

$$\bar{i}_s = \frac{1}{T_s} (0 \cdot DT_s + \hat{i} D'T_s)$$


$$\bar{i}_s = D'\hat{i}$$




- Averaged circuit +

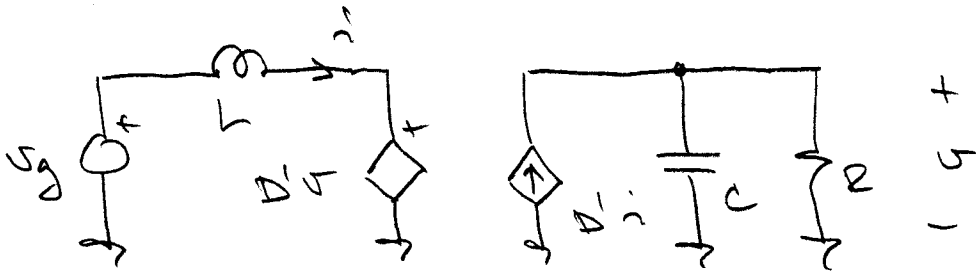

- Average equivalent circuit

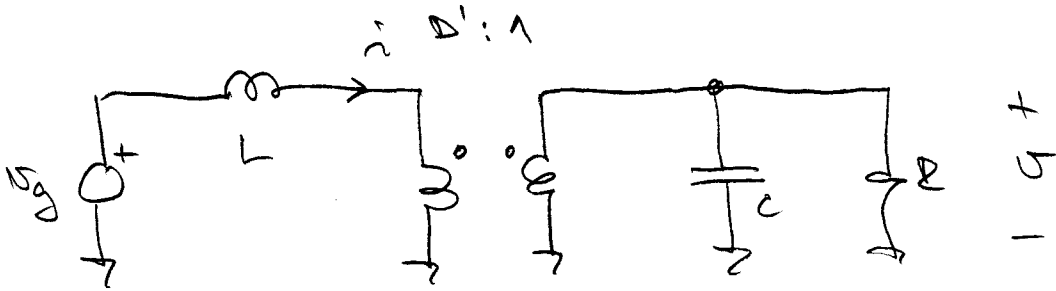


- Regulator transfer function

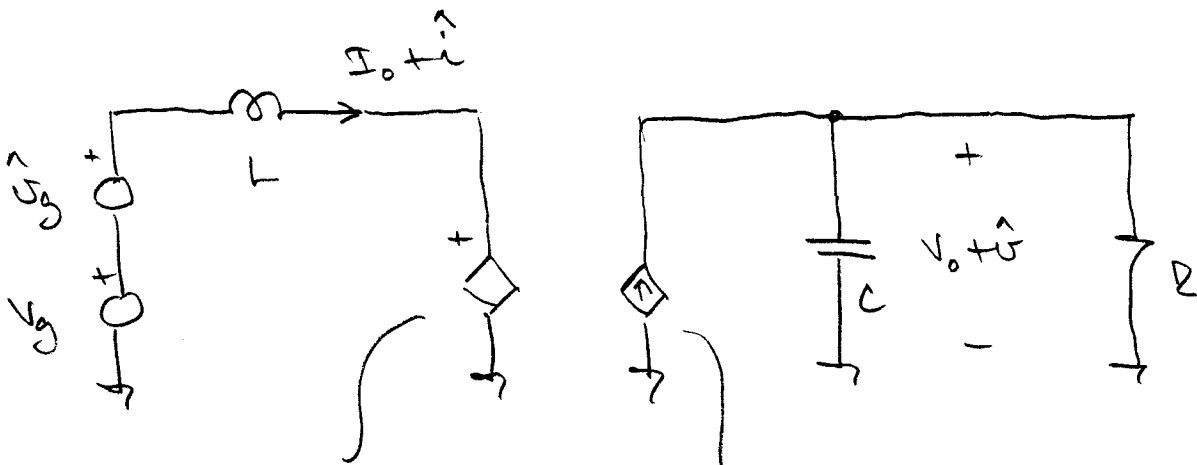


$$\begin{aligned}
 (D'_0 - \hat{d})(v_0 + \hat{v}) &= \\
 &= D'_0 v_0 + \\
 &+ D'_0 \hat{v} - v_0 \hat{d} - \\
 &- \hat{d} \hat{v} = \\
 &= D'_0 (v_0 + \hat{v}) - \\
 &- v_0 \hat{d}
 \end{aligned}$$

$$\begin{aligned}
 (D'_0 - \hat{d})(I_0 + \hat{i}) &= \\
 &= D'_0 I_0 - \\
 &- \hat{d} I_0 + D'_0 \hat{i} - \\
 &- \hat{d} \hat{i} = \\
 &= D'_0 (I_0 + \hat{i}) - \\
 &- \hat{d} I_0
 \end{aligned}$$

- formula using duty cycle

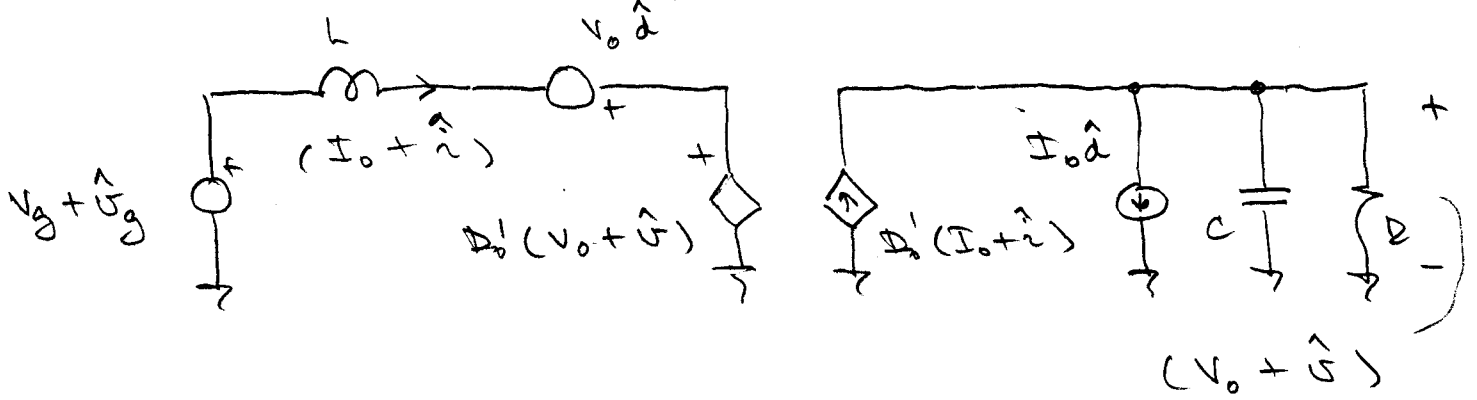

Conversion of duty cycle

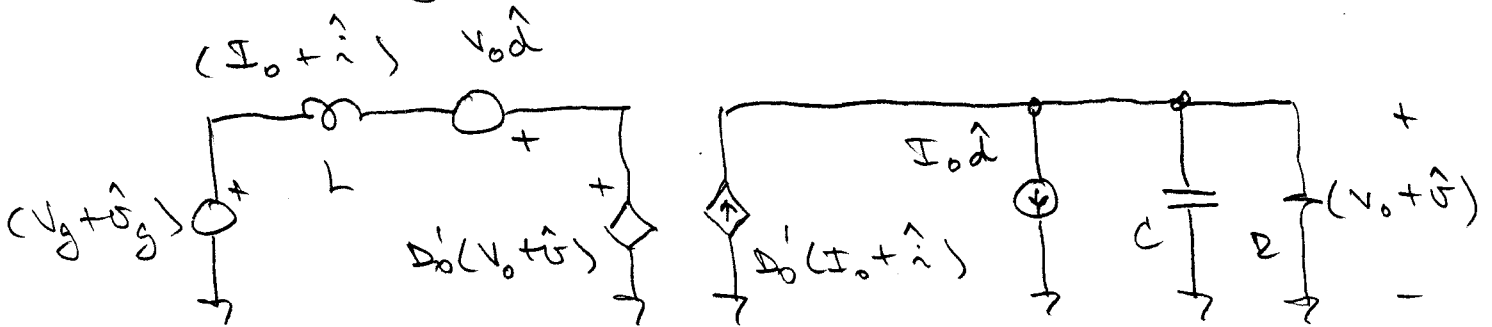

(also is complete averaged & linearized model, canonical form)


- Beata: system also is buck & buck-boost, check canonical form using circuit averaging

# Summary of the circuit averaging procedure


1. Replace switching elements with equivalent current and voltage sources, get an average circuit.
2. Calculate the voltages and currents over the switching period.
3. Reinterpretation in measurement, frequency case transfer.
4. Main advantage is that you get a new circuit.

Beispiel: Bridge Inverter

EXTRA CREDIT

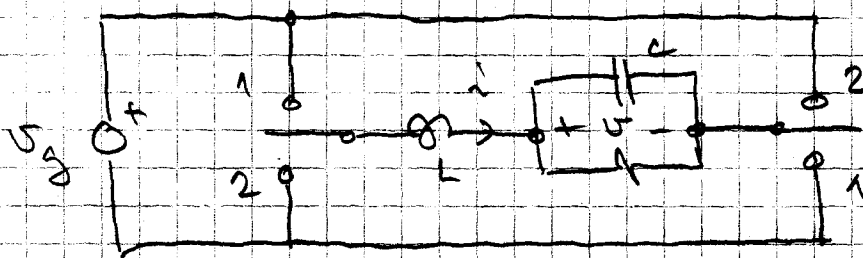

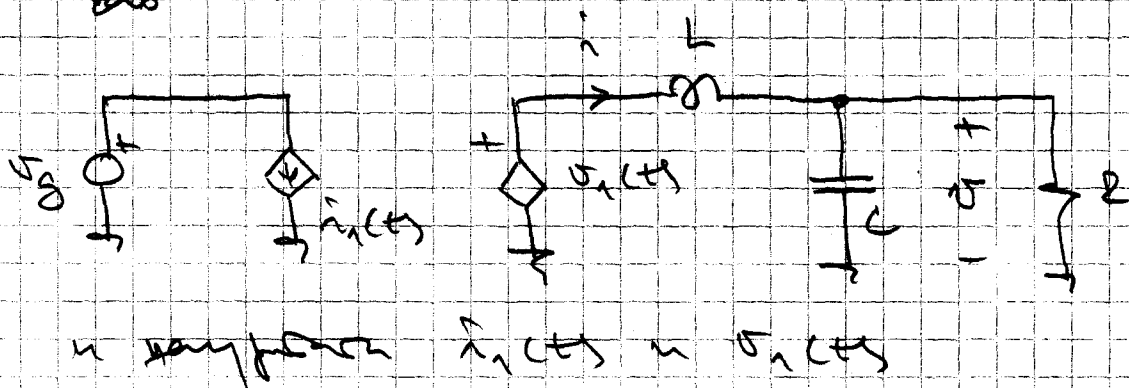a) Darstellung der beiden Zustände der Brücke




8) Analyze large-signal circuit - averaged (averaged) model about working

6) Transfer function and measurement, calculate measurement model

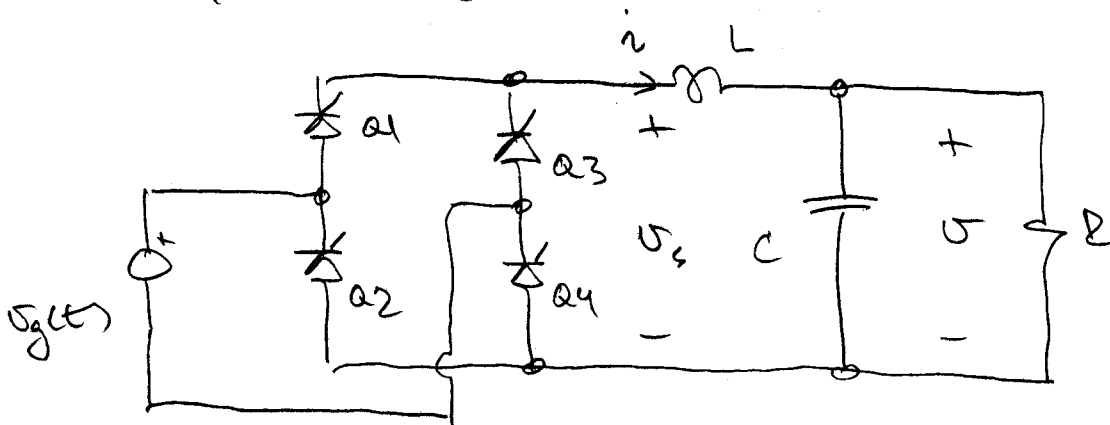2. Small-signal model:

Small-signal relations in a controlled bridge rectifier



a) small-signal transfer functions

$$\frac{\hat{v}}{\hat{v}_g}(s), \quad \frac{\hat{i}}{\hat{v}_g}(s)$$

8) steady-state relation

$$V_o = f(V_{go}, A)$$

b) equivalent circuit

Page 12

$$i = I + \hat{i}(t)$$

$$v = V_0 + \hat{v}(t)$$


$$v_g = (V_{g0} + \hat{v}_g(t)) \sin \omega t$$

- Switching frequency  $\frac{\omega}{2\pi}$  Hz  $\frac{\omega}{4\pi}$


Точные равенства у диодов есть в  
 моменты включения и выключения  
 могут

- Linear ripple approximation лучше работает  
 в том случае, когда частота мала

- Buck - Boost example

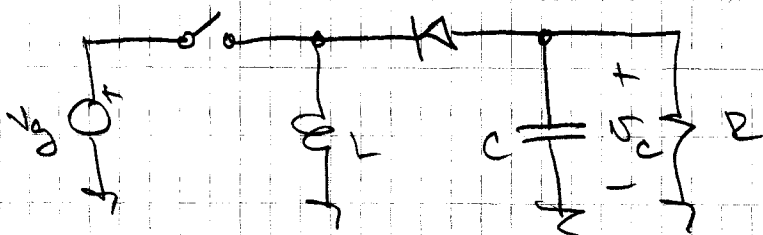

1st Interval,  $\Delta T_s$

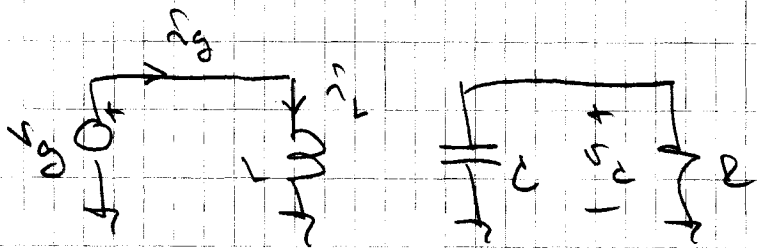


$$L \frac{di_L}{dt} = V_g$$

$$C \frac{dv_C}{dt} = -\frac{v_C}{R}$$

$$i_L = i_C$$

(1)

2nd Interval  $D_2 T_s$

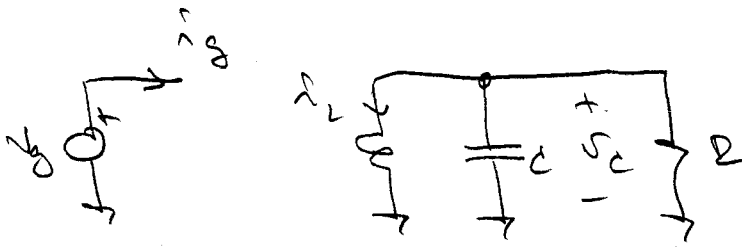


$$L \frac{di_L}{dt} = v_c$$

$$C \frac{dv_c}{dt} = -i_L - \frac{v_c}{R}$$

(2)

$$i_g = 0$$

3rd Interval  $D_3 T_s$

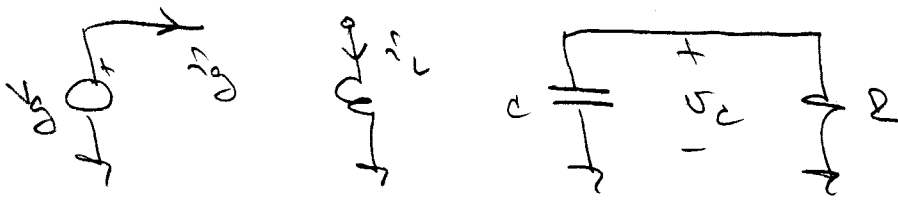



$$L \frac{di_L}{dt} = 0, \quad i_L = 0$$

$$C \frac{dv_c}{dt} = -\frac{v_c}{R}$$

(3)

$$i_g = 0$$

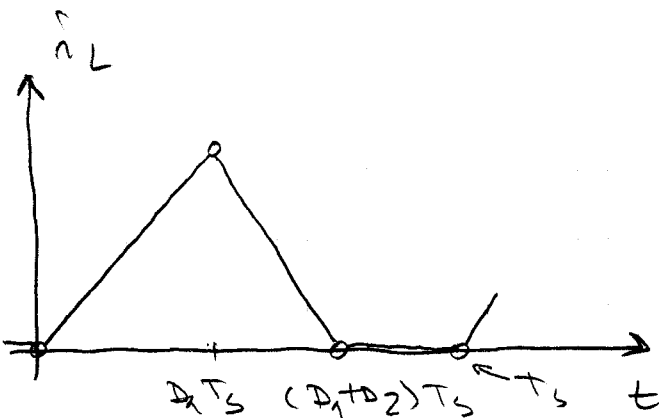

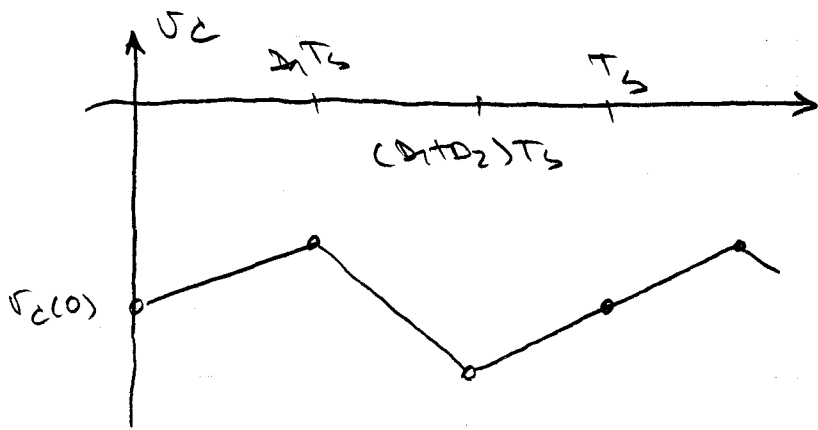

1st interval

$$\hat{i}_L(\Delta T_s) = \hat{i}_{\text{peak}} = \frac{V_g}{L} D_1 T_s \quad (\hat{i}_L(0) = 0) \quad (4)$$

$\underbrace{\hspace{10em}}_{\text{slope time}}$

$$\hat{i}_g = \hat{i}_L$$

$$v_c(\Delta T_s) = v_c(0) - \frac{v_c}{RC} \Delta T_s$$

2nd interval

$$\hat{i}_L((\Delta T_s + D_2) T_s) = \hat{i}_L(\Delta T_s) + \frac{v_c}{L} D_2 T_s$$

$$\hat{i}_g = 0$$

(5)

$$v_c((\Delta T_s + D_2) T_s) = v_c(\Delta T_s) - \underbrace{\left( \frac{\hat{i}_L}{C} + \frac{v_c}{RC} \right)}_{\text{slope}} D_2 T_s$$

however,  $\hat{i}_L$  has increased to  $\hat{i}_L$  over  $D_2 T_s$ ,  
 which you can verify by yourself



$$V_C((D_1+D_2)T_s) \cong V_C(D_1 T_s) -$$

$$- \frac{\bar{I}_D |_{D_2 T_s} + V_C / R}{C} D_2 T_s \cong$$

$$\cong V_C(D_1 T_s) - \frac{\frac{1}{2} \hat{I}_{peak} + \frac{V_C}{R}}{C} D_2 T_s \quad (6)$$

$$\hat{I}_L((D_1+D_2)T_s) = 0 \quad - \text{2nd interval average}$$

$$0 = \hat{I}_L(D_1 T_s) + \frac{V_C}{L} D_2 T_s$$

$$0 = \frac{V_g}{L} D_1 T_s + \frac{V_C}{L} D_2 T_s$$

$$0 = D_1 V_g + D_2 V_C \quad (8)$$

$$\frac{V_C}{V_g} = - \frac{D_1}{D_2} \quad (9)$$

3rd interval

$$\hat{I}_L = 0$$

$$\hat{I}_g = 0$$

$$V_C(T_s) = V_C((D_1+D_2)T_s) - \frac{V_C}{RC} D_3 T_s \quad (10)$$

Dynamical Equation for output (capacitor) voltage

considering Eq. (4), (6) & (10) for  $\delta u$  we get  
output  $v_c(T_s)$  & duty cycle  $v_c(0)$  give

$$v_c(T_s) = v_c(0) - \frac{v_c}{RC} T_s - \frac{\frac{1}{2} \hat{i}_{peak}}{C} D_2 T_s \quad (11)$$

Approximate change in voltage:

$$\frac{dv_c}{dt} \approx \frac{\Delta v_c}{\Delta t} = \frac{v_c(T_s) - v_c(0)}{T_s}$$

From (11)


$$\frac{v_c(T_s) - v_c(0)}{T_s} = -\frac{v_c}{RC} - \frac{D_2 \hat{i}_{peak}}{2C} \quad (12)$$

$$\hat{i}_{peak} = \frac{V_g}{L} D_1 T_s$$

$$C \frac{dv_c}{dt} = -\frac{v_c}{R} - \frac{D_1 D_2 V_g T_s}{2L} \quad (13)$$

Equation for the average input current  $\bar{i}_g$ :

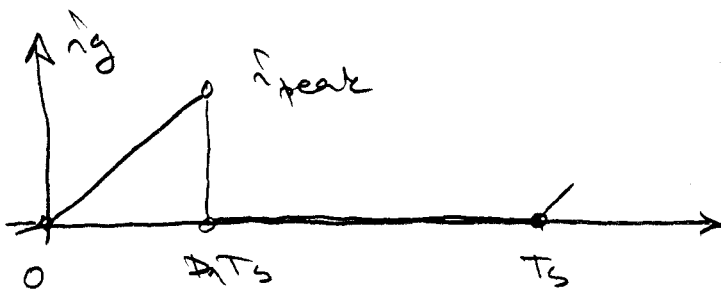(Assumes conduction mode, input & output properties)



$$\begin{aligned} \bar{i}_g &= \frac{1}{T_s} \int_0^{T_s} i_g(\tau) d\tau = \frac{1}{T_s} \left( \frac{1}{2} i_{peak} \right) D_1 T_s = \\ &= \frac{D_1^2 V_g T_s}{2L} \end{aligned} \quad (14)$$

Unknowns:

$$(15) \quad D_1 V_g + D_2 V_c = 0 \quad \text{us Eq. (8)}$$

expression for  $D_2$

$$(16) \quad C \frac{dv_c}{dt} = -\frac{V_c}{R} - \frac{D_1 D_2 V_g T_s}{2L} \quad \text{us Eq. (13)}$$

charge balance

$$(17) \quad \bar{i}_g = \frac{D_1^2 V_g T_s}{2L} \quad \text{us Eq. (14)}$$

average input current

Also je nemušenost susedu daju  $D_1, D_2, V_g$   
 u  $V_c$  koje ne mogu biti konstantne y partu u  
 kondukcijama

Note: Uena expression za  $\frac{di_L}{dt}$   $\frac{di_L}{dt} = 0$ ,  
 namo  $i_L(0) = i_L(T_s) = 0$

Perpetual: U jednaenja koje se pojavljuju u  
 namo kao partu u, zadržati eq C

### Small - Signal AC Equations

- perturb & linearize

$$D_1(t) = D_{10} + \hat{d}_1(t)$$

$$D_2(t) = D_{20} + \hat{d}_2(t)$$

$$V_g(t) = V_{g0} + \hat{v}_g(t)$$

$$V_c(t) = V_{c0} + \hat{v}_c(t)$$

$$\bar{i}_g(t) = I_{g0} + \hat{i}_g(t)$$

Eq. (15)

$$(D_{10} + \hat{d}_1)(V_{g0} + \hat{v}_g) + (D_{20} + \hat{d}_2)(V_{c0} + \hat{v}_c) = 0$$

$$0 = \underbrace{(D_{10} V_{g0} + D_{20} V_{c0})}_{\text{DC terms}} +$$

$$+ D_{10} \hat{v}_g + V_{g0} \hat{d}_1 + D_{20} \hat{v}_c + V_{c0} \hat{d}_2 +$$

Linear ac

$$+ \hat{d}_1 \hat{v}_g + \hat{d}_2 \hat{v}_c$$

nonlinear

Eq. (16) becomes

$$C \frac{d}{dt} (V_{c0} + \hat{v}_c) = - \frac{V_{c0} + \hat{v}_c}{R} - \frac{(D_{10} + \hat{d}_1)(D_{20} + \hat{d}_2)(V_{g0} + \hat{v}_g) T_s}{2L}$$

$$C \frac{d\hat{v}_c}{dt} = - \frac{V_{c0}}{R} - \frac{D_{10} D_{20} V_{g0} T_s}{2L} -$$

dc

$$- \frac{D_{10} D_{20} \hat{v}_g T_s}{2L} - \frac{D_{10} \hat{d}_2 V_{g0} T_s}{2L} - \frac{\hat{v}_c}{R} -$$

Linear ac

$$- \frac{\hat{d}_1 D_{20} V_{g0} T_s}{2L} - \text{nonlinear terms}$$

Linear ac

DC terms

$$0 = D_{10} V_{g0} + D_{20} V_{c0}$$

expression for  $D_{20}$

$$0 = -\frac{V_{c0}}{R} - \frac{D_{10} D_{20} V_{g0} T_s}{2L}$$

charge balance

$$I_{g0} = \frac{D_{10}^2 V_{g0} T_s}{2L}$$

input current

3 equations, 3 unknowns ( $D_{20}$ ,  $V_{c0}$ ,  $I_{g0}$ )

Solution:

$$D_{20} = \sqrt{k}$$

where  $k = \frac{2L}{RT_s}$

$$V_{c0} = -\frac{V_{g0} D_{10}}{\sqrt{k}}$$

$$I_{g0} = \frac{D_{10}^2}{k} \frac{V_{g0}}{R}$$

## Small-Signal AC Terms

$$0 = D_{10} \hat{v}_g + V_{g0} \hat{d}_1 + D_{20} \hat{v}_c + V_{c0} \hat{d}_2 \quad (\text{exp. for } \hat{d}_2)$$

$$C \frac{d\hat{v}_c}{dt} = -\frac{\hat{v}_c}{R} - \frac{T_s}{2L} (D_{10} D_{20} \hat{v}_g + D_{10} V_{g0} \hat{d}_2 + D_{20} V_{g0} \hat{d}_1)$$

(capacitor charge)

$$\hat{i}_g = \frac{D_{10}^2 T_s}{2L} \hat{v}_g + \frac{D_{10} V_{g0} T_s}{L} \hat{d}_1 =$$

$$= \frac{D_{10}^2}{Rk} \hat{v}_g + \frac{2 D_{10} V_{g0}}{Rk} \hat{d}_1 \quad (\text{input current})$$

$$\hat{d}_2 = -\frac{D_{10} \hat{v}_g + V_{g0} \hat{d}_1 + D_{20} \hat{v}_c}{V_{c0}} \quad \sim \text{given: equilibrium}$$

$\hat{d}_2 \rightarrow \text{input } \hat{d}_1 - \text{etc}$

$$C \frac{d\hat{v}_c}{dt} = -\frac{\hat{v}_c}{R} - \frac{T_s}{2L} \left( \hat{v}_g \left( D_{10} D_{20} - D_{10}^2 \frac{V_{g0}}{V_{c0}} \right) + \right.$$

$$\left. + \hat{d}_1 \left( D_{20} V_{g0} - D_{10} \frac{V_{g0}^2}{V_{c0}} \right) - \hat{v}_c D_{10} D_{20} \frac{V_{g0}}{V_{c0}} \right)$$

$$C \frac{d\hat{v}_c}{dt} = -\hat{v}_c \left( \frac{1}{R} + \frac{1}{R} \right) + \hat{v}_g \frac{2 D_{10}}{R \sqrt{k}} + \hat{d}_1 \frac{2 V_{g0}}{R \sqrt{k}}$$


↑  
output current  
daves

# Equivalent circuit model

## Output relation

$$C \frac{d\hat{v}_c}{dt} = -\hat{v}_c \left( \frac{1}{R} + \frac{1}{R} \right) + \hat{v}_g \frac{2D_{n0}}{2\sqrt{K}} + \hat{d}_1 \frac{2V_{g0}}{2\sqrt{K}}$$

a node equation

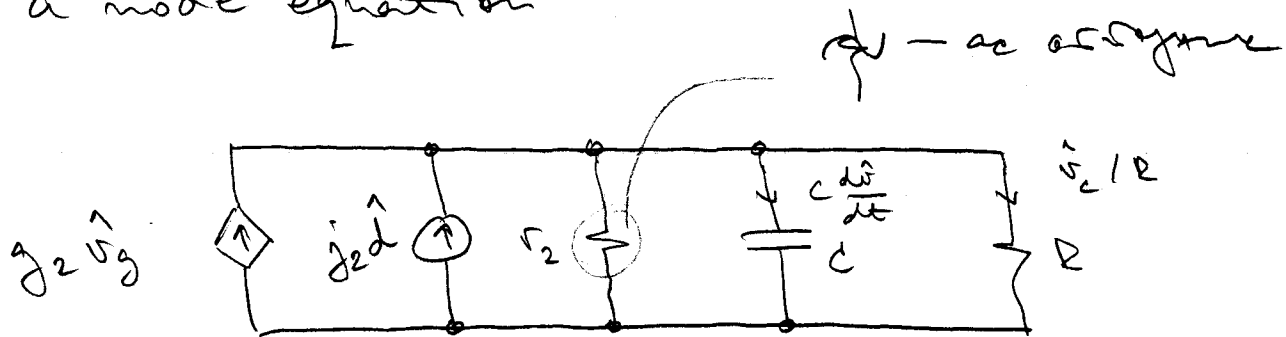


$$g_2 = \frac{2D_{n0}}{2\sqrt{K}}, \quad j_2 = \frac{2V_{g0}}{2\sqrt{K}}, \quad v_2 = R$$

↑  
 dir v<sub>2</sub> = max  
 ac equivalent
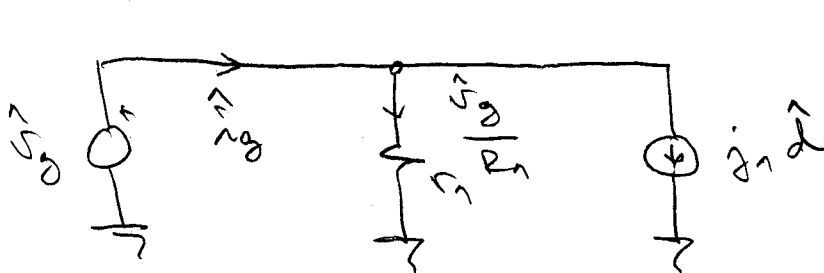
## Input relation

$$\hat{v}_g = \frac{D_{n0}}{R\sqrt{K}} \hat{v}_g + \frac{2D_{n0}V_{g0}}{2\sqrt{K}} \hat{d}_1$$



$$r_1 = R \frac{K}{D_{n0}^2}$$

$$j_1 = \frac{V_{g0}}{R} \frac{2D_{n0}}{K}$$


↑  
 after ac  
 resistor



$r_1$  &  $r_2$  are effective ac resistances only;

they do not enter into the dc model, nor they represent power loss

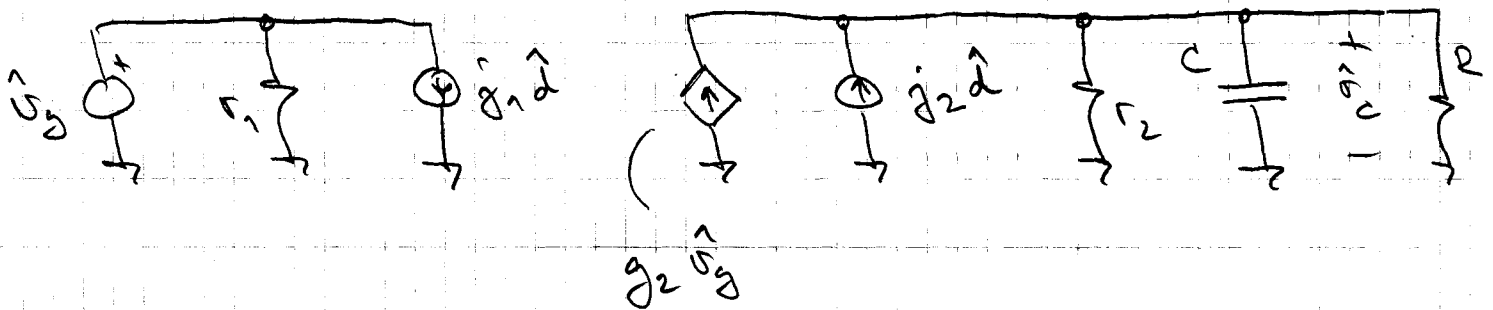Complete ac small-signal model for buck-boost in discontinuous mode



$r_1$  &  $r_2$  are ac resistors

## Summary of the Analysis Technique

- 1 Must determine  $v(T_s)$  in terms of  $v(0)$ , then approximate  $\frac{dv}{dt} = \frac{v(T_s) - v(0)}{T_s}$
- 2 Cannot approximate  $i(t)$  as nearly constant, since inductor current ripple is not small. Instead, use average value of  $i$ .
- 3 An additional equation is needed to determine the length of the second interval  $D_2 T_s$ : The second interval ends when  $i((D_1 + D_2) T_s) = 0$ .

Result: Nonlinear diff. Eq. which describe  $\frac{dv}{dt}$ . No equation for  $\frac{di}{dt}$ , since  $i(T_s) = i(0) = 0 \rightarrow \frac{di}{dt} = 0$ , and the inductor does not contribute a pole to the converter dynamics.

- One can construct small-signal ac model by perturbation and linearization, as usual

# Canonical Circuit Model - DCM




Converter	$r_1$	$g_1$	$g_2$	$g_2$	$g_2$	$r_2$
buck	$\frac{1-M}{M^2} R$	$\frac{2V_o}{R} \sqrt{\frac{1-M^2}{K}}$	$\frac{M^2}{1-M} \frac{1}{R}$	$\frac{M(2-M)}{(1-M)R}$	$\frac{2V_o}{2M} \sqrt{\frac{1-M}{K}}$	$(1-M)R$
boost	$\frac{M-1}{M^2} R$	$\frac{2V_o}{R} \sqrt{\frac{M}{K(M-1)}}$	$\frac{M}{M-1} \frac{1}{R}$	$\frac{M(2M-1)}{(M-1)R}$	$\frac{2V_o}{R \sqrt{KM(M-1)}}$	$\frac{M-1}{M} R$
buck-boost	$\frac{R}{M^2}$	$\frac{2 V_o }{R \sqrt{K}}$	0	$\frac{2M}{R}$	$\frac{2 V_o }{R \sqrt{KM}}$	R

$$M = \frac{V_o}{V_g} = \begin{cases} \frac{2}{1 + \sqrt{1 + 4K/D^2}} & \text{buck} \\ \frac{1 + \sqrt{1 + 4D^2/K}}{2} & \text{boost} \\ -\frac{D}{\sqrt{K}} & \text{buck-boost} \end{cases}$$

Small-signal transfer functions are easily found from the model:

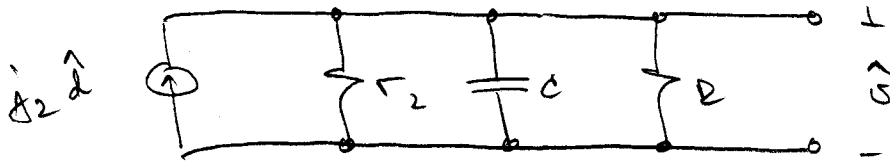
a)  $\frac{\hat{v}_o}{\hat{d}}$  :  $\hat{v}_g = 0$



$$\hat{v}_o = \hat{d} g_2 \left( r_2 \parallel \frac{1}{sC} \parallel R \right)$$

$$\frac{\hat{v}_o}{\hat{d}} = G_{do} \frac{1}{1 + \frac{s}{\omega_p}} \quad \text{— can be repeated for } a$$

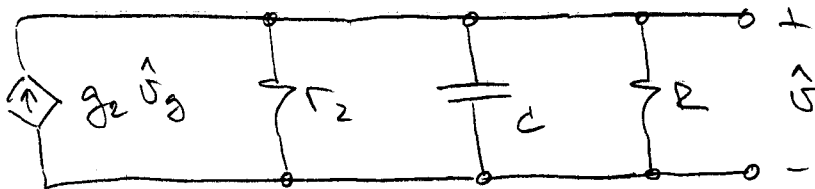b)  $\frac{\hat{v}_o}{\hat{v}_g}$  : set  $\hat{d} = 0$



$$\hat{v}_o = g_2 \hat{v}_g \left( r_2 \parallel \frac{1}{sC} \parallel R \right)$$

$$\frac{\hat{v}_o}{\hat{v}_g} = \frac{G_{go}}{1 + \frac{s}{\omega_p}}$$

$$b) \text{ Zeit: } \frac{G_2}{g} = 0, \quad \vec{a} = 0$$

$$\text{Zeit} = r_2 \parallel \frac{1}{g} \parallel R$$