
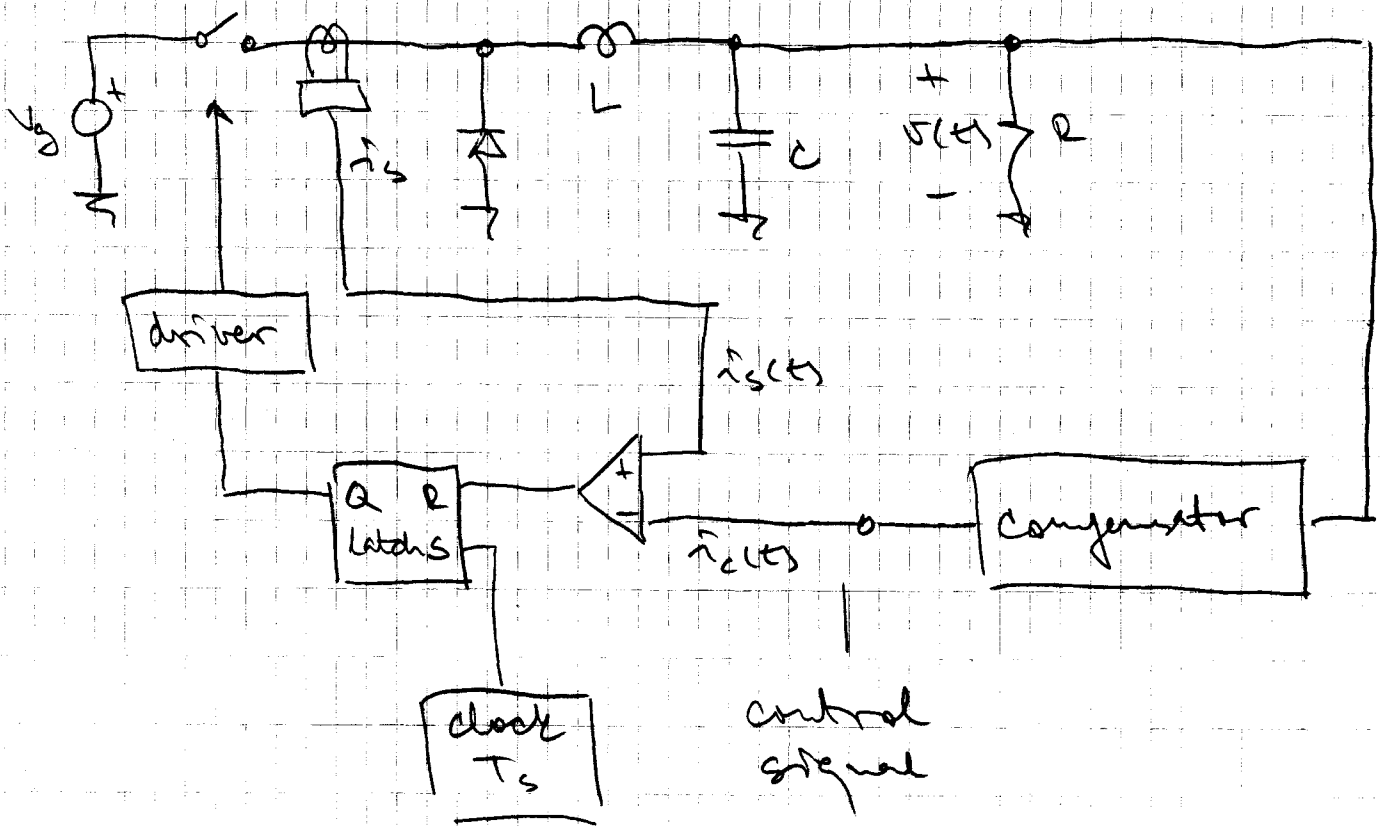


Maxwell Chopper, vai π faza mpyasa

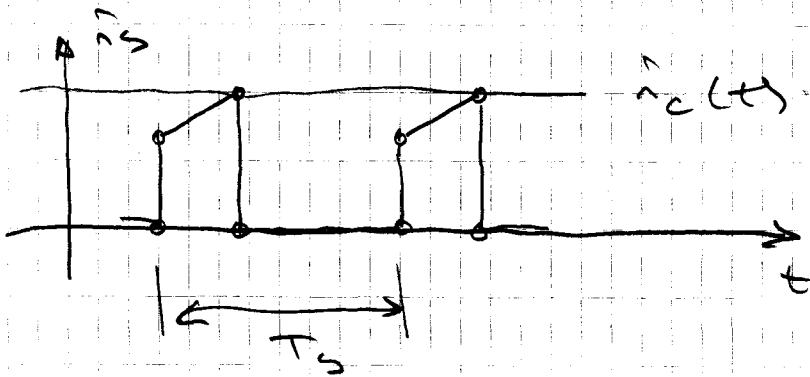- go caga - duty ratio programmed mode
 $v(t)$ is constant as $D(t)$
- y raga here (10 degree) "current-programmed" mode, uzras is constant usdofon mpyasa frequency caga is microscope (peak transistor current), peak ($i_s(t) \approx i_c(t)$)
- π faza: buck converter



- qle acilise feruogrije, navaana, je pericubna
- Dcty nje gupetno konyomcano
- kano jay konyogoy



Definicion / nase sekure equipt gupemjane


- 1° dynamics is potentially simpler
 $\frac{\hat{i}_s}{\hat{i}_c}$ nra jear na nava ay $\frac{\hat{i}_s}{\hat{i}_c}$.
 Peana nava n gupit nra, am na
 nra nra gupit nra ay PWM nra
- 2° Definicija nra nra nra nra nra
 nra, nra nra nra nra nra
- 3° Nra nra nra nra, nra nra nra
 nra, nra nra nra nra nra
 n closed loop.

4. Log push-pull-a u log full-bridge-a
 Hava fjadurena ca zactehen perife

Naime:

1. Za steady-state $D > 0.5$ fjadurana
 medu τ i τ_{max} . Osvetava se gaganom
 "artificial ramp" to τ_s . Buta alpiners

Usoznica periferia:

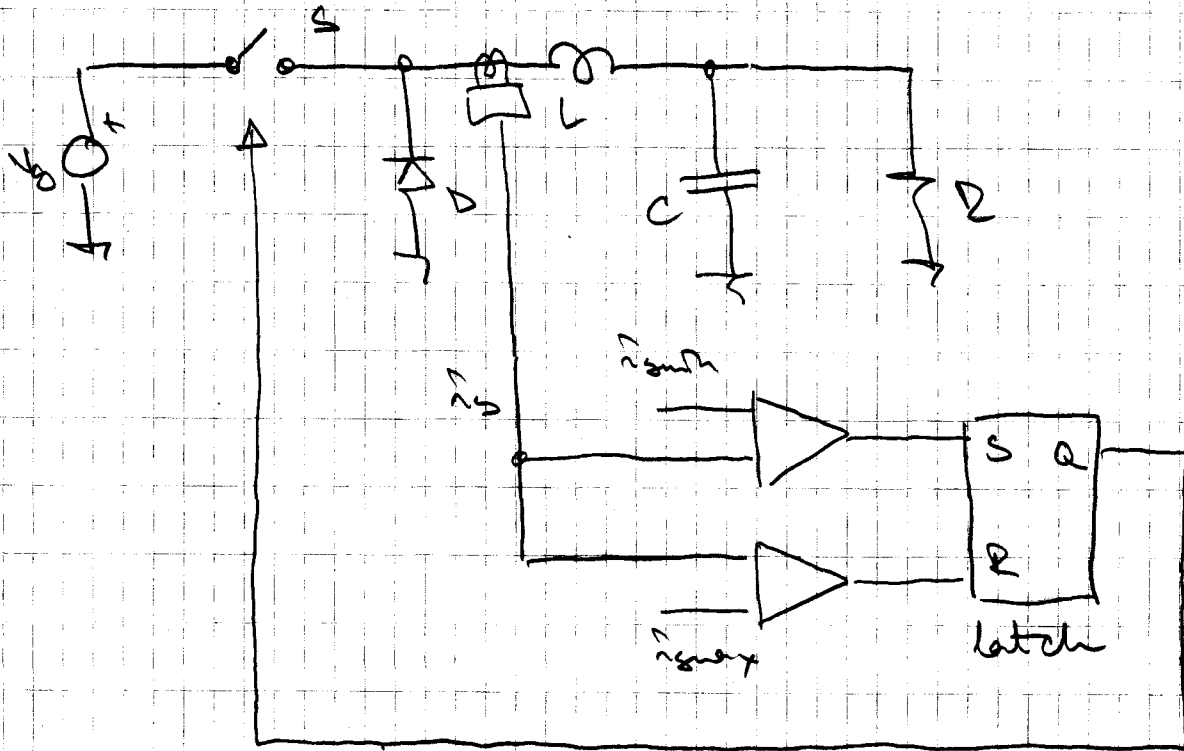


- Hava fjadurena saduzhen
- f_s i τ kactehen
- kommutatsiya
- Hava se saduzhen u se kactehen
- kommutatsiya vega kactehen τ_c

$$\begin{aligned} \tau_c + \tau_f &= \tau_{max} \\ \tau_c - \tau_r &= \tau_{rise} \end{aligned} \quad \text{③}$$

→ Hava se kactehen!

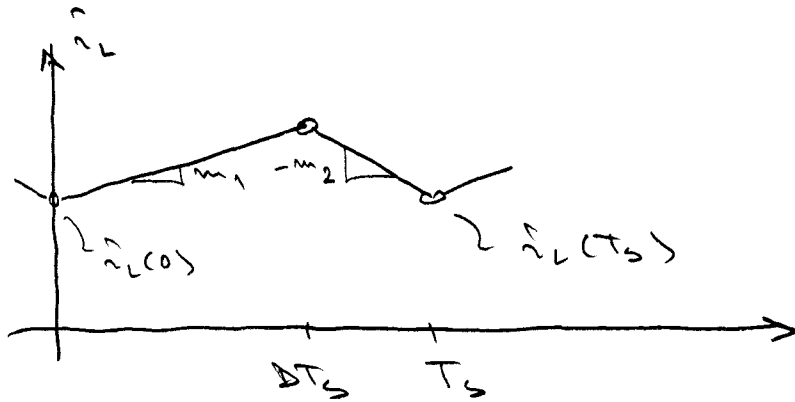Discrete-Time Analysis of Basic Current-Mode Converter



$$m_1 = \frac{d\hat{i}_L}{dt} \quad ; \quad \text{1st interval}$$

$$-m_2 = \frac{d\hat{i}_L}{dt} \quad ; \quad \text{2nd interval}$$

	m_1	m_2
buck	$\frac{V_g - V}{L}$	V/L
boost	V_g/L	$(V - V_g)/L$
buck-boost	V_g/L	$-V/L$

$$\hat{i}_L(DT_s) = \hat{i}_c = \hat{i}_L(0) + m_1 DT_s$$

$$D = \frac{\hat{i}_c - \hat{i}_L(0)}{m_1 T_s}$$

2nd interval

$$\begin{aligned}\hat{r}_L(T_s) &= \hat{r}_L(DT_s) - D'T_s m_2 = \\ &= \hat{r}_L(0) + m_1 DT_s - m_2 D'T_s\end{aligned}\quad (**)$$

steady-state

$$\hat{r}_L(0) = \hat{r}_L(T_s)$$

$$0 = m_1 D - m_2 D' \quad (***)$$



Consider small perturbation in $\hat{r}_L(0)$:

$$\hat{r}_L(0) = I_{L0} + \hat{\hat{r}}_L(0)$$

I_{L0} is steady-state $\hat{r}_L(0)$ kuzi zapochavala
poglyamuy (**)

Pri srazhchenii $|\hat{\hat{r}}_L(0)| \ll |I_{L0}|$, kotory ya klyuch
ya m ca n pozhe nam shaga
|~~nechislennost~~ | |~~chislennost~~ |

Zatem na me $\hat{\hat{r}}_L(nT_s)$

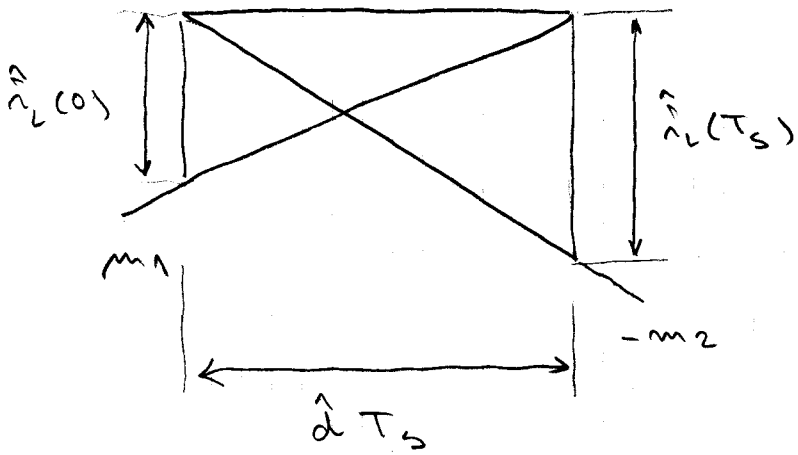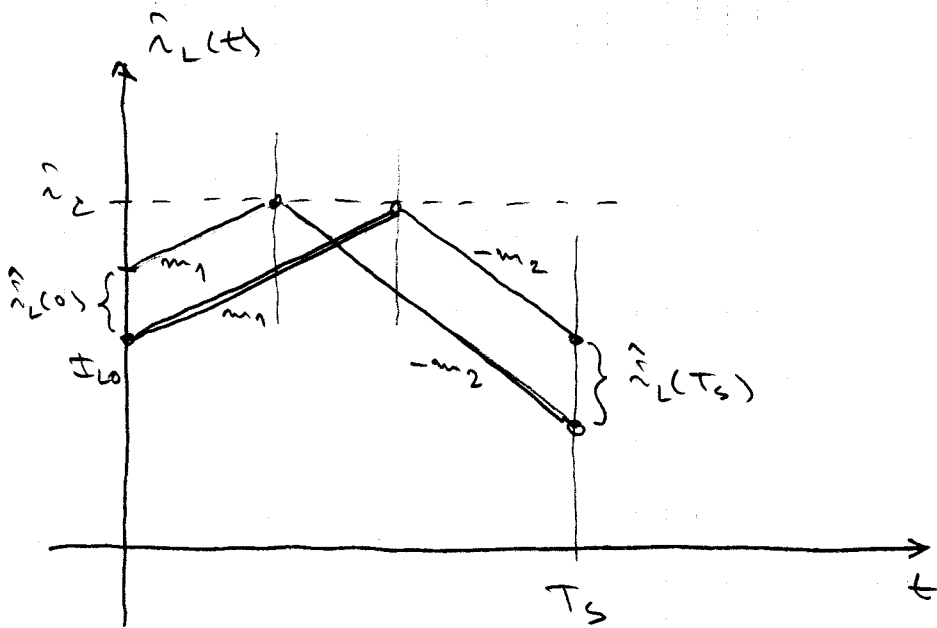

$$\hat{d} < 0$$

$$\hat{r}_L(0) > 0$$

$$\hat{r}_L(T_s) < 0$$

$$-\hat{r}_L(0) = m_1 \hat{d} T_s$$

$$-\hat{r}_L(T_s) = -m_2 \hat{d} T_s$$

eliminate $\hat{d} T_s$

$$-\frac{\hat{r}_L(0)}{m_1} = \frac{\hat{r}_L(T_s)}{m_2}$$

$$\hat{z}_L(T_S) = \hat{z}_L(0) \left(-\frac{m_2}{m_1} \right)$$

$$\frac{m_2}{m_1} = \frac{D}{D'}$$

(**)

$$\hat{z}_L(T_S) = \hat{z}_L(0) \left(-\frac{D}{D'} \right)$$

$$\hat{z}_L(nT_S) = \hat{z}_L(0) \left(-\frac{D}{D'} \right)^n$$

da $0 < D < 1$

$$\frac{D}{D'} < 1$$

$$\frac{D}{1-D} < 1$$

$$D < 1-D$$

$$2D < 1$$

$$D < \frac{1}{2}$$

- $0 < D < 1$

- Die Differenz $n \cdot T_S$ sollte klein sein

Example Operation of boost converter with

$$V_g = 20, V = 50$$

note $\frac{V}{V_g} = \frac{1}{D'} \Rightarrow D' = \frac{2}{5} \Rightarrow D = \frac{3}{5} > \frac{1}{2}$

so the current programmed mode should be unstable.

$$\left(-\frac{D}{D'}\right) = \left(-\frac{3/5}{2/5}\right) = -1.5$$

$$\underline{n} \quad \underline{\hat{i}(nT_s) = \hat{i}(0) \left(-\frac{D}{D'}\right)^n}$$

0	$\hat{i}(0)$
1	$-1.5 \hat{i}(0)$
2	$+2.25 \hat{i}(0)$
3	$-3.375 \hat{i}(0)$

etc.

-growing oscillation

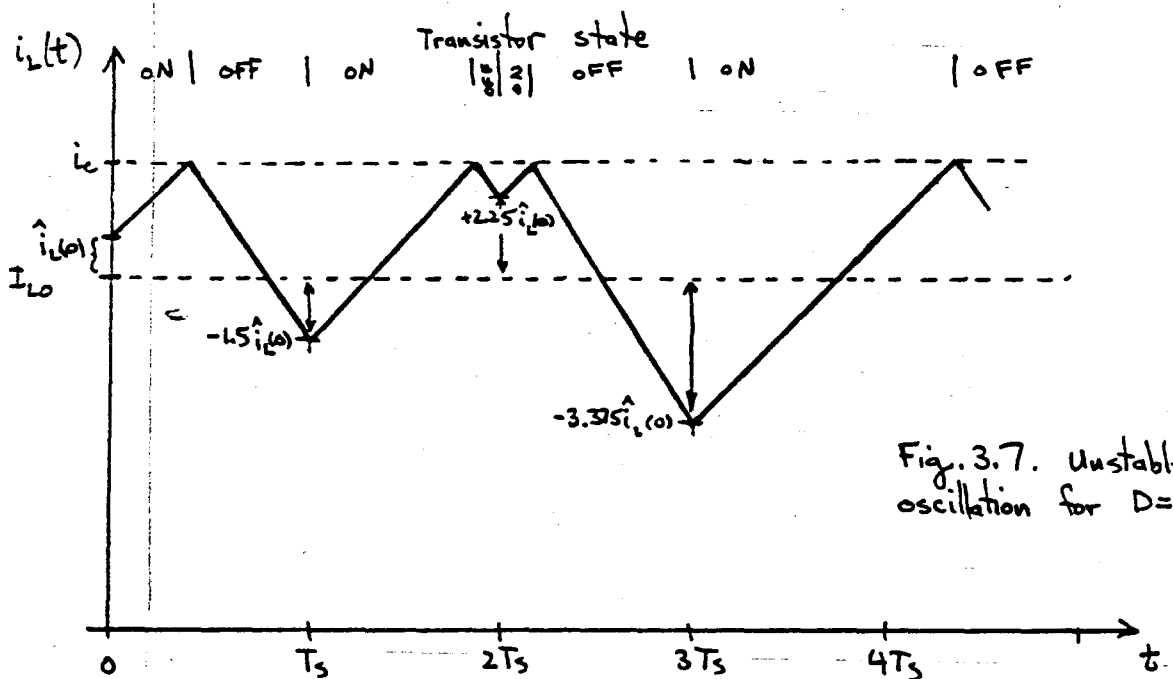


Fig. 3.7. Unstable oscillation for $D=0.6$

It can be seen from Fig. 3.7 that the oscillations grow in amplitude, and the current-mode controller does not operate correctly. However, once the oscillations become large, they no longer grow without bound. Instead, the inherent nonlinearity (saturation) of the system limits the maximum amplitude of the oscillations.

For $V_g = 20$, $V = 30$:


$$\text{then } D = \frac{1}{3}, \quad -\frac{D}{D'} = -\frac{1}{2}$$

$$\hat{i}(nT_s) = \hat{i}(0) \left(-\frac{D}{D'}\right)^n$$

n	$\hat{i}(nT_s)$
0	$\hat{i}(0)$
1	$-\frac{1}{2} \hat{i}(0)$
2	$\frac{1}{4} \hat{i}(0)$
3	$-\frac{1}{8} \hat{i}(0)$

etc.


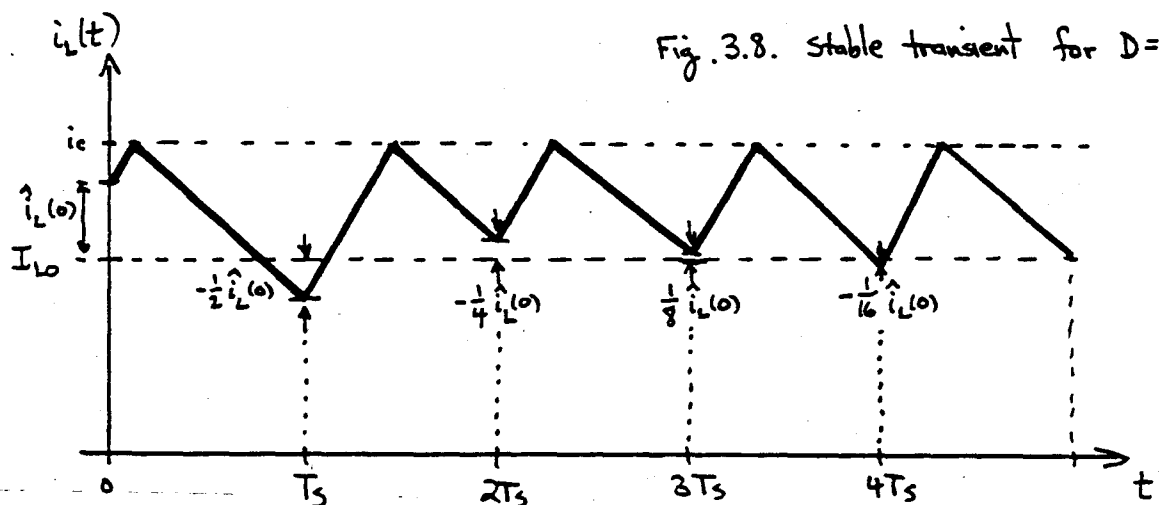
disturbance becomes small after a few intervals



The condition is $D > \frac{1}{2}$ the value of converter topology.

Artificial Ramp

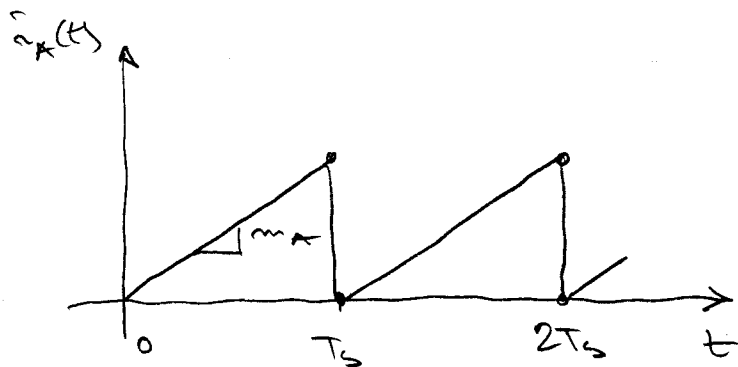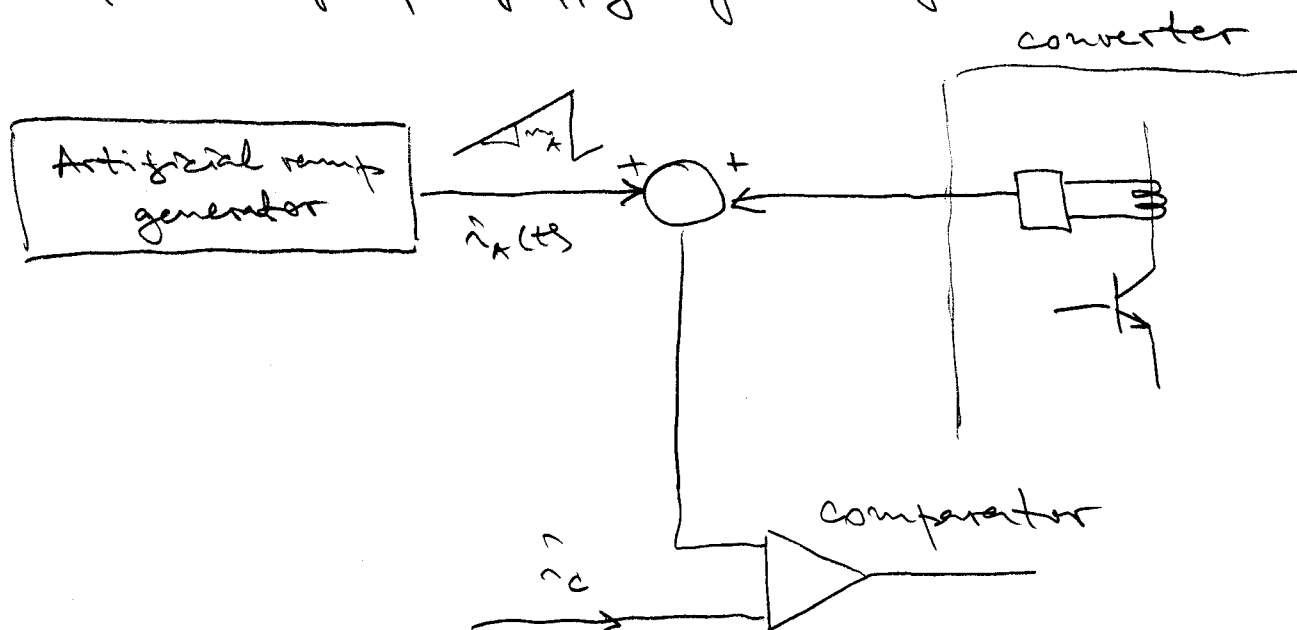Commonly-used solution, require an artificial ramp for reference current injection.




определить ее нач. value

$$\hat{i}_A(t) + \hat{i}_L(t) = \hat{i}_C$$

определим

$$\hat{i}_L(t) = \hat{i}_C - \hat{i}_A(t)$$

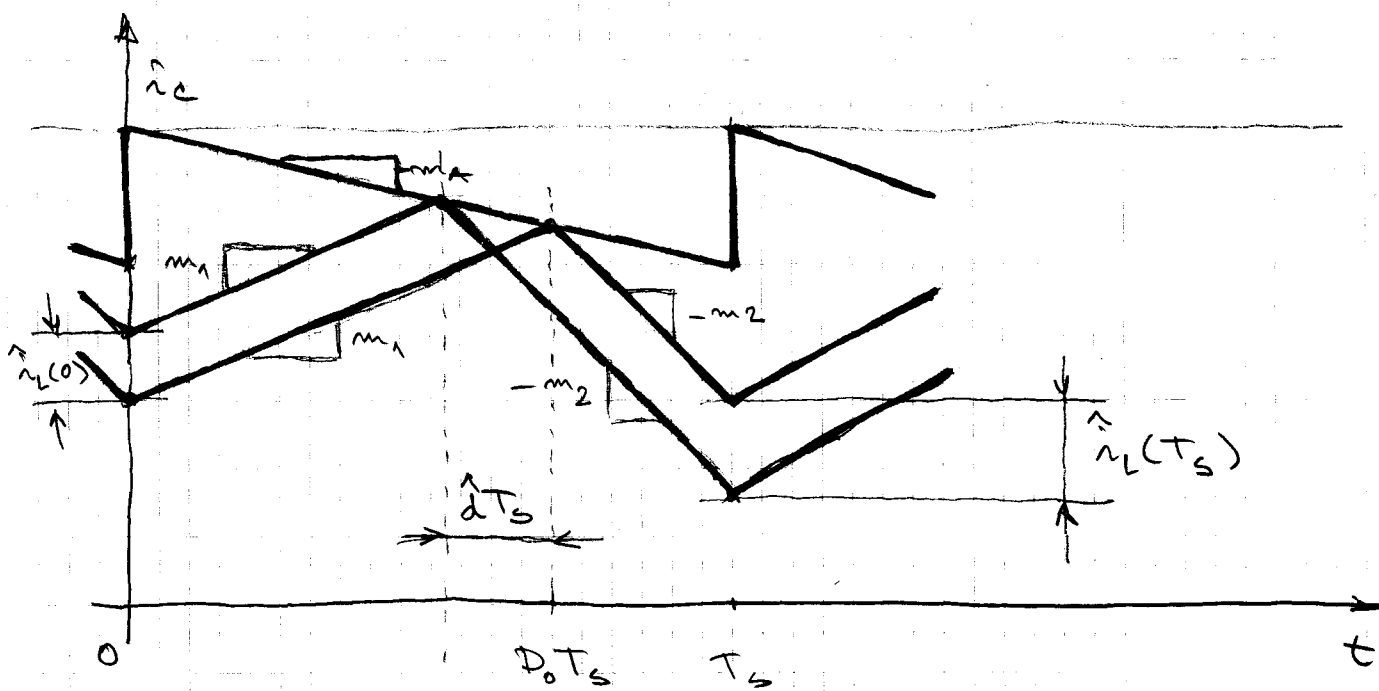
→ нач. value $\hat{i}_L(0)$ и определены value $\hat{i}_L(T_s)$ и $\hat{i}_L(t)$ в промежутке $0 < t < T_s$



$$-\hat{i}_L(0) = \hat{d} T_s m_1 - \hat{d} T_s (-m_A) = \\ = \hat{d} T_s (m_1 + m_A)$$

$$-\hat{i}_L(T_s) = -m_2 \hat{d} T_s - \hat{d} T_s (-m_A) = \\ = \hat{d} T_s (m_A - m_2)$$

важно! →

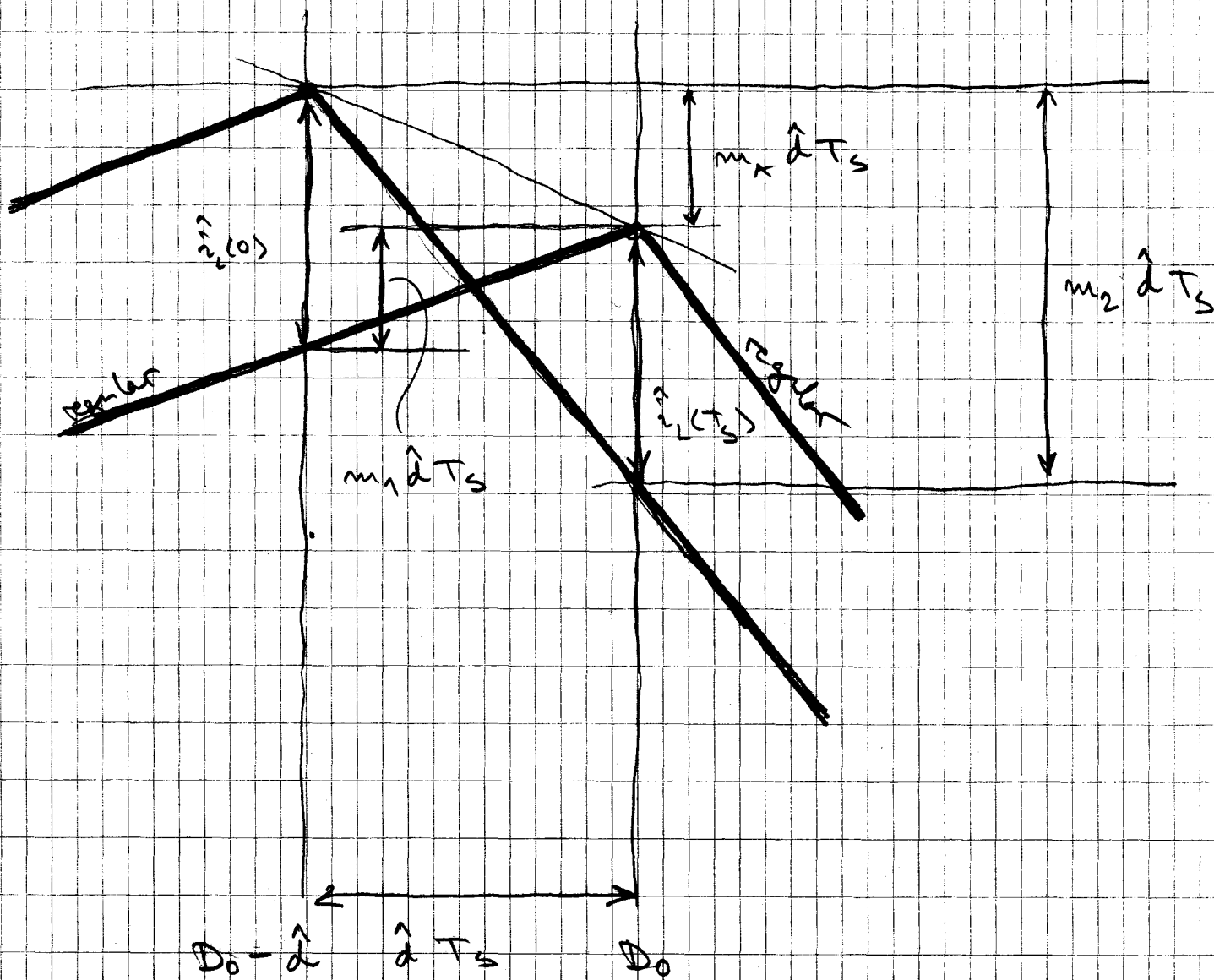

$$\hat{z}_L(0) = m_A \hat{dT}_S + m_1 \hat{dT}_S = (m_A + m_1) \hat{dT}_S$$

$$\hat{z}_L(T_S) = -m_2 \hat{dT}_S + m_A \hat{dT}_S = (m_A - m_2) \hat{dT}_S$$

$$\frac{\hat{z}_L(T_S)}{\hat{z}_L(0)} = \frac{m_A - m_2}{m_A + m_1}$$

$$\frac{\vec{r}_L(T_S)}{\vec{r}_L(0)} = \left(-\frac{m_2 - m_A}{m_1 + m_A} \right)$$

$$\vec{r}_L(nT_S) = \left(-\frac{m_2 - m_A}{m_1 + m_A} \right)^n \vec{r}_L(0)$$

$m_A = 0$ - абсолютно жесткая связь

$$\begin{array}{l} \vec{r}_L \rightarrow \infty \\ \vec{r}_L \rightarrow 0 \end{array} \quad \begin{array}{l} \uparrow \\ \downarrow \end{array} \quad \left| \frac{m_2 - m_A}{m_1 + m_A} \right| \begin{array}{l} > 1 \\ < 1 \end{array}$$

знак: $-\frac{m_2 - m_A}{m_1 + m_A} \quad (m_A)$


связь

$$D_0 > \frac{1}{2} \quad m_2 > m_1$$

$$D_0 < \frac{1}{2} \quad m_1 > m_2$$

$$D_0 > \frac{1}{2}$$

$$m_2 > m_1$$

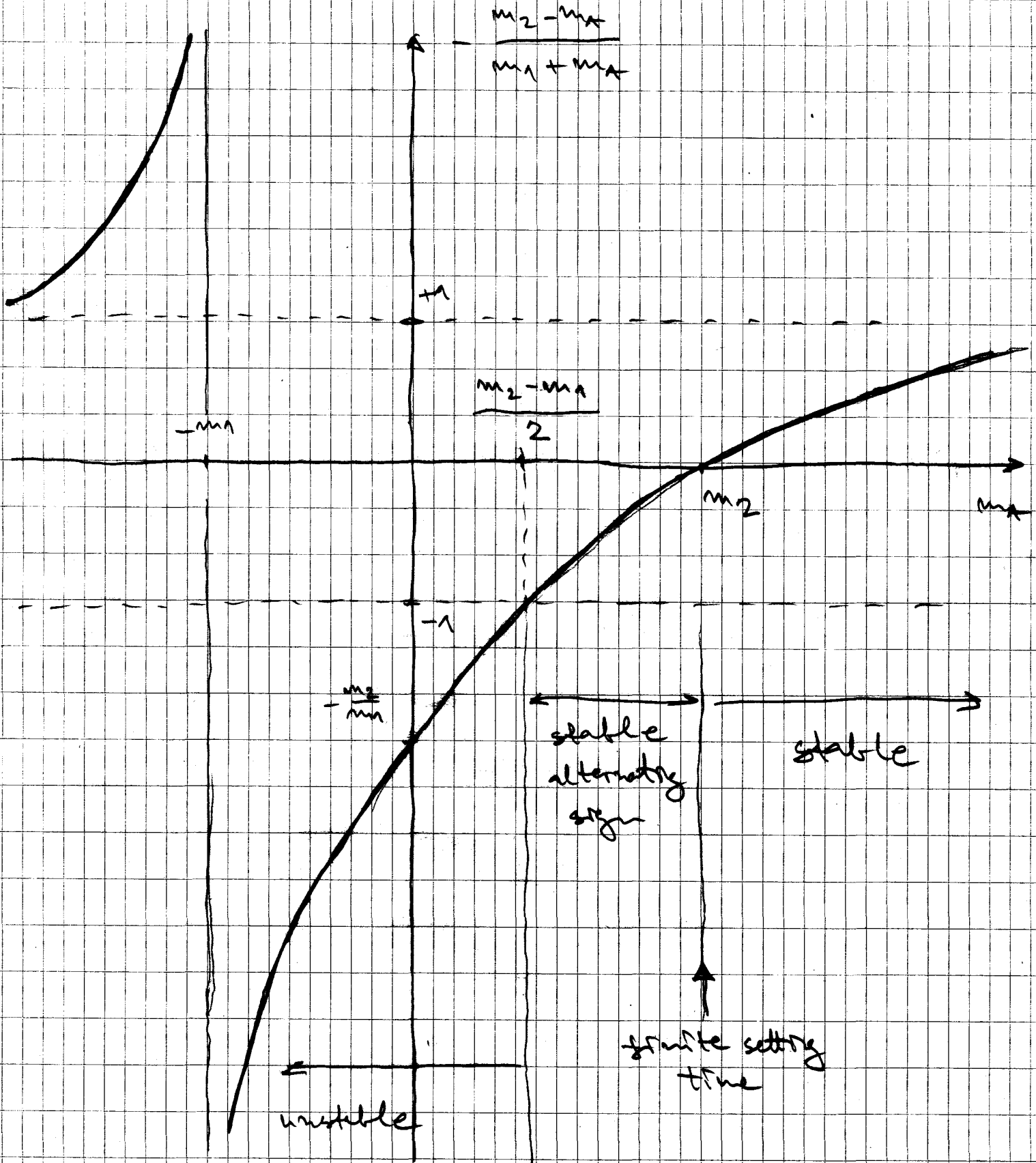

$$m_A > m_2 \quad - \text{stable}$$


$$\frac{m_2 - m_1}{2} < m_A < m_2 \quad - \text{stable, alternating sign}$$

$$m_A < \frac{m_2 - m_1}{2} \quad - \text{unstable}$$

more like m_A no phase \rightarrow more like ω
 \rightarrow ω , no \rightarrow phase

$$m_A = m_2 \quad - \text{finite settling time}$$

$D_0 < \frac{1}{2}$, $m_2 < m_1$

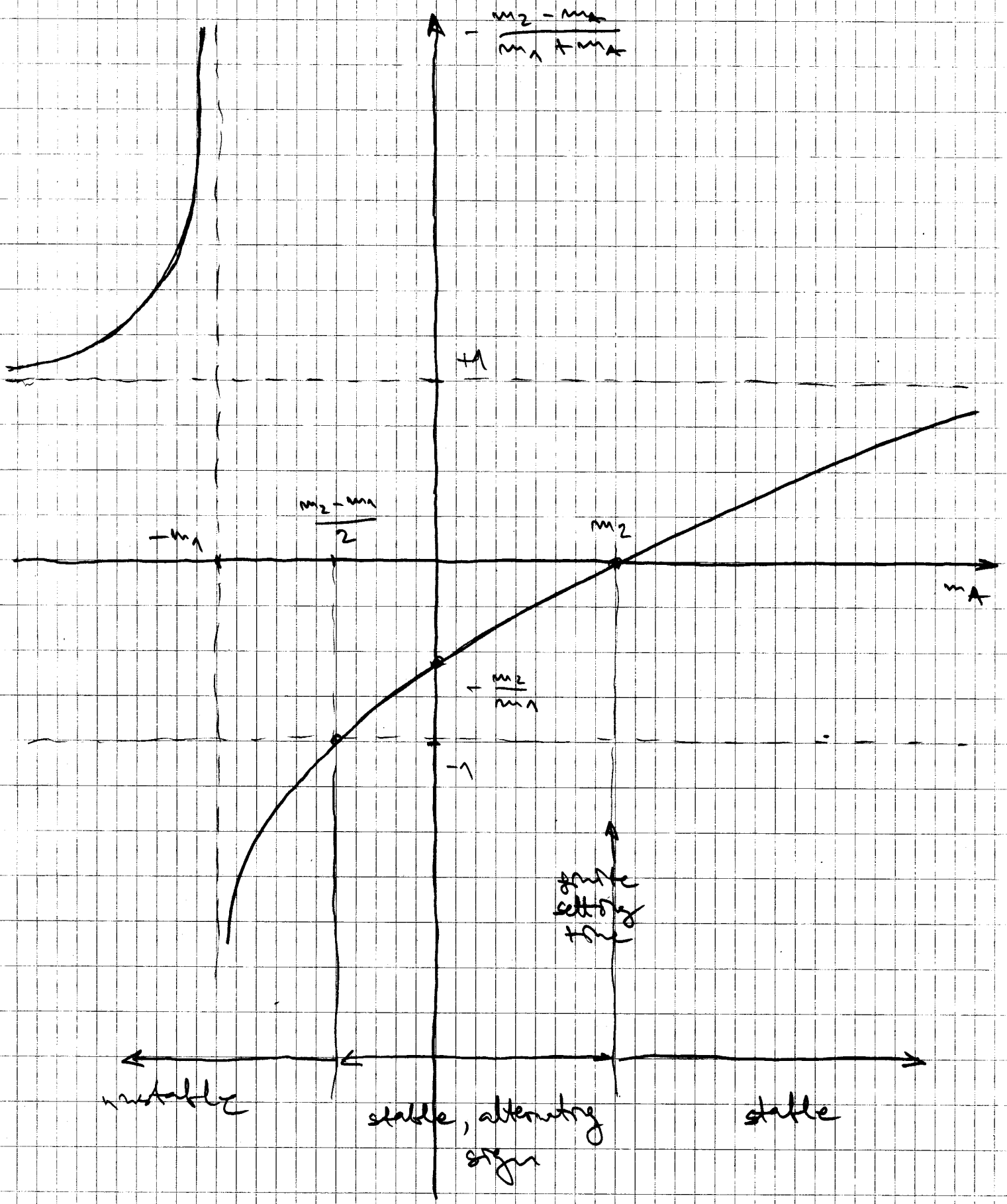

$$m_A > m_2 \quad - \text{stable}$$

$$m_2 > m_A > \frac{m_2 - m_1}{2} \quad - \text{stable, alternating sign}$$

$$m_A = m_2 \quad - \text{finite setting time}$$

$$m_A < \frac{m_2 - m_1}{2} \quad - \text{unstable}$$


finite setting time?

m_2 ce masa ca Do, m_1 ce
sistemul raspunde. He make


ce sistemul finite setting time lag
raspunde foarte repede

Permanently adjustable voltage source with current regulation

- dynamic behavior permanently

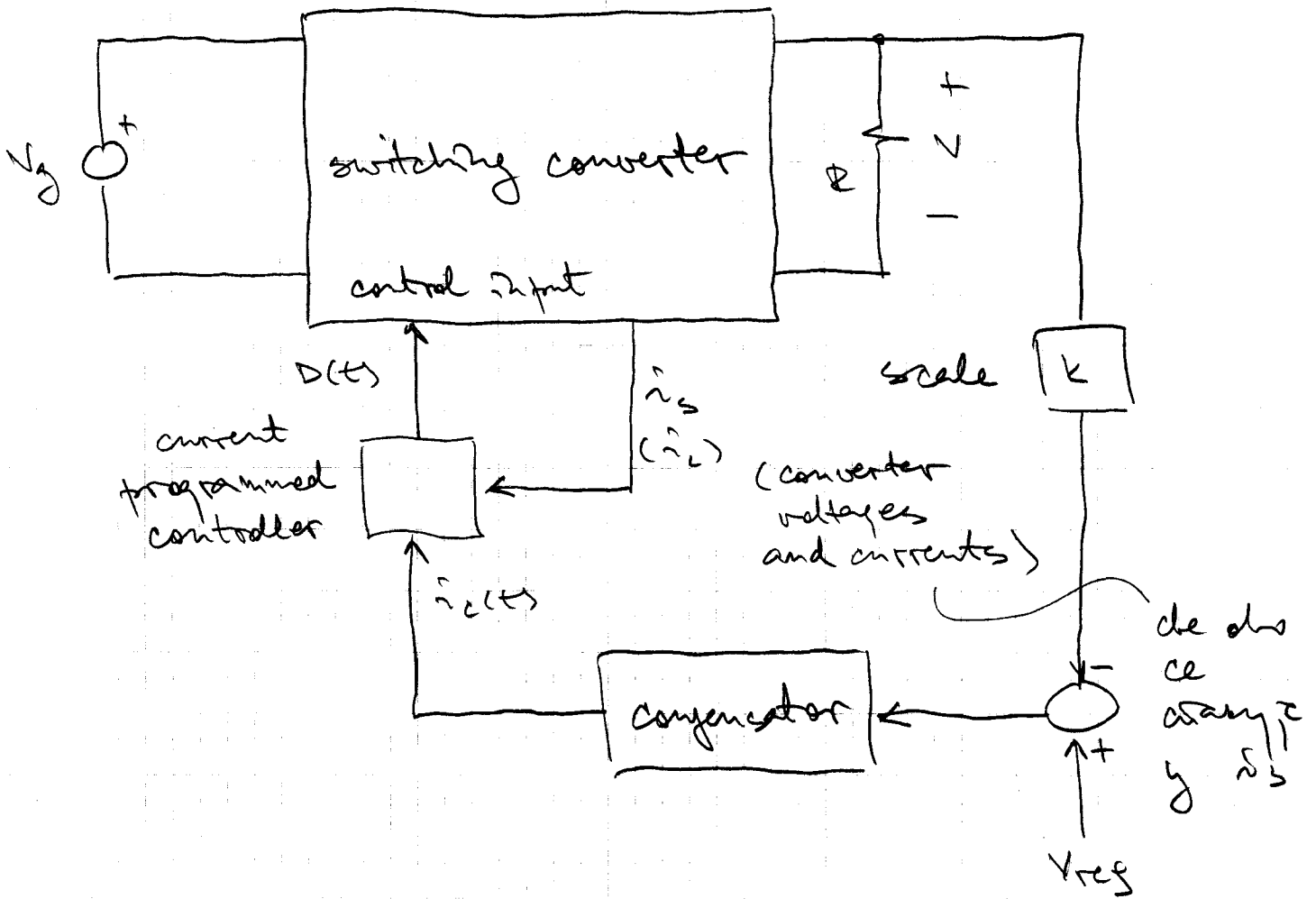


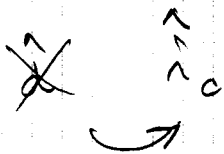
- equivalent circuit, small signal model,



$i_L \approx i_C$ - do general for - q_{ij} as

- ~~peanut~~ ~~diagram~~ ~~for~~ ~~a~~ ~~known~~ ~~resistor~~ ~~value~~
- ~~other~~ state-space averaging

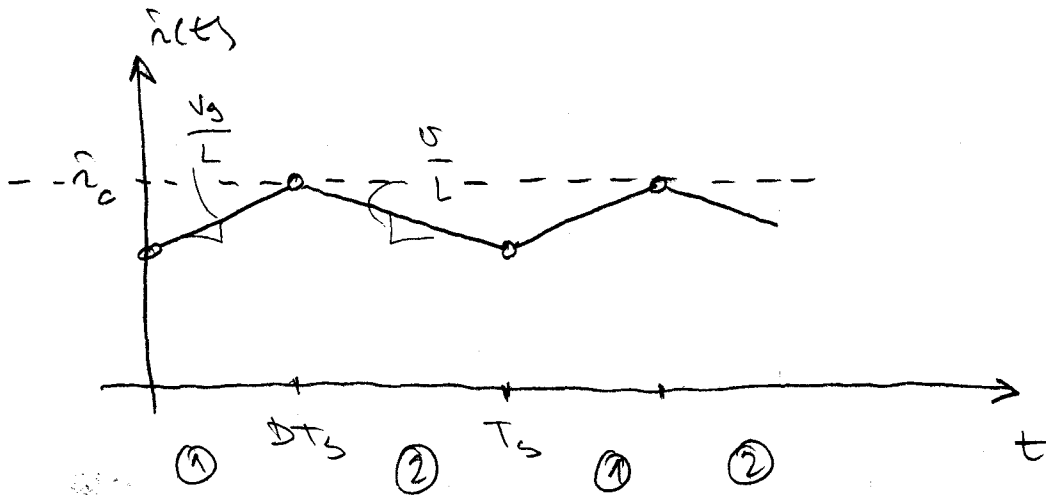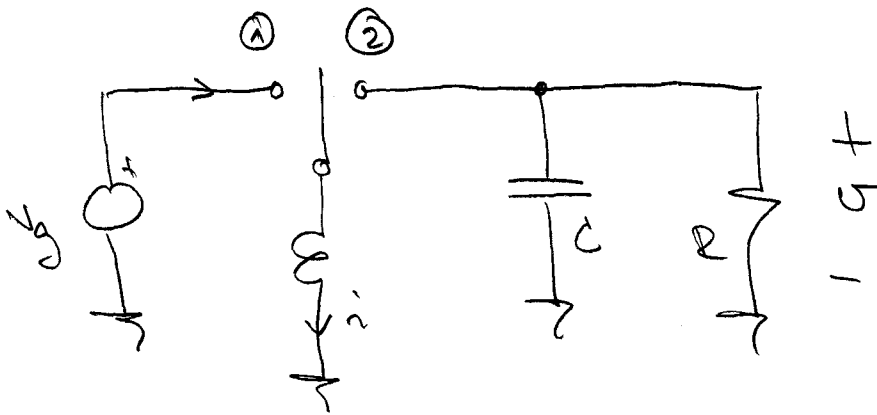Simplified Equivalent Circuit Modelling,
Buck-Boost Example



state-space Equations

$$L \frac{d\hat{i}}{dt} = D_0' \hat{v} + D_0 \hat{v}_g + (V_g - V_0) \hat{d}$$

$$C \frac{d\hat{v}}{dt} = -D_0' \hat{i} - \frac{\hat{v}}{R} + I_0 \hat{d}$$

$$\hat{i}_g = D_0 \hat{i} + I_0 \hat{d}$$

Analysis

$$sL \hat{i}(s) = D_0' \hat{v}(s) + D_0 \hat{v}_g(s) + (V_g - V_0) \hat{d}(s)$$

$$sC \hat{v}(s) = -D_0' \hat{i}(s) - \frac{\hat{v}(s)}{R} + I_0 \hat{d}(s)$$

$$\hat{i}_g(s) = D_0 \hat{i}(s) + I_0 \hat{d}(s)$$

converter is stable, ripple is small,
artificial ramp is not too large

$$\hat{i}_c(s) \approx \hat{i}(s)$$

$$sL \hat{i}_c(s) \approx D_0' \hat{v}(s) + D_0 \hat{v}_g(s) + (V_g - V_0) \hat{d}(s)$$

$$\hat{d} = \frac{sL \hat{i}_c(s) - D_0' \hat{v}(s) - D_0 \hat{v}_g(s)}{V_g - V_0}$$

- given: electromagnetic $\hat{d}(s)$ and remember ca $\hat{z}_c(s)$

$$sL \hat{v}(s) = -D_0' \hat{z}_c(s) - \frac{\hat{v}(s)}{R} + I_0 \frac{sL \hat{z}_c(s) - D_0' \hat{v}(s) - D_0 \hat{v}_g(s)}{V_g - V_0}$$

$$\hat{z}_g(s) = D_0 \hat{z}_c(s) + I_0 \frac{sL \hat{z}_c(s) - D_0' \hat{v}(s) - D_0 \hat{v}_g(s)}{V_g - V_0}$$

- combine in frequency domain

$$sL \hat{v}(s) = \left(\frac{sL I_0}{V_g - V_0} - D_0' \right) \hat{z}_c(s) - \left(\frac{D_0' I_0}{V_g - V_0} + \frac{1}{R} \right) \hat{v}(s) - \left(\frac{D_0 I_0}{V_g - V_0} \right) \hat{v}_g(s)$$

$$\hat{z}_g(s) = \left(D_0 + \frac{sL I_0}{V_g - V_0} \right) \hat{z}_c(s) - \left(\frac{D_0' I_0}{V_g - V_0} \right) \hat{v} - \left(\frac{D_0 I_0}{V_g - V_0} \right) \hat{v}_g(s)$$

frequency steady-state equations

$$V_0 = -\frac{D_0}{D_0'} V_g ; I_0 = -\frac{V_0}{D_0' R} = \frac{D_0 V_g}{D_0'^2 R}$$

$$\frac{I_0}{V_g - V_0} = \frac{D_0 N_g}{D_0'^2 R (V_g + \frac{D_0}{D_0'} V_g)} = \frac{D_0}{D_0' R}$$


на 1e:

$$sC \vec{U} = \left(\frac{sL D_0}{D_0' R} - D_0' \right) \vec{z}_c - \left(\frac{D_0}{R} + \frac{1}{R} \right) \vec{U} - \left(\frac{D_0^2}{D_0' R} \right) \vec{U}_g$$


$$\vec{z}_g = \left(\frac{sL D_0}{R D_0'} + D_0' \right) \vec{z}_c - \left(\frac{D_0}{R} \right) \vec{U} - \left(\frac{D_0^2}{D_0' R} \right) \vec{U}_g$$

↑ это не активная нагрузка, а эквив. конт. внос


- нагрузка не имеет емкости

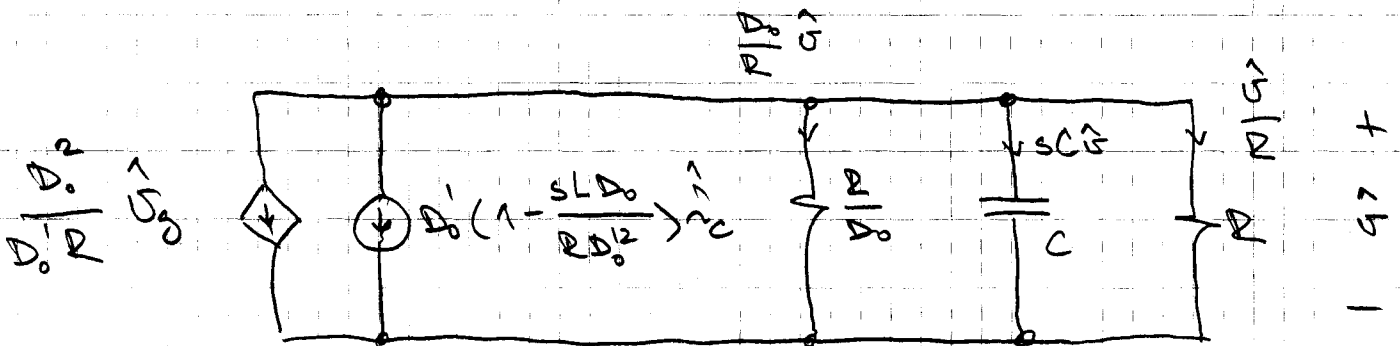

- One input current equation:

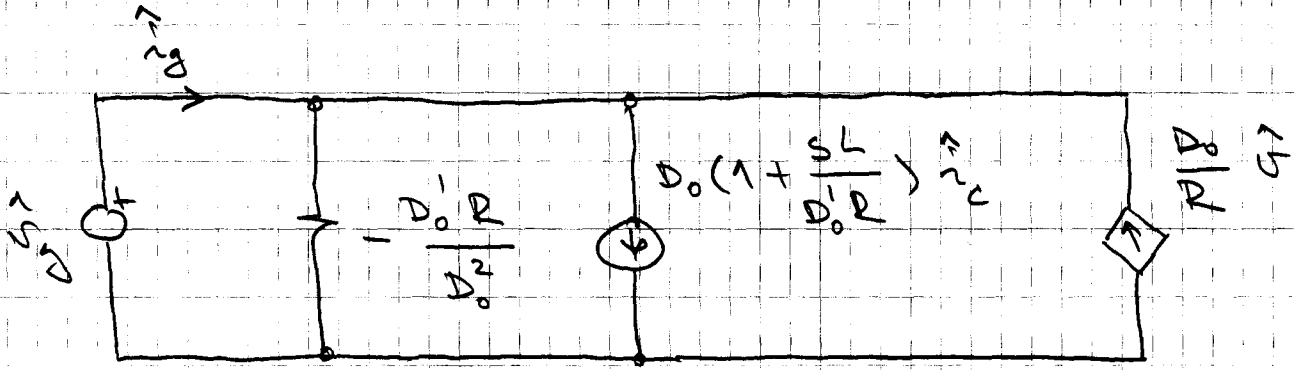

Частотен:

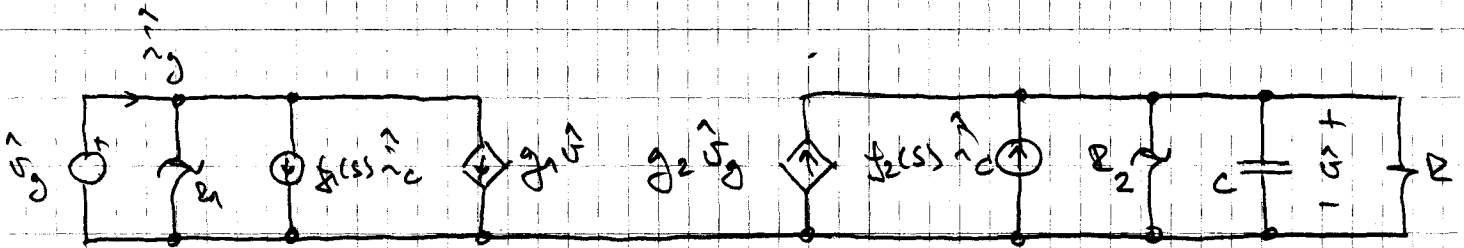

$$R_1 = -\frac{D_0'}{D_0} R, \quad f_1(s) = D_0 \left(1 + s \frac{L}{D_0' R} \right), \quad g_1 = -\frac{P}{D_0}$$

$$R_2 = \frac{R}{D_0}, \quad f_2(s) = -D_0' \left(1 - s \frac{D_0 L}{D_0^2 R} \right), \quad g_2 = -\frac{D_0^2}{D_0' R}$$

НЗ дрот ева се бае јероче претупит, исказа
уштејакса, ...

Transfer: Control to output transfer function

$$\frac{\hat{u}_c}{\hat{u}_g} = f_2 R_2 \parallel R \parallel \frac{1}{sC} \quad (\hat{u}_g = 0)$$

$$\frac{\hat{u}_c}{\hat{u}_g} = -R \frac{1-D_0}{1+D_0} \frac{1-s \frac{D_0 h}{D_0^2 R}}{1+s \frac{RC}{1+D_0}}$$

line-to-output transfer function

$$\frac{\hat{u}_g}{\hat{u}_g} = g_2 R_2 \parallel R \parallel \frac{1}{sC} \quad (\hat{u}_c = 0)$$

$$\frac{\hat{u}_g}{\hat{u}_g} = -\frac{D_0^2}{1-D_0^2} \frac{1}{1+s \frac{RC}{1+D_0}}$$

output impedance

$$Z_{out} = R_2 \parallel R \parallel \frac{1}{sC} = \frac{R}{1+D_0} \frac{1}{1+s \frac{RC}{1+D_0}}$$

$$\hat{u}_c = 0, \quad \hat{u}_g = 0$$

Tip: step 2: buck converter

$$sL \hat{i}(s) = \hat{d} V_g + D_0 \hat{v}_g - \hat{v}$$

$$sC \hat{v}(s) = \hat{i} - \hat{v}/R$$

$$\hat{i}_g(s) = \hat{d} I_0 + D_0 \hat{i}$$

↑ use state-space averaging - a

anforderung

$$\hat{i}(s) \approx \hat{i}_c(s)$$

$$sL \hat{i}_c(s) = \hat{d} V_g + D_0 \hat{v}_g - \hat{v}$$

$$\hat{d}(s) \approx \frac{sL \hat{i}_c - D_0 \hat{v}_g + \hat{v}}{V_g}$$


zuerst $\hat{d}(s)$ in green dc identity

$$I_0/V_g = D_0/R$$

$$sC \hat{v} = \hat{i}_c - \frac{\hat{v}}{R}$$

$$\hat{i}_g = \hat{i}_c D_0 \left(1 + s \frac{L}{R}\right) - \frac{D_0^2}{R} \hat{v}_g + \frac{D_0}{R} \hat{v}$$

first-order small-signal equations

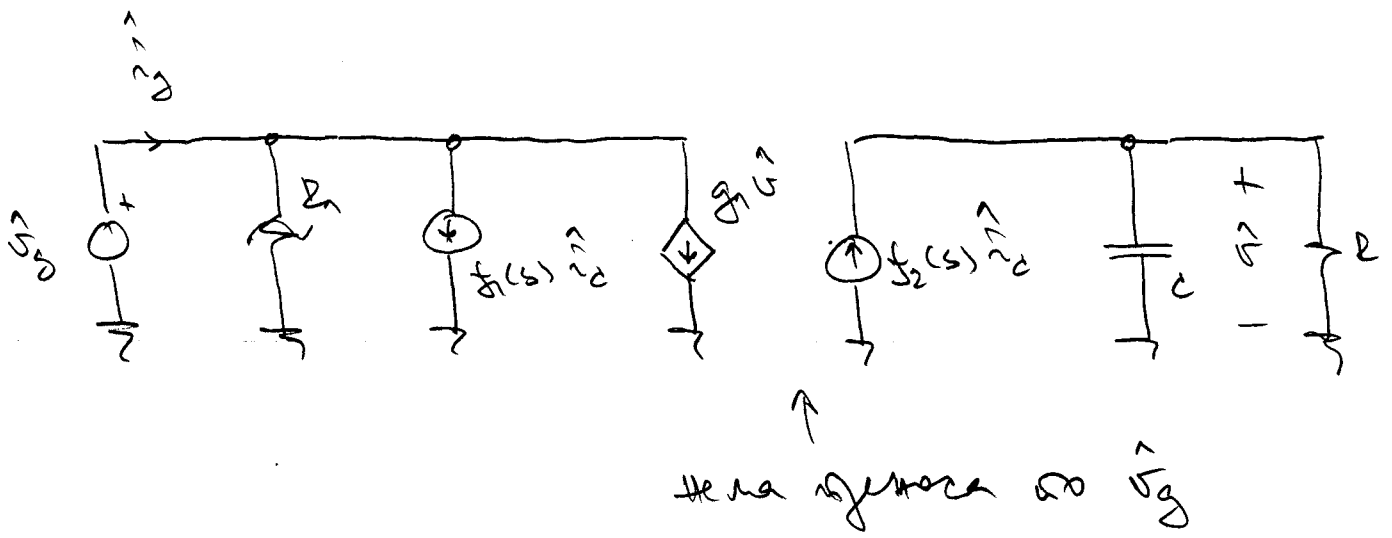

$$R_1 = -\frac{R}{f_2(s)}, \quad f_1(s) = D_0 \left(1 + s \frac{L}{R}\right), \quad g = \frac{D_0}{A} \quad |$$

$$f_2(s) = 1$$

control-to-output transfer function:

$$\frac{\hat{u}_c}{\hat{u}_g} = f_2(s) R \parallel \frac{1}{sC} = \frac{R}{1 + sRC}$$

line-to-output transfer function:


$$\frac{\hat{u}_c}{\hat{u}_g} = 0 \quad (\text{good "line rejection"})$$

output impedance

$$Z_{out} = R \parallel \frac{1}{sC} = \frac{R}{1 + sRC}$$

(more complex system)

Bemfa: CPM boost converter

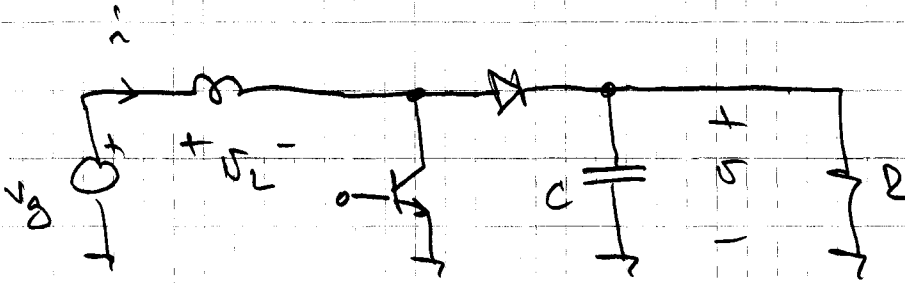


$$L \frac{di}{dt} = v_g - D_0' v + d V_0$$

$$C \frac{dv}{dt} = -\frac{v}{R} + D_0' i - d I_0$$

gabae camu . . .

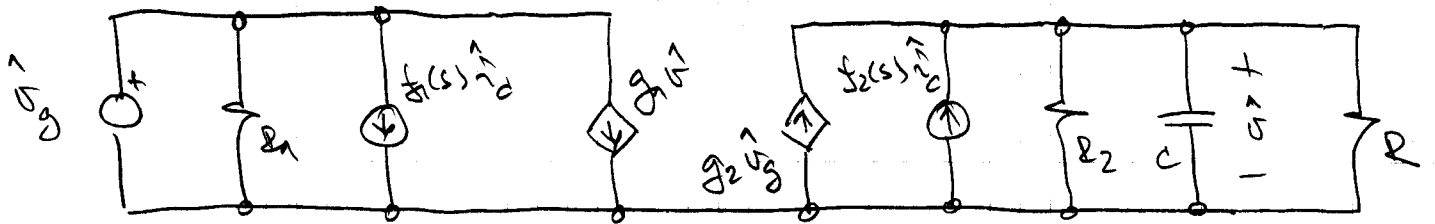A Canonical Model for the Current Programmed Mode



Simple first-order model

converter	R_1	$f_1(s)$	g_1	g_2	$f_2(s)$	R_2
buck	$-\frac{R}{D_0^2}$	$D_0(1 + s\frac{L}{R})$	$\frac{R}{D_0}$	0	1	∞
boost	∞	1	0	$\frac{1}{D_0' R}$	$D_0'(1 - \frac{sL}{D_0'^2 R})$	R
buck-boost	$-\frac{D_0' R}{D_0^2}$	$D_0(1 + s\frac{L}{D_0 R})$	$-\frac{R}{D_0}$	$-\frac{D_0'^2}{D_0 R}$	$-D_0'(1 - \frac{sD_0 L}{D_0'^2 R})$	$\frac{R}{D_0}$