

Models of Basic Converters, Current Loaded

1 DC model

| | V_{OUT}, V_C | I_{IN} | I_L |
|------------|----------------------------|-----------------------------|---------------------------|
| buck | $D_0 V_{IN}$ | $D_0 I_{OUT}$ | I_{OUT} |
| boost | $\frac{V_{IN}}{D'_0}$ | $\frac{I_{OUT}}{D'_0}$ | $\frac{I_{OUT}}{D'_0}$ |
| buck-boost | $-\frac{D_0}{D'_0} V_{IN}$ | $-\frac{D_0}{D'_0} I_{OUT}$ | $-\frac{1}{D'_0} I_{OUT}$ |

2 Pulse Width Modulation Control

| | $\frac{\widehat{v}_{OUT}(s)}{\widehat{v}_{IN}(s)}$ | $\frac{\widehat{v}_{OUT}(s)}{\widehat{i}_{OUT}(s)}$ | $\frac{\widehat{v}_{OUT}(s)}{\widehat{d}(s)}$ |
|------------|---|---|---|
| buck | $\frac{D_0}{1 + s^2 LC}$ | $-\frac{sL}{1 + s^2 LC}$ | $\frac{V_{IN}}{1 + s^2 LC}$ |
| boost | $\frac{1}{D'_0} \frac{1}{1 + s^2 \frac{LC}{D'^2_0}}$ | $\frac{-s \frac{L}{D'^2_0}}{1 + s^2 \frac{LC}{D'^2_0}}$ | $\frac{V_{IN}}{D'^2_0} \frac{1 - s \frac{LI_{OUT}}{D'_0 V_{IN}}}{1 + s^2 \frac{LC}{D'^2_0}}$ |
| buck-boost | $-\frac{D_0}{D'_0} \frac{1}{1 + s^2 \frac{LC}{D'^2_0}}$ | $\frac{-s \frac{L}{D'^2_0}}{1 + s^2 \frac{LC}{D'^2_0}}$ | $-\frac{V_{IN}}{D'^2_0} \frac{1 + s \frac{LI_{OUT}}{D'_0 V_{IN}}}{1 + s^2 \frac{LC}{D'^2_0}}$ |

3 Current Mode Control

| | $\frac{\widehat{v}_{OUT}(s)}{\widehat{v}_{IN}(s)}$ | $\frac{\widehat{v}_{OUT}(s)}{\widehat{i}_{OUT}(s)}$ | $\frac{\widehat{v}_{OUT}(s)}{\widehat{i}_L(s)}$ |
|------------|--|---|--|
| buck | 0 | $-\frac{1}{sC}$ | $\frac{1}{sC}$ |
| boost | $\frac{1}{D'_0} \frac{1}{1 + s \frac{CV_{IN}}{D'_0 I_{OUT}}}$ | $-\frac{V_{IN}}{D'_0 I_{OUT}} \frac{1}{1 + s \frac{CV_{IN}}{D'_0 I_{OUT}}}$ | $\frac{V_{IN}}{I_{OUT}} \frac{1 - s \frac{LI_{OUT}}{D'_0 V_{IN}}}{1 + s \frac{CV_{IN}}{D'_0 I_{OUT}}}$ |
| buck-boost | $-\frac{D_0}{D'_0} \frac{1}{1 - s \frac{CV_{IN}}{D'_0 I_{OUT}}}$ | $\frac{V_{IN}}{D'_0 I_{OUT}} \frac{1}{1 - s \frac{CV_{IN}}{D'_0 I_{OUT}}}$ | $\frac{V_{IN}}{I_{OUT}} \frac{1 + s \frac{LI_{OUT}}{D'_0 V_{IN}}}{1 - s \frac{CV_{IN}}{D'_0 I_{OUT}}}$ |