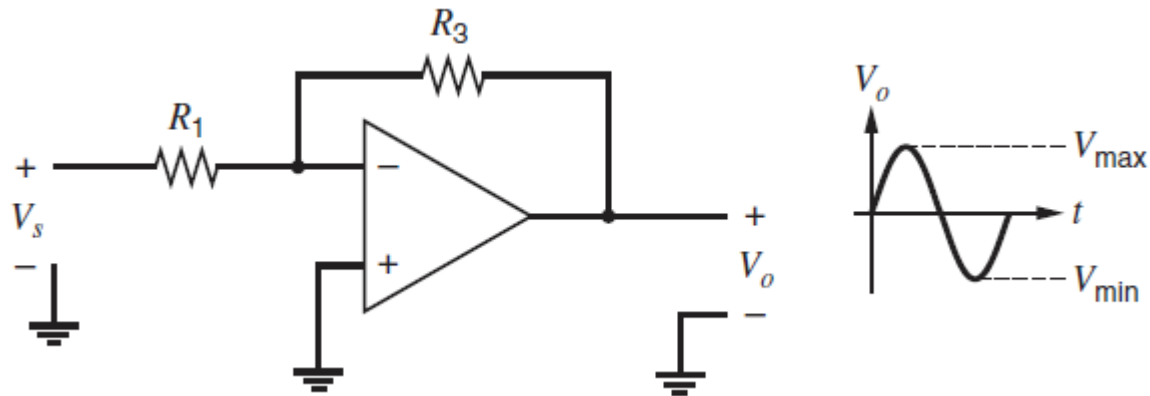


Osnovi analogne elektronike


IV semestar

**KOLA SA OPERACIONIM
POJAČAVAČIMA I NEGATIVNOM
POVRATNOM SPREGOM**


Operacioni pojačavač sa jednostrukim izlazom



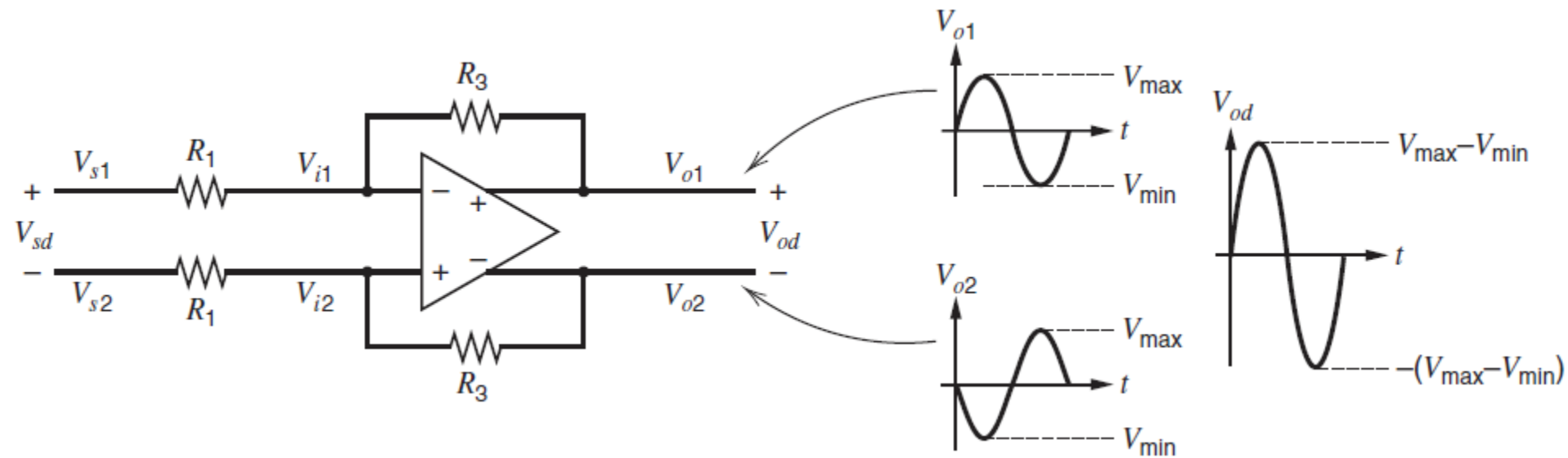Operacioni pojačavač sa diferencijalnim izlazom



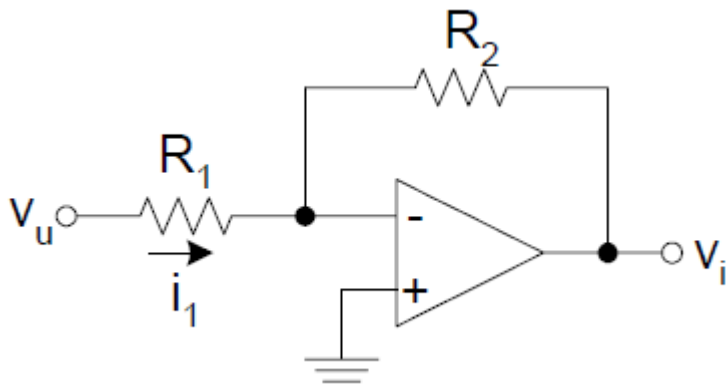Invertujući pojačavač sa beskonačnim pojačanjem




$$i_1 = \frac{v_u}{R_1}$$

$$v_i = -R_2 i_1 = -\frac{R_2}{R_1} v_u$$

$$A_v = \frac{v_i}{v_u} = -\frac{R_2}{R_1}$$

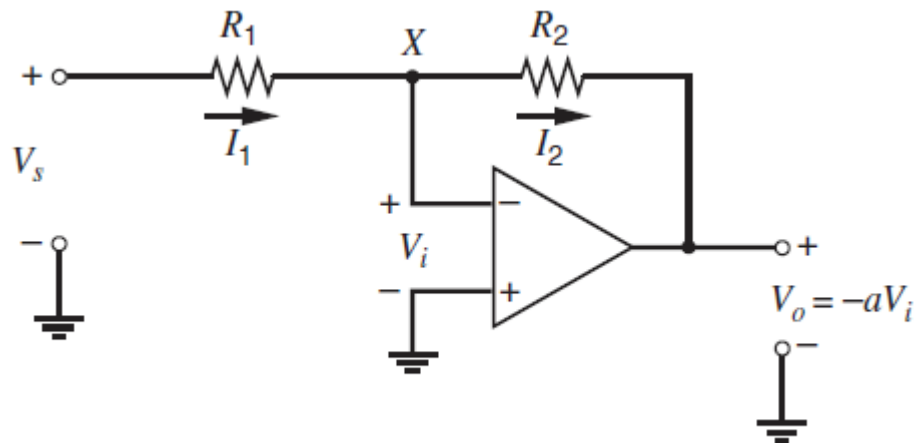Invertujući pojačavač sa konačnim pojačanjem



$$\frac{V_s - V_i}{R_1} + \frac{V_o - V_i}{R_2} = 0$$


$$V_i = \frac{-V_o}{a}$$

$$\frac{V_o}{V_s} = -\frac{R_2}{R_1} \left[\frac{1}{1 + \frac{1}{a} \left(1 + \frac{R_2}{R_1} \right)} \right]$$

$$\frac{V_o}{V_s} \simeq -\frac{R_2}{R_1}$$

$$a \left(\frac{R_1}{R_1 + R_2} \right) \gg 1$$

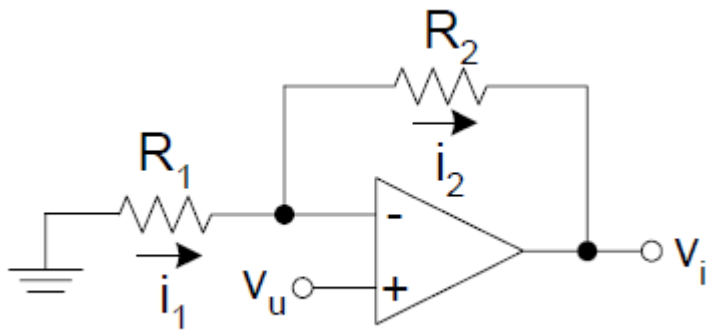Neinvertujući pojačavač sa beskonačnim pojačanjem




$$i_1 = \frac{v_u}{R_1}$$

$$i_2 = \frac{v_i - v_u}{R_2} = i_1 = \frac{v_u}{R_1}$$

$$A_v = \frac{v_i}{v_u} = \frac{R_1 + R_2}{R_1} = 1 + \frac{R_2}{R_1}$$

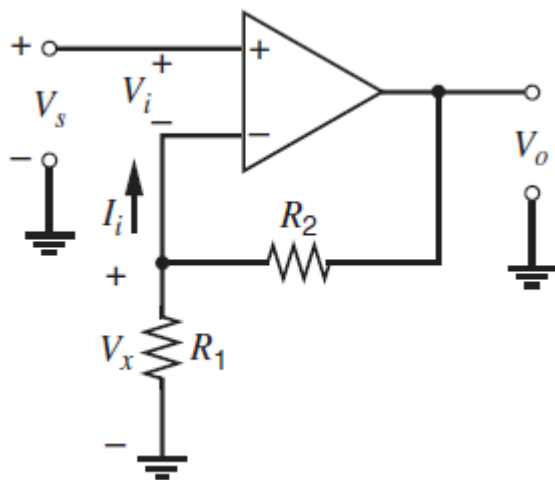
Neinvertujući pojačavač sa konačnim pojačanjem



$$V_x = V_o \left(\frac{R_1}{R_1 + R_2} \right) = V_s - \frac{V_o}{a}$$

$$\frac{V_o}{V_s} = \left(1 + \frac{R_2}{R_1} \right) \frac{\frac{aR_1}{R_1 + R_2}}{1 + \frac{aR_1}{R_1 + R_2}} \simeq \left(1 + \frac{R_2}{R_1} \right) \quad a \left(\frac{R_1}{R_1 + R_2} \right) \gg 1$$

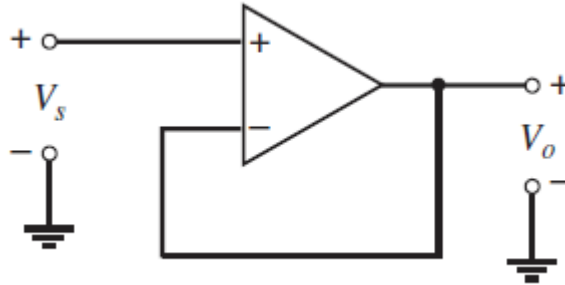Jedinični bafer sa beskonačnim pojačanjem




$$R_1 \rightarrow \infty$$

$$R_2 = 0$$

$$a \gg 1$$

$$\frac{V_o}{V_s} = 1$$

Sabirač

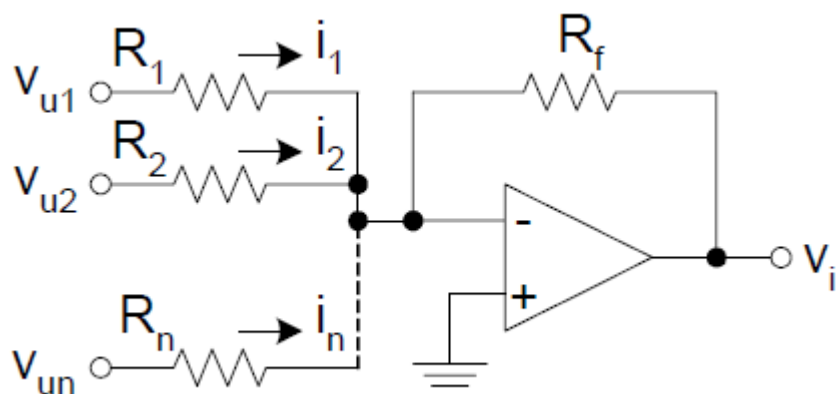

$$i_k = \frac{v_{uk}}{R_k}, k = 1, 2, \dots, n$$


$$v_i = -R_f \sum_{k=1}^n i_k = -R_f \sum_{k=1}^n \frac{v_{uk}}{R_k}$$

Za identične ulazne otpornike:

$$R_1 = R_2 = \dots = R_n = R$$

$$v_i = -R_f \sum_{k=1}^n \frac{v_{uk}}{R_k} = -\frac{R_f}{R} \sum_{k=1}^n v_{uk}$$

Diferencijalni pojačavač

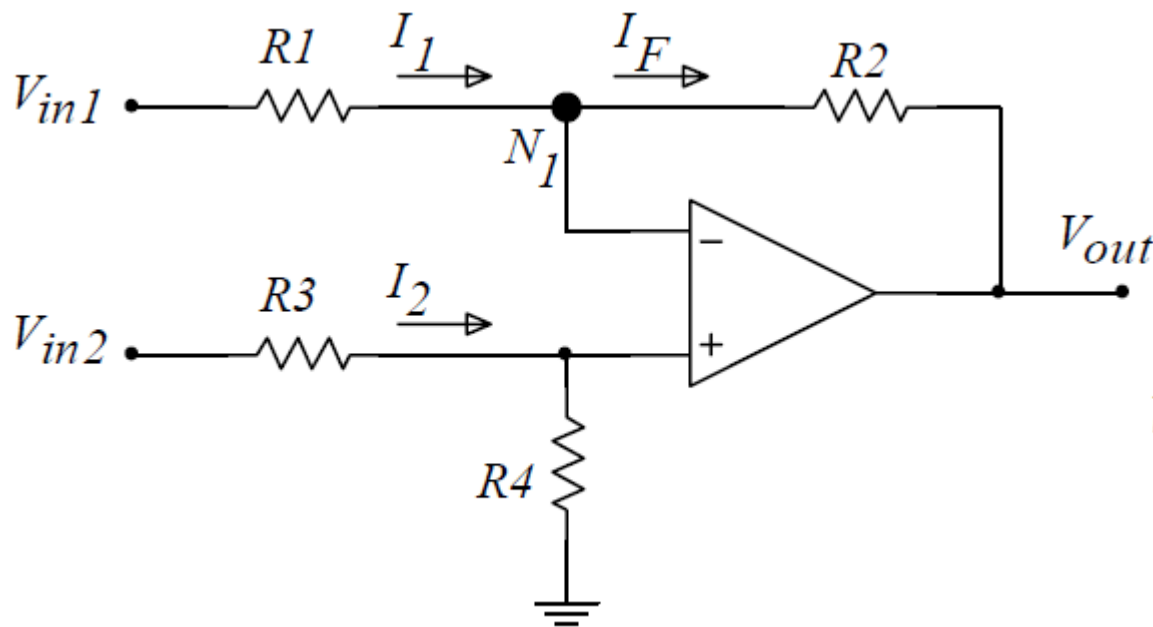

Izlazni napon se računa kao superpozicija dva napona:

$$V_{out1} = -V_{in1} \left(\frac{R2}{R1} \right)$$

$$V_{out2} = V_{in2} \left(\frac{R4}{R3 + R4} \right) \left(1 + \frac{R2}{R1} \right)$$

$$V_{out} = V_{out2} + V_{out1} = V_{in2} \left(\frac{R4}{R3 + R4} \right) \left(1 + \frac{R2}{R1} \right) - V_{in1} \frac{R2}{R1}$$


$$V_{out} = \frac{R2}{R1} (V_{in2} - V_{in1})$$

Izlazni napon je proporcionalan razlici ulaznih napona ako je:

$$\left(\frac{R4}{R3 + R4} \right) \left(1 + \frac{R2}{R1} \right) = \frac{R2}{R1}$$

$$\frac{R4}{R3} = \frac{R2}{R1}$$

Diferencijalni pojačavač

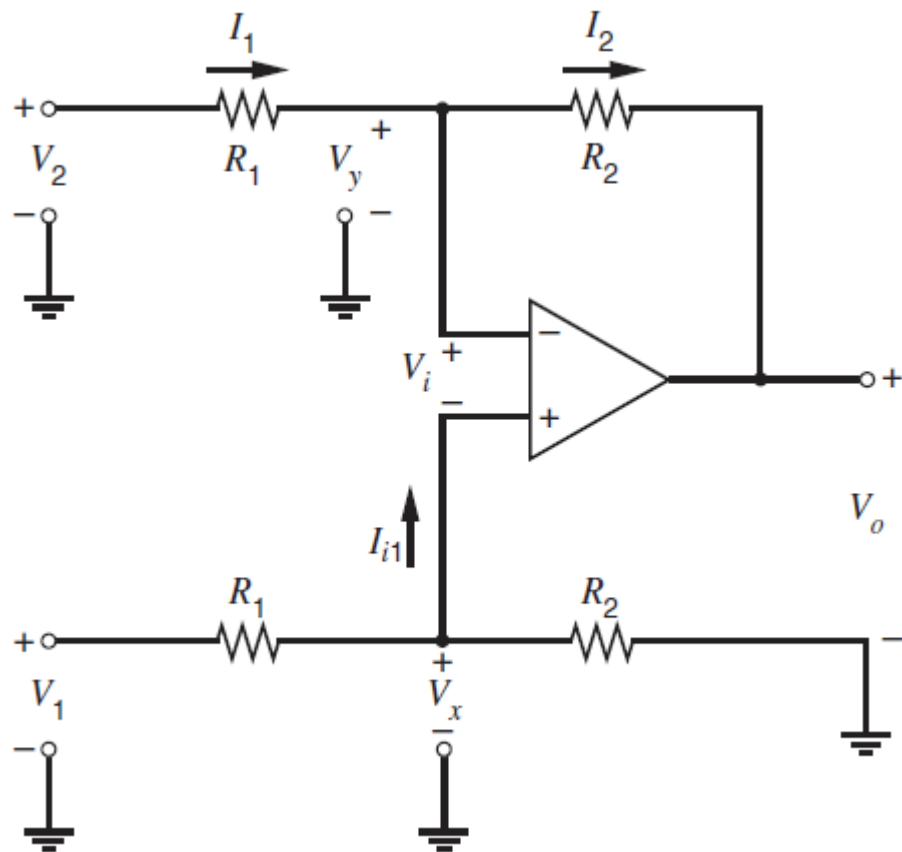

$$V_x = V_1 \left(\frac{R_2}{R_1 + R_2} \right)$$

$$I_1 = \left(\frac{V_2 - V_y}{R_1} \right) = I_2$$

$$V_o = V_y - I_2 R_2$$


$$a \gg 1$$

$$V_i = 0$$


$$V_y = V_x$$

$$V_o = \frac{R_2}{R_1} (V_1 - V_2)$$


Instrumentacioni pojačavač

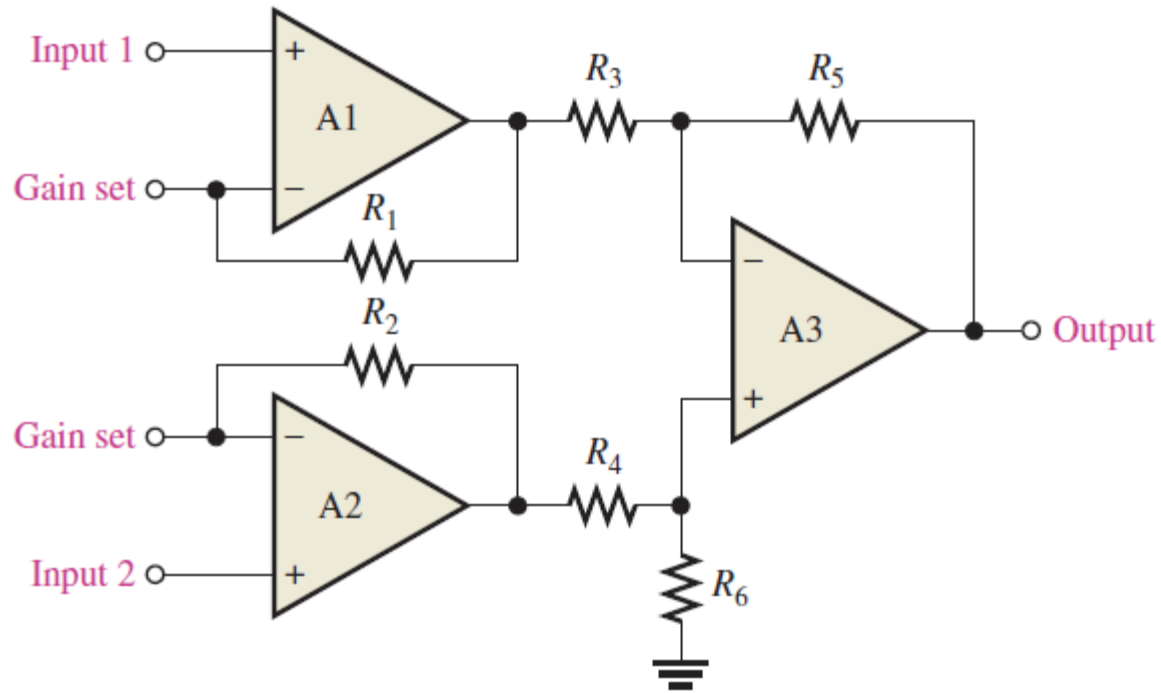

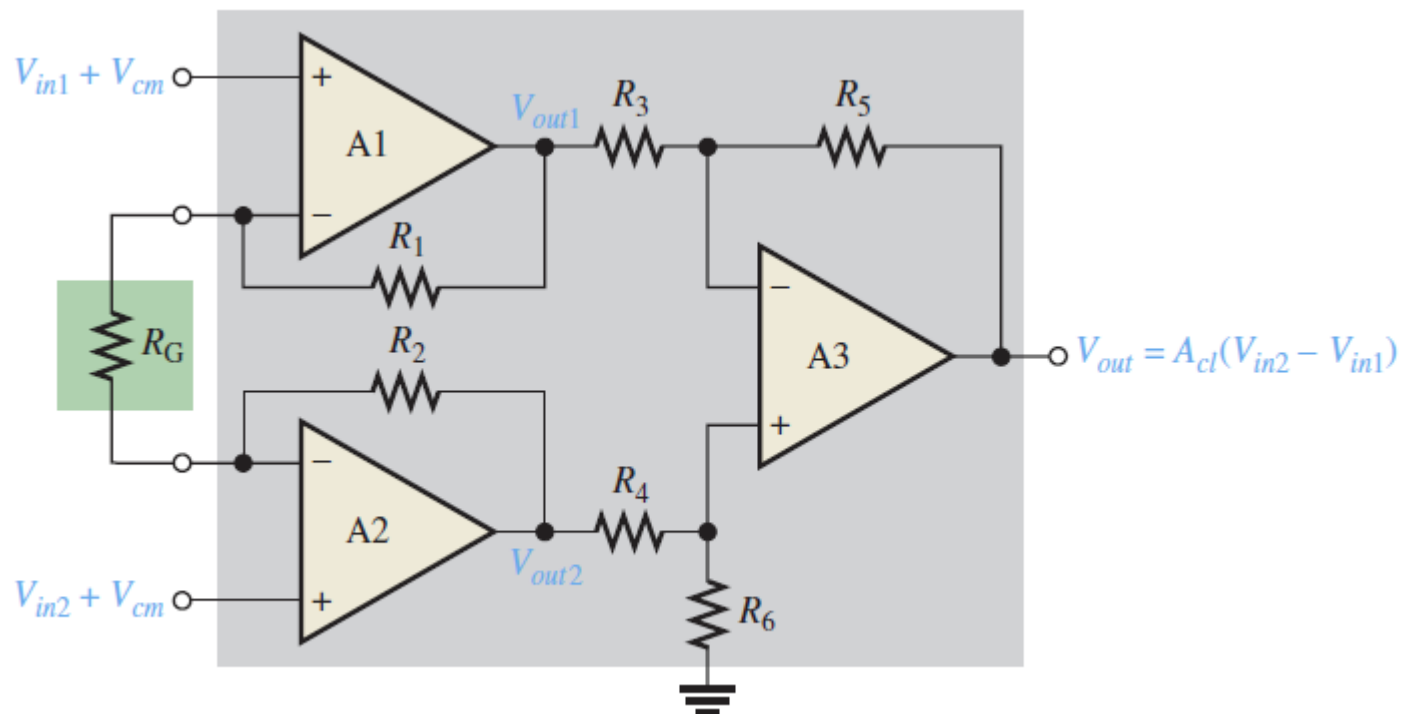
Instrumentacioni pojačavač sa otpornikom za zadavanje pojačanja



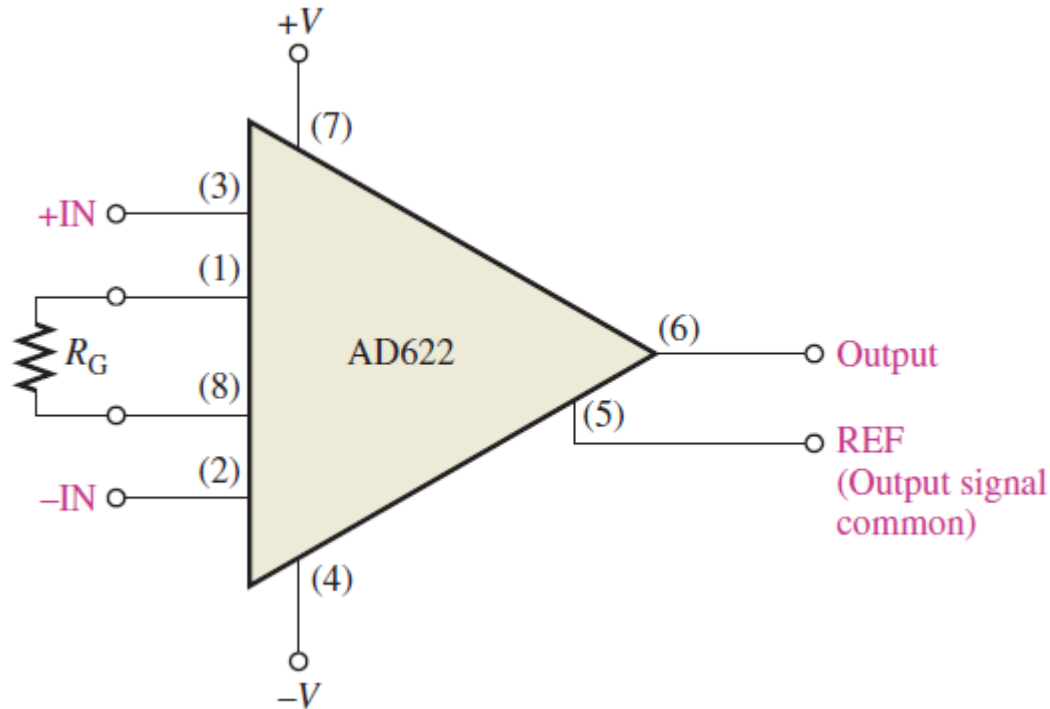
Integrirani instrumentacioni pojačavač sa otpornikom za zadavanje pojačanja



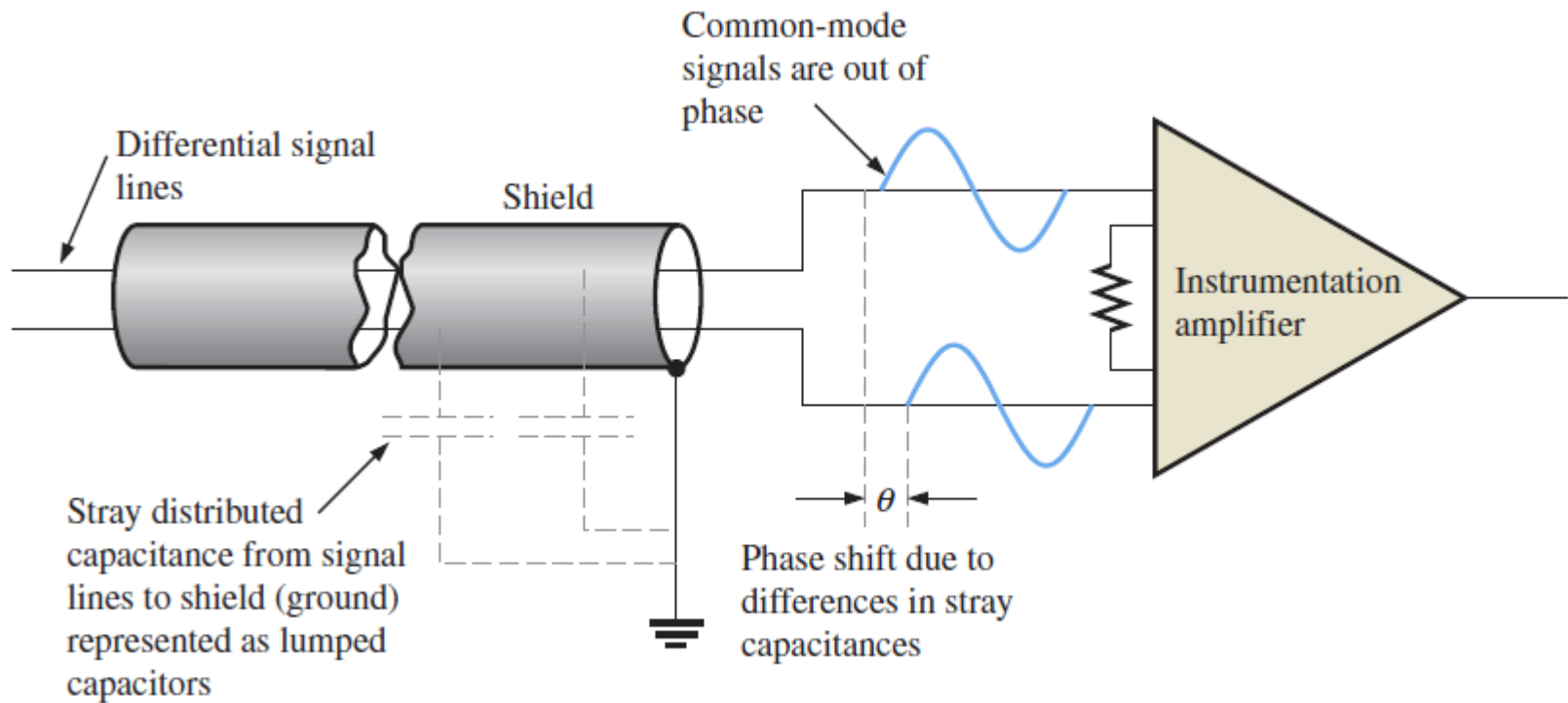
Povezivanje instrumentacionog pojačavača sa udaljenim senzorom



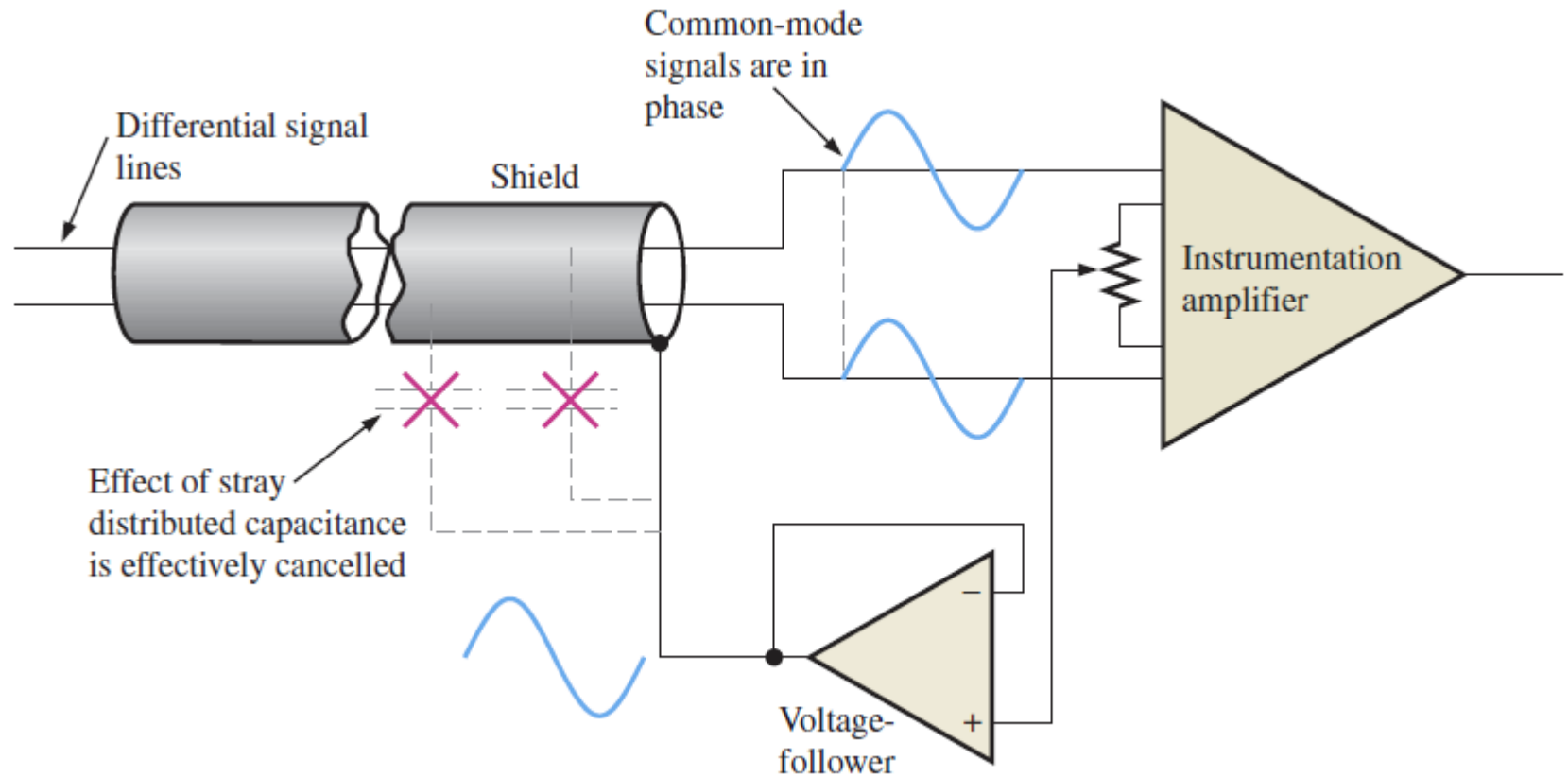Povezivanje instrumentacionog pojačavača sa udaljenim senzorom



Instrumentacioni pojačavač

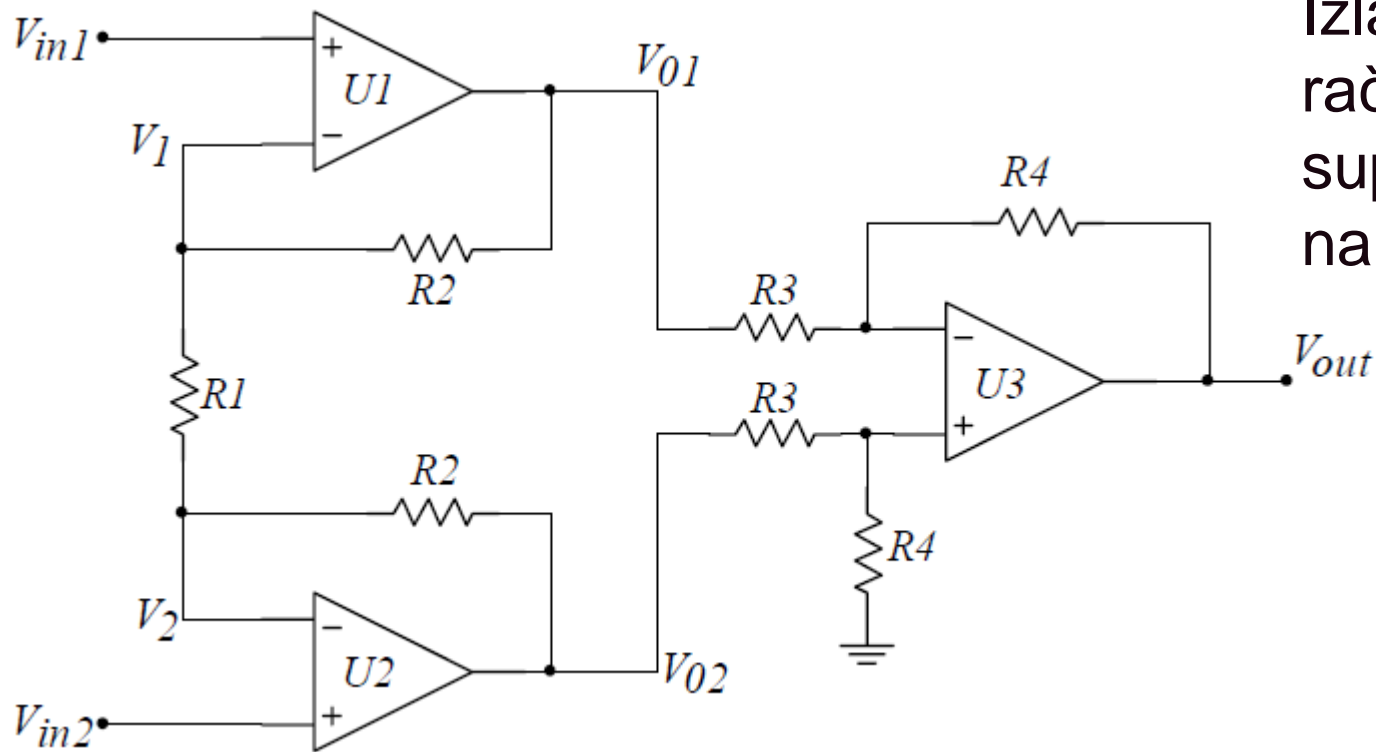

Izlazni napon se računa kao superpozicija dva napona:


$$V_{01} = \left(1 + \frac{R2}{R1}\right) V_{in1} - \frac{R2}{R1} V_{in2}$$

$$V_{out} = V_{01} + V_{02}$$

$$V_{02} = \left(1 + \frac{R2}{R1}\right) V_{in2} - \frac{R2}{R1} V_{in1}$$

$$V_{out} = \frac{R4}{R3} \left(1 + \frac{2R2}{R1}\right) (V_{in2} - V_{in1})$$

Logaritamski pojačavač

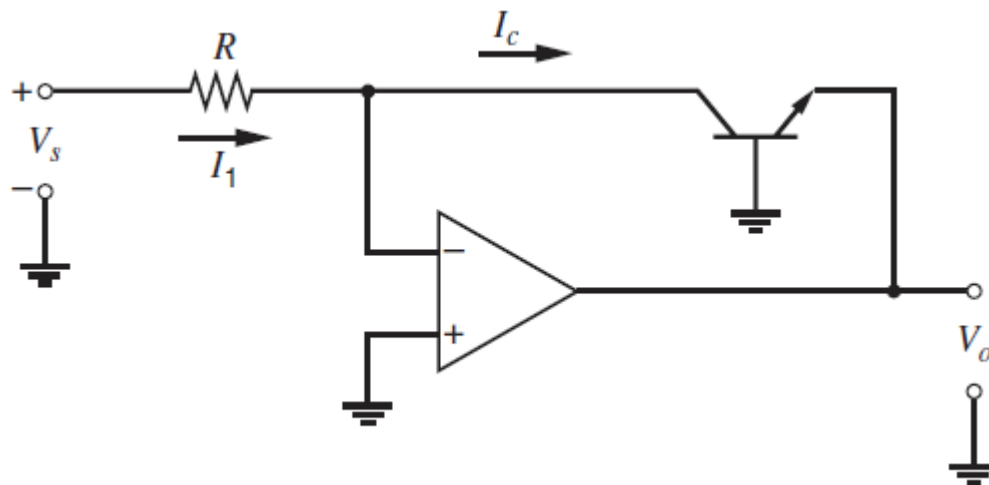


$$I_1 = \frac{V_s}{R} = I_c = I_S \left[\exp \left(\frac{V_{be}}{V_T} \right) - 1 \right] \simeq I_S \exp \left(\frac{V_{be}}{V_T} \right)$$

$$V_o = -V_{be}$$

$$V_o = -V_T \ln \left(\frac{V_s}{I_S R} \right)$$

Integrator

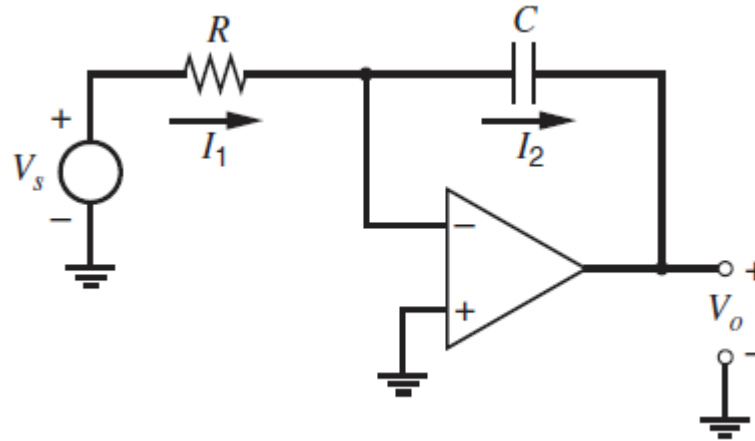


$$I_1 = \frac{V_s}{R} = I_2$$

$$V_o = -\frac{1}{C} \int_0^t I_2 d\tau + V_o(0)$$

$$V_o(t) = -\frac{1}{RC} \int_0^t V_s(\tau) d\tau + V_o(0)$$

Trorežimski integrator

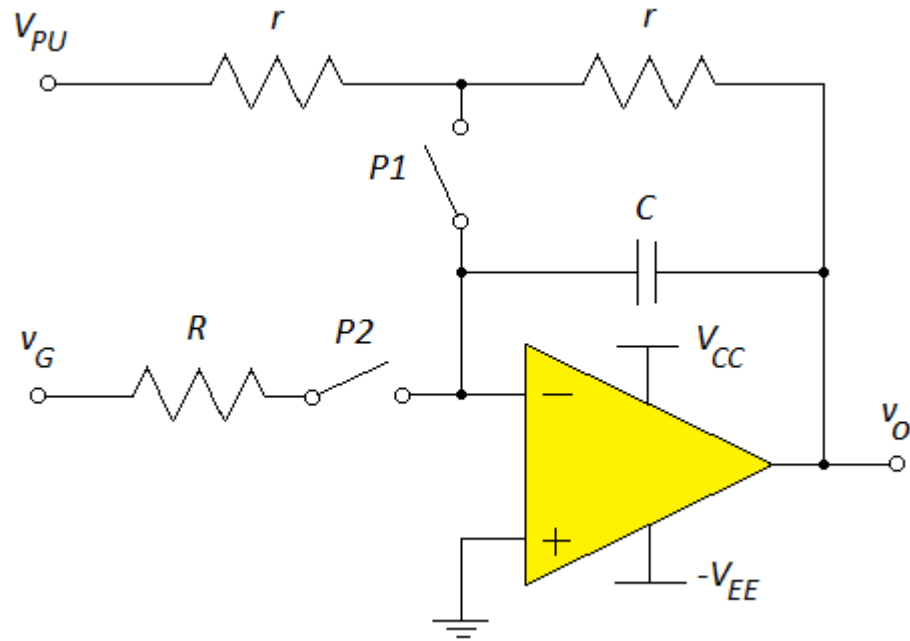


Tri režima rada u zavisnosti od položaja prekidača $P1$ i $P2$ su:

- ❖ postavljanje početnih uslova
- ❖ integracija
- ❖ pamćenje.

Otpornici r se kompromisno biraju da budu što manji za brže postavljanje početnih uslova, ali i što veći za ograničenje izlazne struje operacionog pojačavača u režimima integracije i pamćenja.

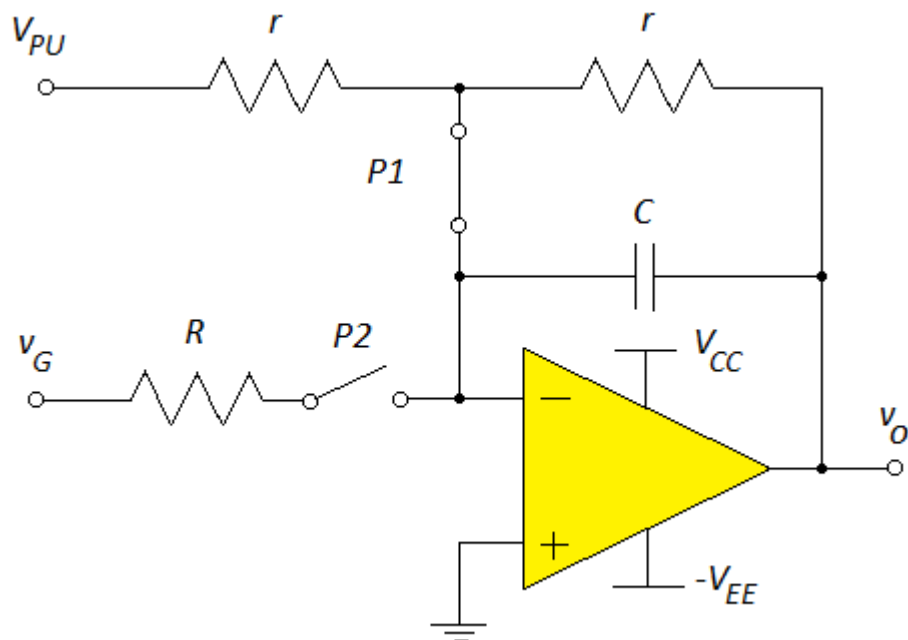
Trorežimski integrator režim postavljanja početnih uslova



Na kraju postavljanja početnih uslova, struja kroz kondenzator C je nula, tako da pojačavač radi kao invertujući pojačavač.

$$v_O = -\frac{r}{r} V_{PU} = -V_{PU}$$


Trorežimski integrator režim integracije

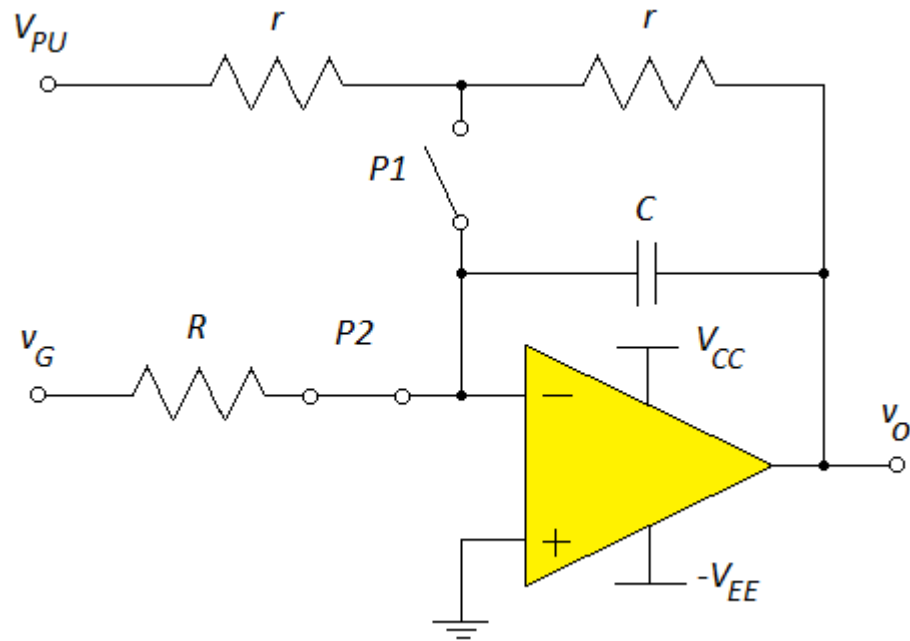

Na kraju režima integracije, izlazni napon je:

$$v_O(T_{INT}) = -V_{PU} - \frac{1}{RC} \int_0^{T_{INT}} v_G(t) dt$$

Trorežimski integrator režim pamćenja

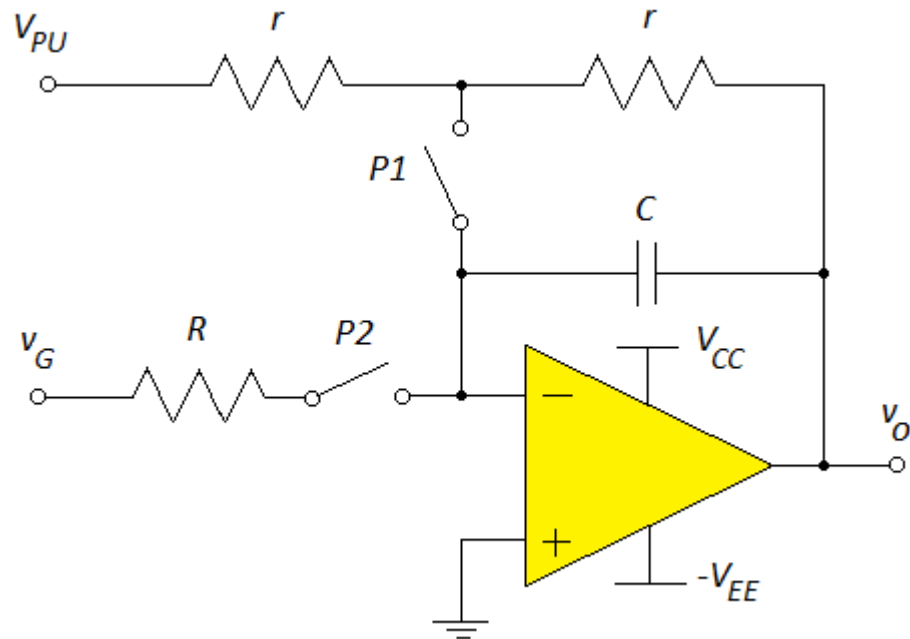


Na kraju režima pamćenja, izlazni napon je:

$$v_O(T_{PAM}) = -V_{PU} - \frac{1}{RC} \int_0^{T_{INT}} v_G(t) dt$$

Trorežimski integrator sa brzim postavljanjem početnih uslova

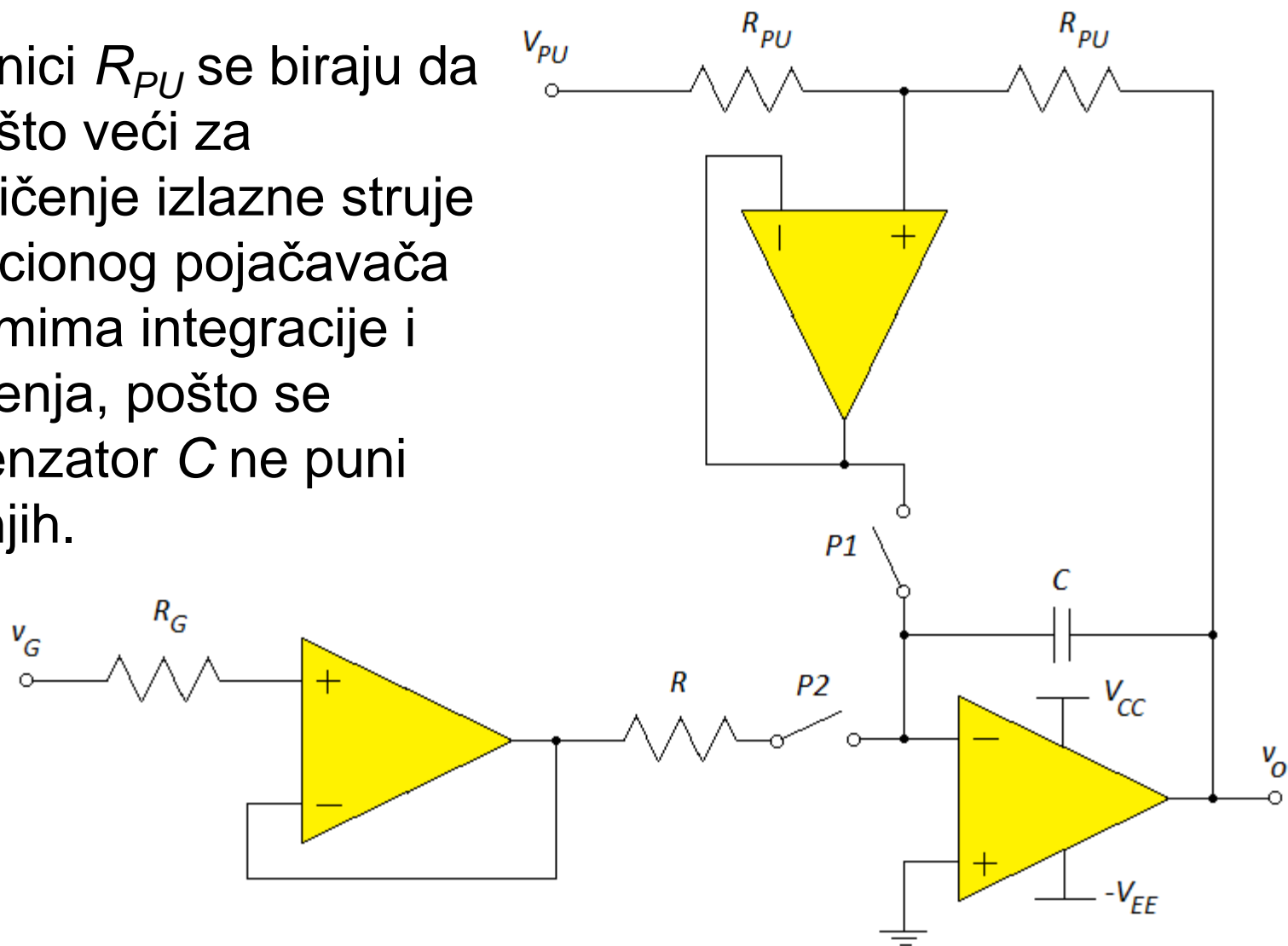
Otpornici R_{PU} se biraju da budu što veći za ograničenje izlazne struje operacionog pojačavača u režimima integracije i pamćenja, pošto se kondenzator C ne puni kroz njih.



Trorežimski integrator vremenski dijagrami

Primer: $V_{PU} < 0$ i $v_G = \text{const} > 0$

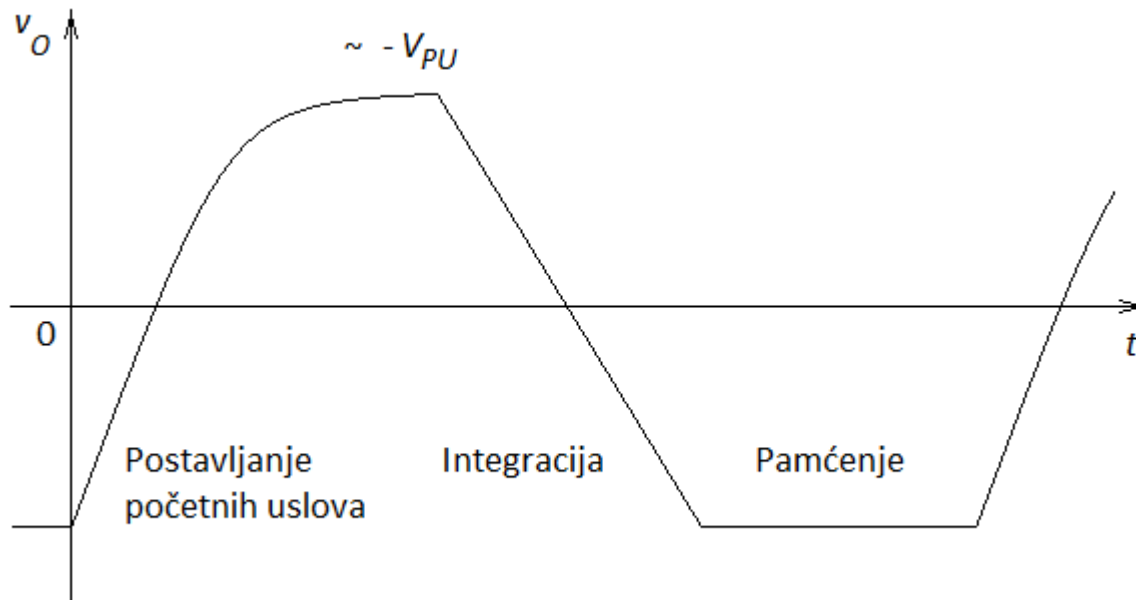
Za vreme režima integracije, izlazni napon je: $v_O(t) = -V_{PU} - \frac{V_G}{RC}t$




Trorežimski integrator sa brzim zadavanjem početnih uslova vremenski dijagrami

Primer: $V_{PU} < 0$ i $v_G = \text{const} > 0$

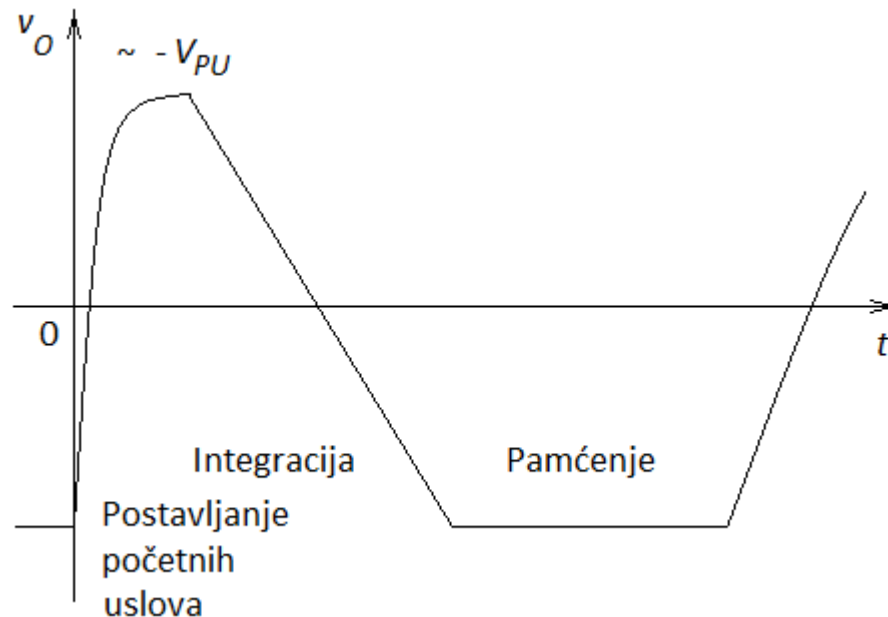Za vreme režima integracije, izlazni napon je: $v_O(t) = -V_{PU} - \frac{V_G}{RC}t$




Diferencijator

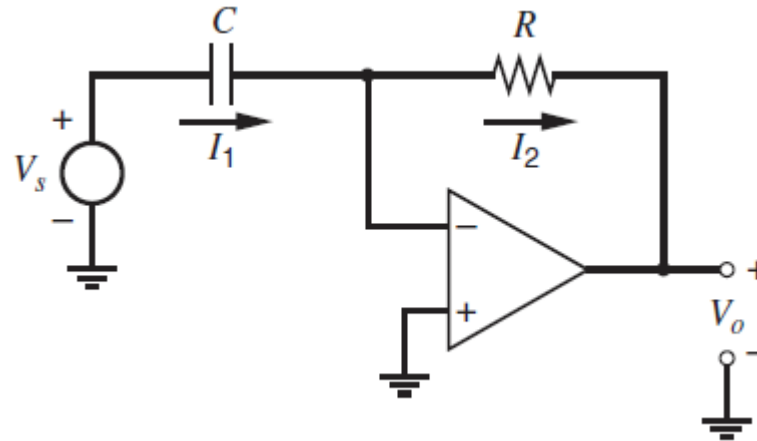


$$I_1 = C \frac{dV_s}{dt} = I_2$$

$$V_o = -RI_2 = -RC \frac{dV_s}{dt}$$


Diferencijalni invertujući pojačavač

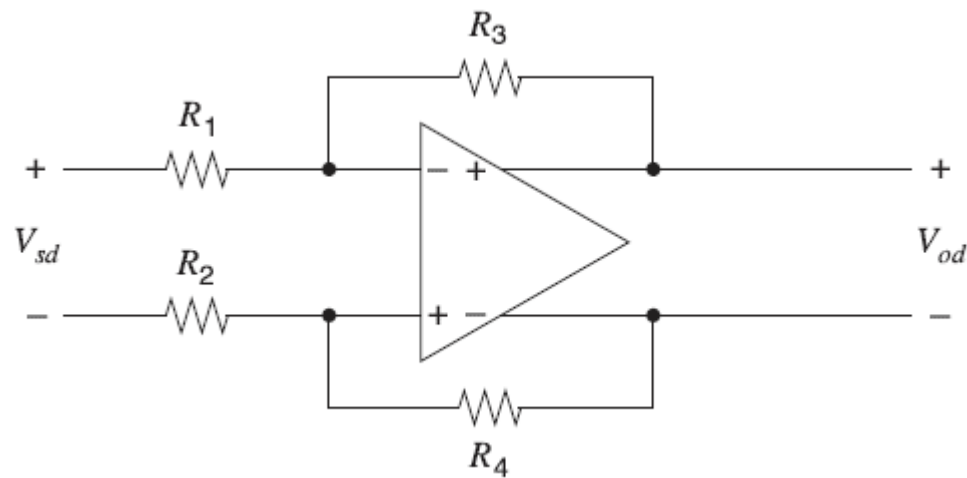


Diferencijalni integrator

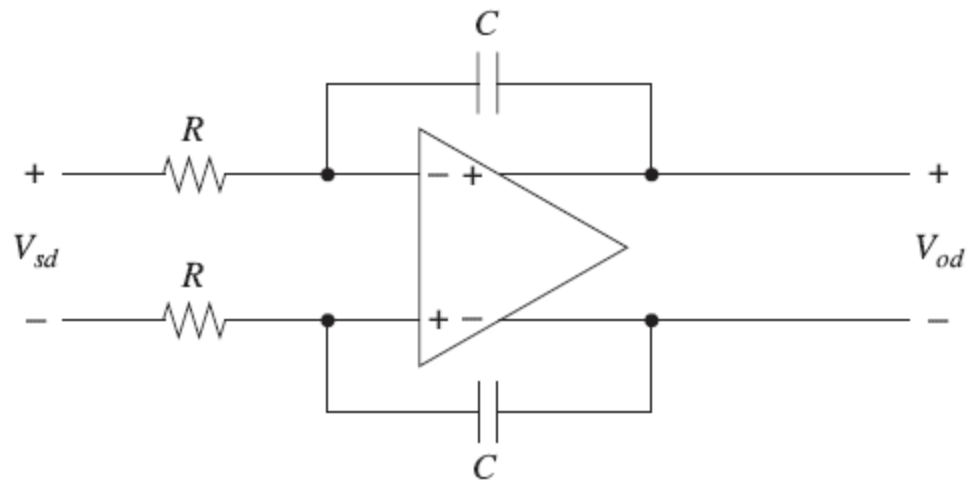

Diferencijalni diferencijator

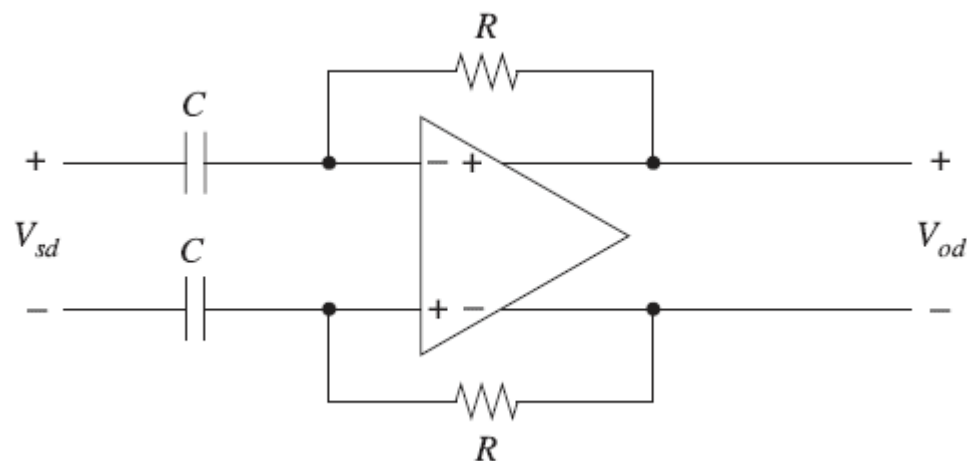

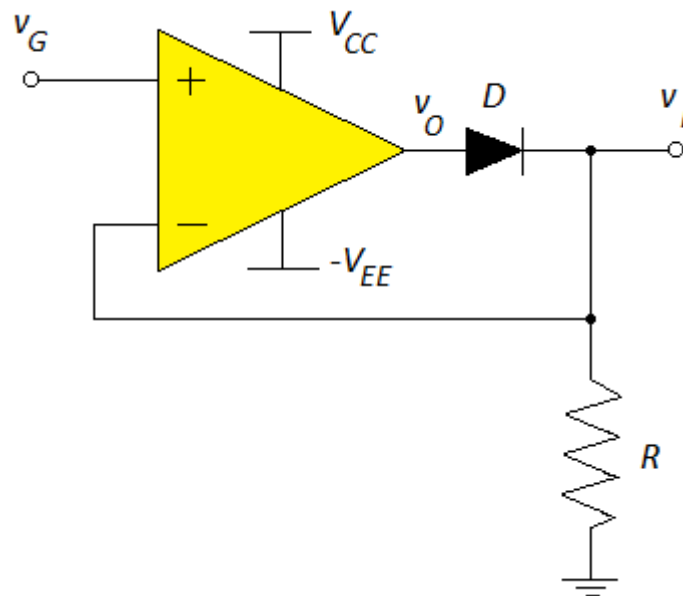
Polutalasni usmerač sa jednom diodom i operacionim pojačavačem



Ukupno postoji 8 varijanti kola u zavisnosti od:


- ❖ Smera diode D (prikazanog ili obrnutog)
- ❖ Izvora za napajanje ($V_R < 0$) umesto mase na otporniku R
- ❖ Izvora za napajanje ($V_R > 0$) umesto mase na otporniku R

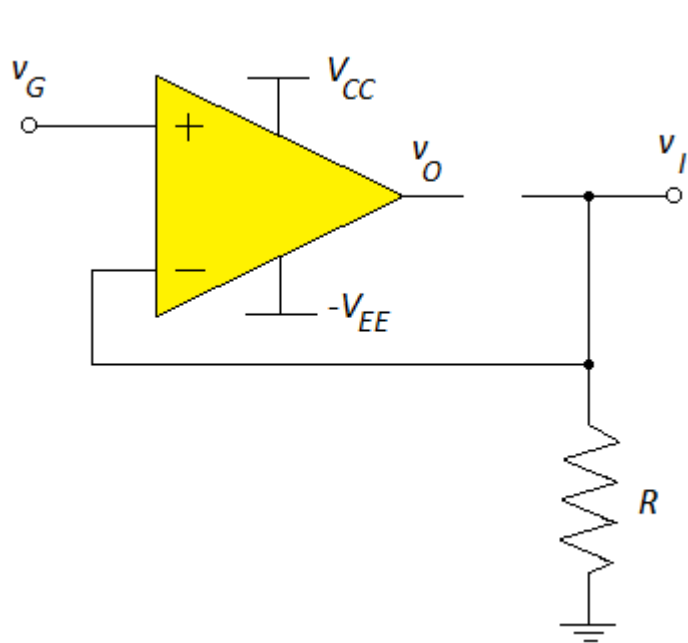Polutalasni usmerač sa jednom diodom i beskonačnim pojačanjem






Dioda ne vodi, pa ne postoji negativna povratna sprega.
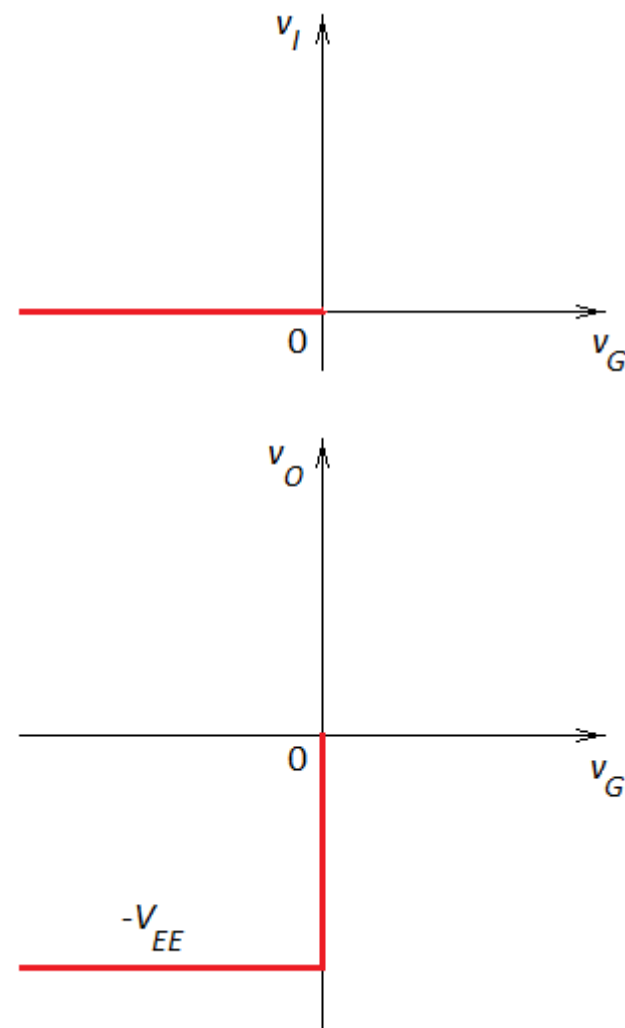
$$v_G < 0 \quad v_I = 0 \quad v_O = -V_{EE}$$



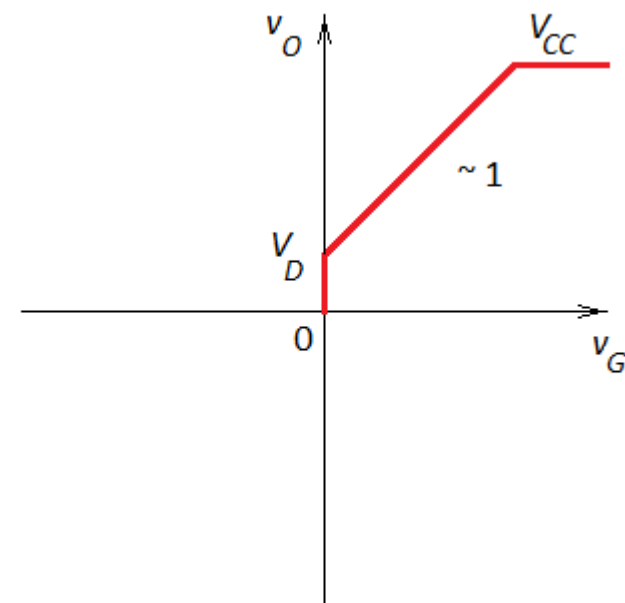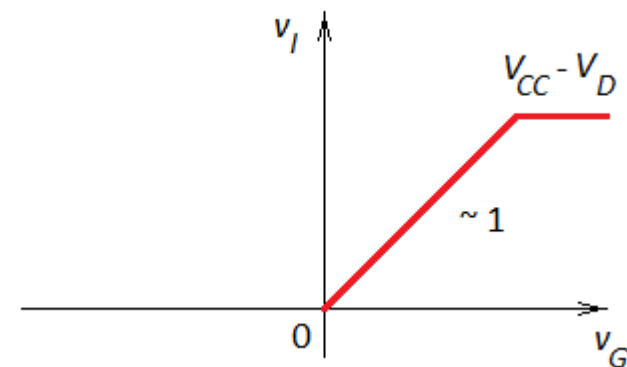
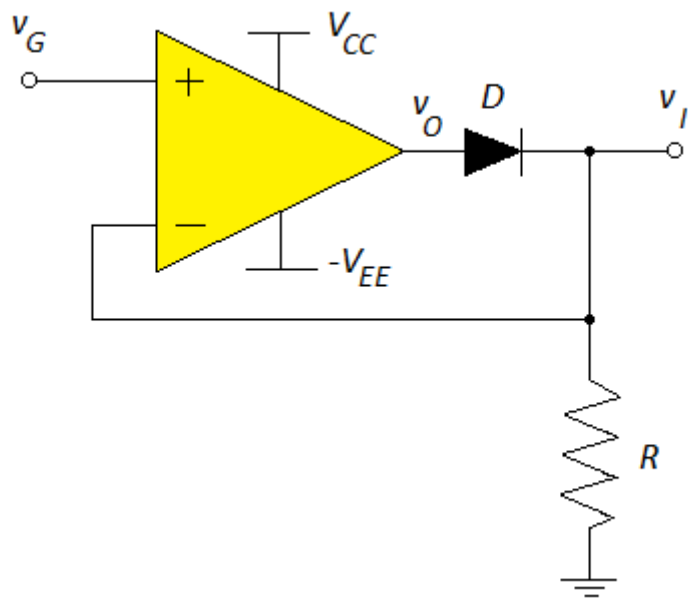
Polutalasni usmerač sa jednom diodom i beskonačnim pojačanjem




Dioda vodi, pa postoji negativna povratna sprega.

$$v_G \geq 0 \quad v_I = v_G \quad v_O = v_G + V_D$$

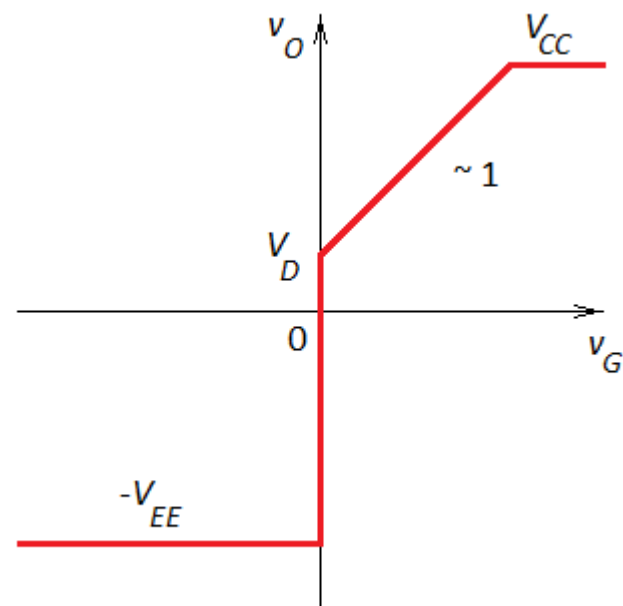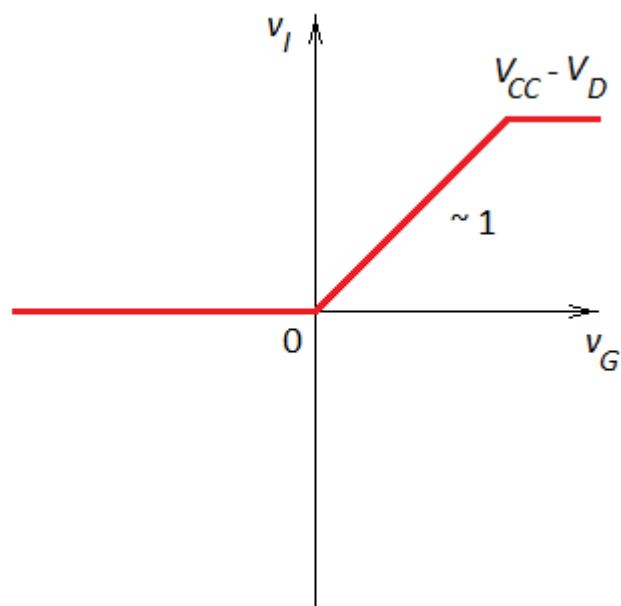Polutalasni usmerač sa jednom diodom i beskonačnim pojačanjem




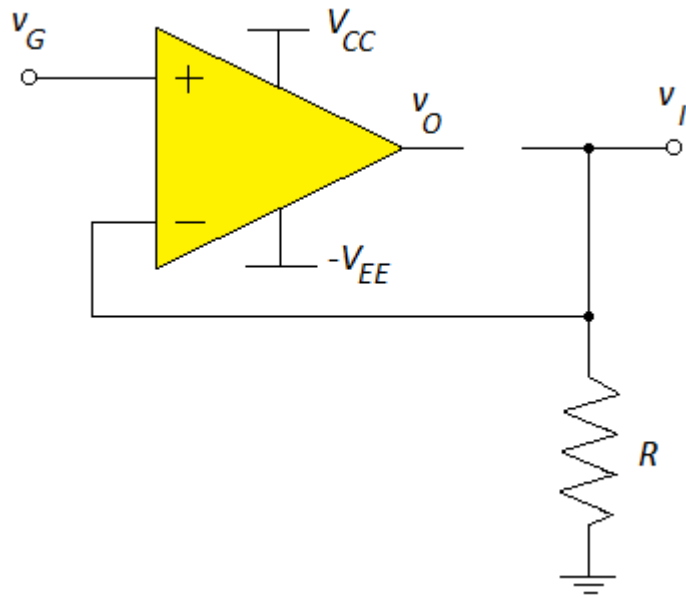Polutalasni usmerač sa jednom diodom i konačnim pojačanjem




Dioda ne vodi, pa ne postoji negativna povratna sprega.
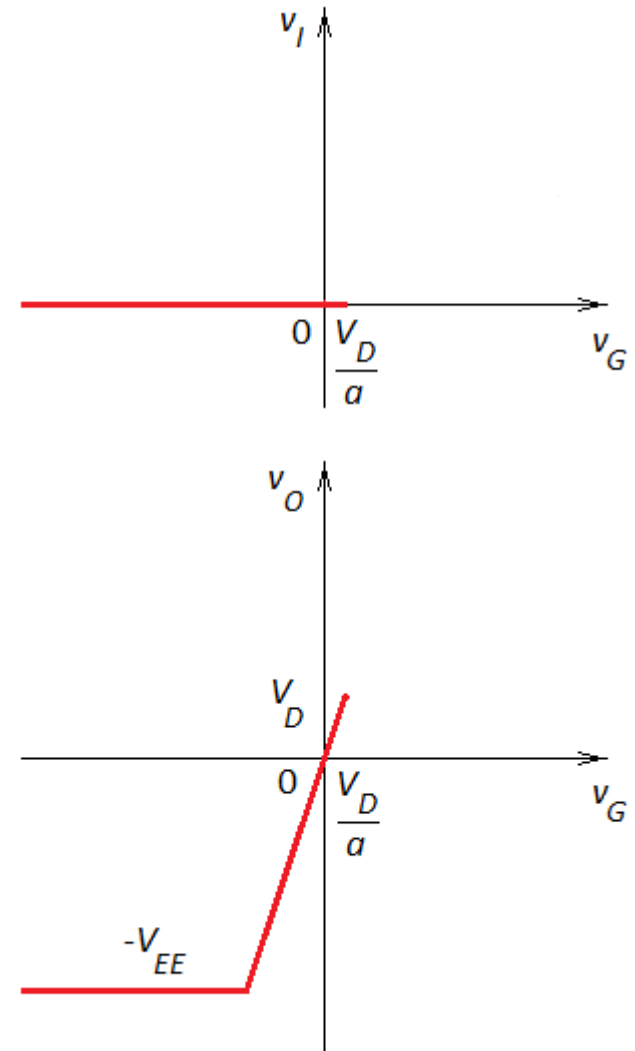
$$v_G < \frac{V_D}{a} \quad v_I = 0 \quad v_O = av_G \quad v_O = -V_{EE}$$





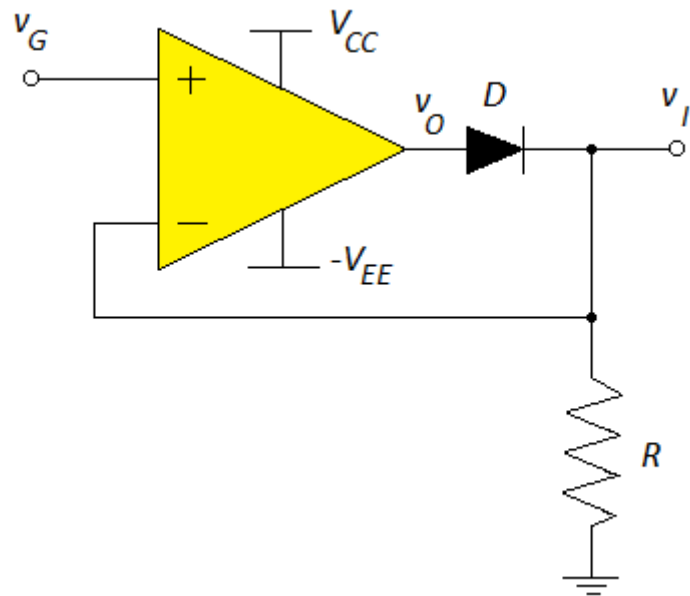Polutalasni usmerač sa jednom diodom i konačnim pojačanjem



$$v_I = \frac{a}{a+1} v_G - \frac{1}{a+1} V_D$$

$$v_O = \frac{a}{a+1} (v_G + V_D)$$

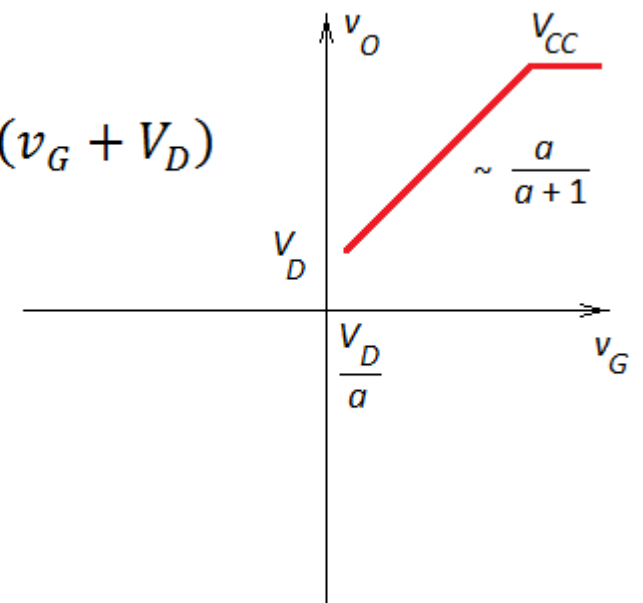
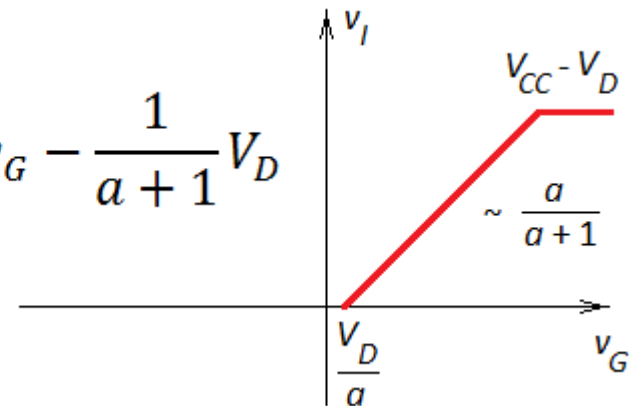


$$v_G \geq \frac{V_D}{a} \quad v_O = a(v_G - v_I)$$



$$v_O = v_I + V_D \quad a(v_G - v_I) = v_I + V_D$$

$$av_G = (a+1)v_I + V_D$$

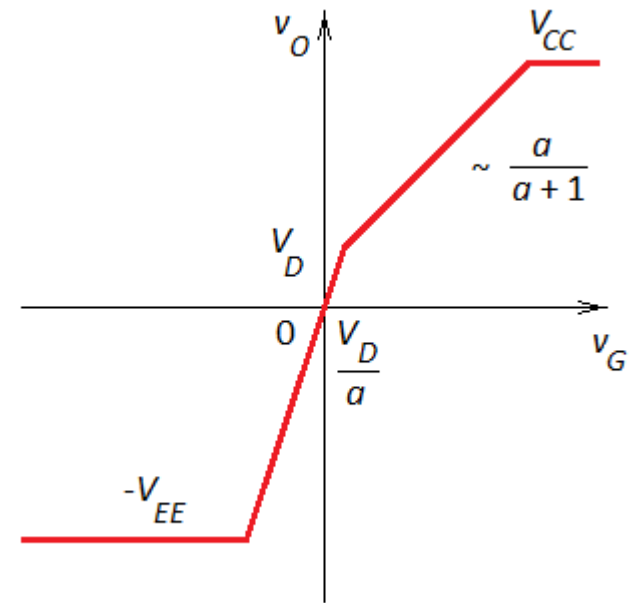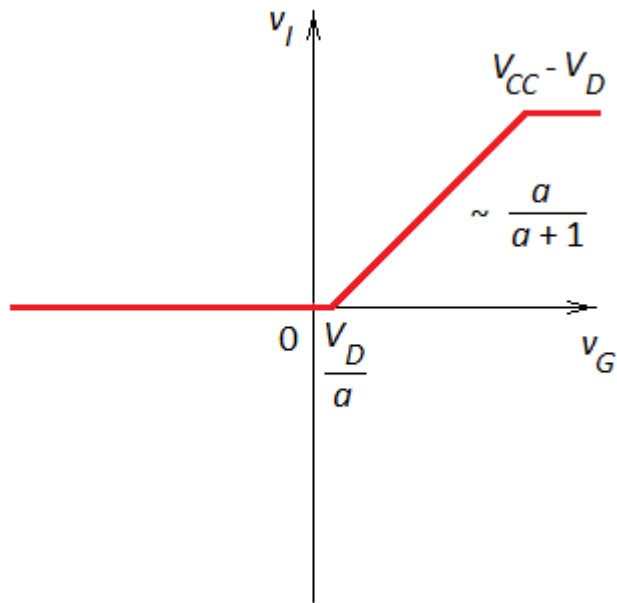
Polutalasni usmerač sa jednom diodom i konačnim pojačanjem



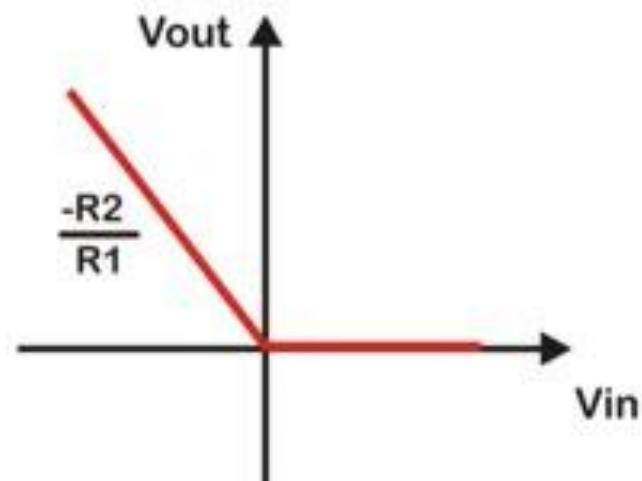
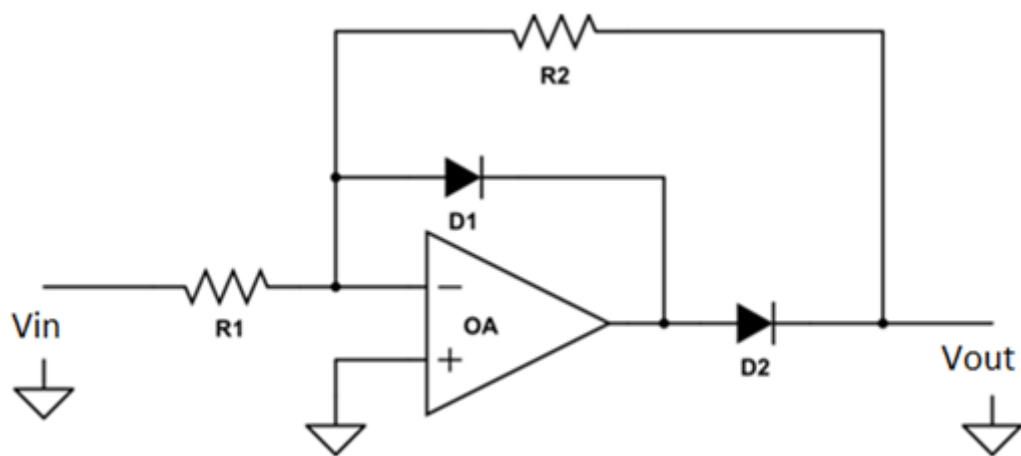
Polutalasni usmerač sa dve diode (šema, prenosna funkcija i vremenski dijagrami)



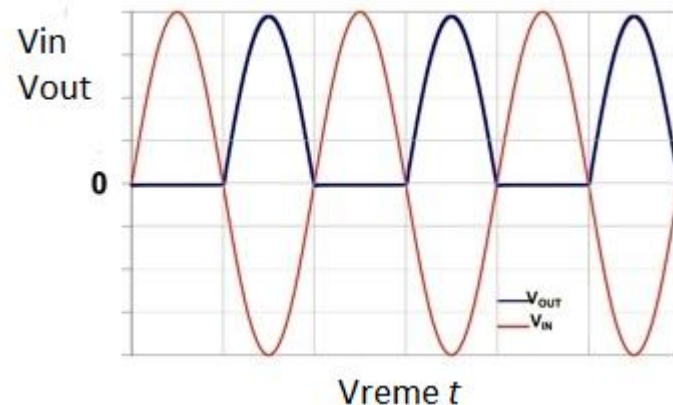Negativna povratna sprega ne menja polaritet signala na ulazu pojačavača, tako da je ulaz na invertujućem (-) priključku pozitivan za pozitivan V_{in} , i negativan za negativno V_{in} .



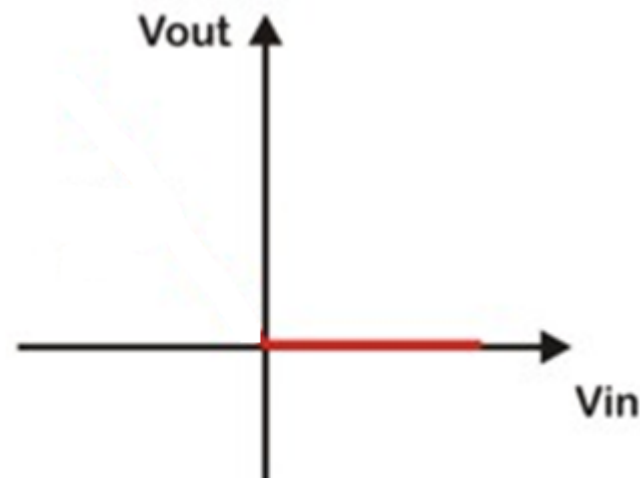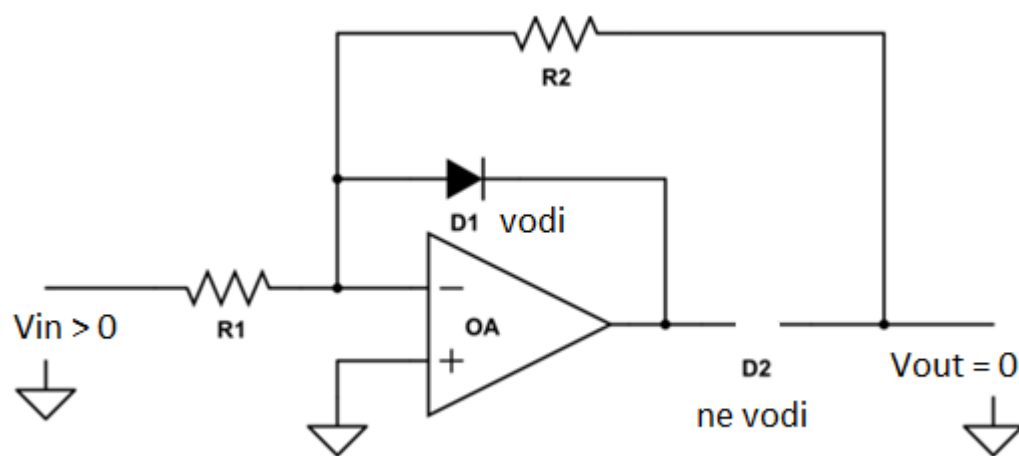Polutalasni usmerač sa dve diode (šema, prenosna funkcija i vremenski dijagrami)




$$v^+ = 0$$



$$v^- = 0^+ = 0 + \varepsilon, \varepsilon > 0, \varepsilon \rightarrow 0$$

$$v_{OA} = a(v^+ - v^-) = -av^- = -a\varepsilon < 0, a \rightarrow \infty$$

$$v_{OA} = -V_{D1} < 0$$

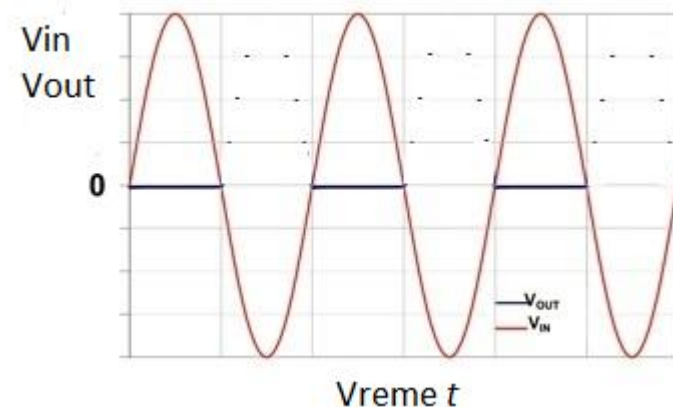

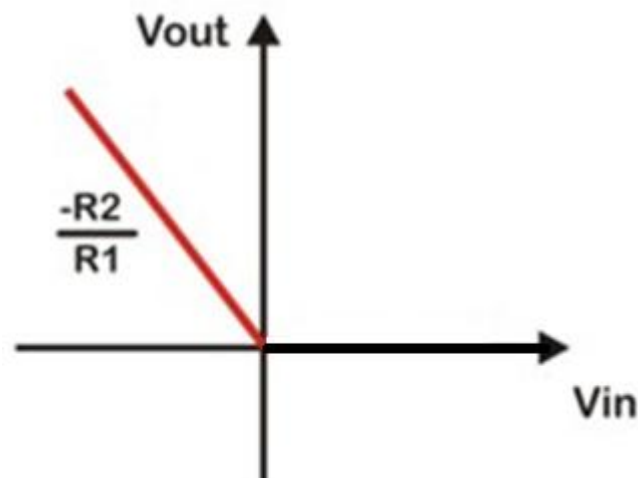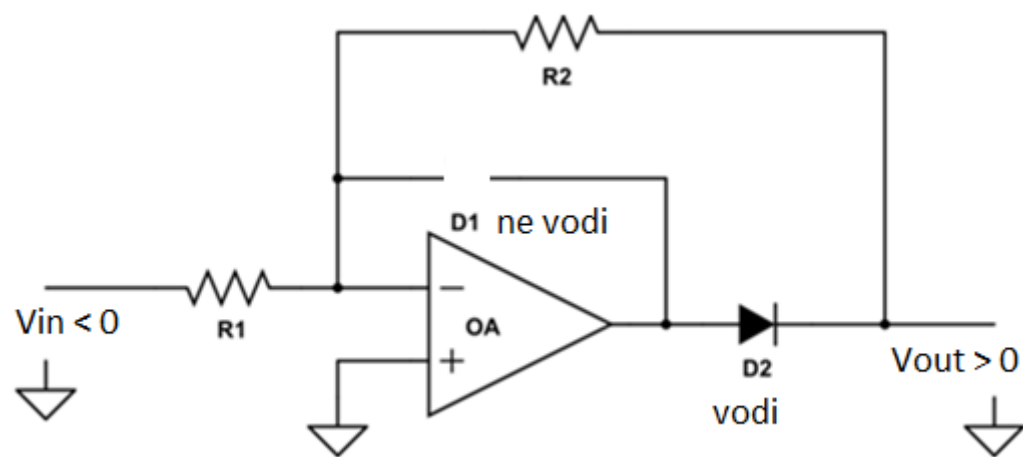Polutalasni usmerač sa dve diode (šema, prenosna funkcija i vremenski dijagrami)




$$v^+ = 0$$


$$v^- = 0^- = 0 - \varepsilon, \varepsilon > 0, \varepsilon \rightarrow 0$$

$$v_{OA} = a(v^+ - v^-) = -av^- = a\varepsilon > 0, a \rightarrow \infty$$
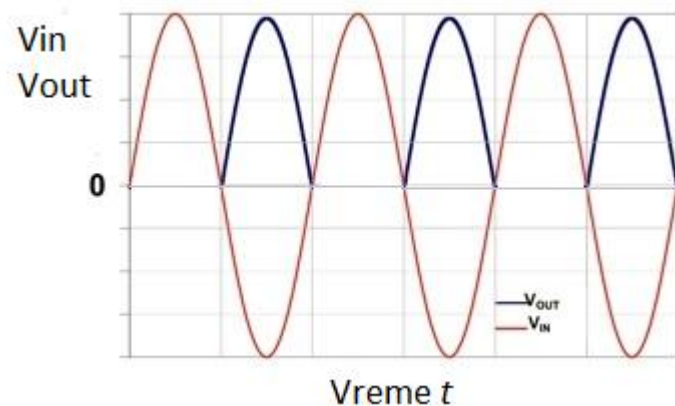
$$v_{OA} = V_{D2} - \frac{R_2}{R_1} V_{in} > 0$$



Punotalasni usmerač sa dve diode

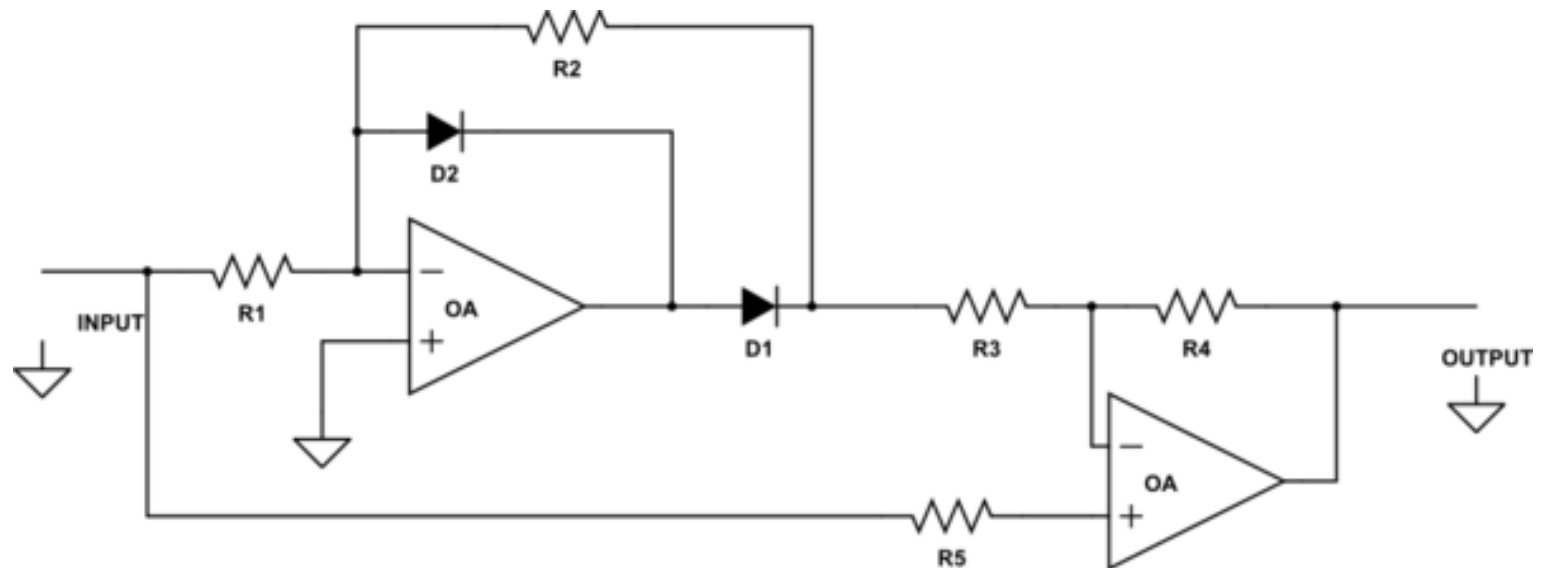

Osnovi analogne elektronike

IV semestar

**KOLA SA OPERACIONIM
POJAČAVAČIMA I NEGATIVNOM
POVRATNOM SPREGOM**