
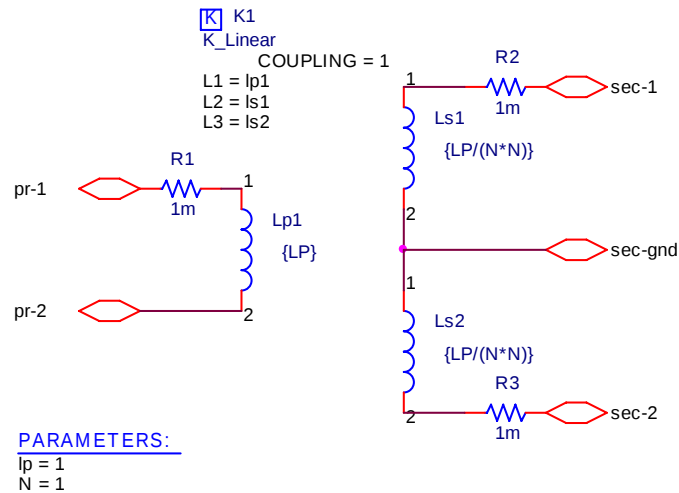



Create Subcircuit: Operational Amplifier

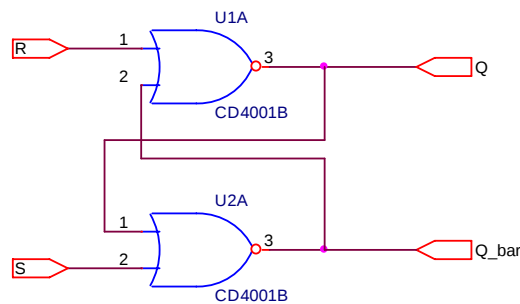

Create Subcircuit: Transformer



Create Subcircuit: SR Latch

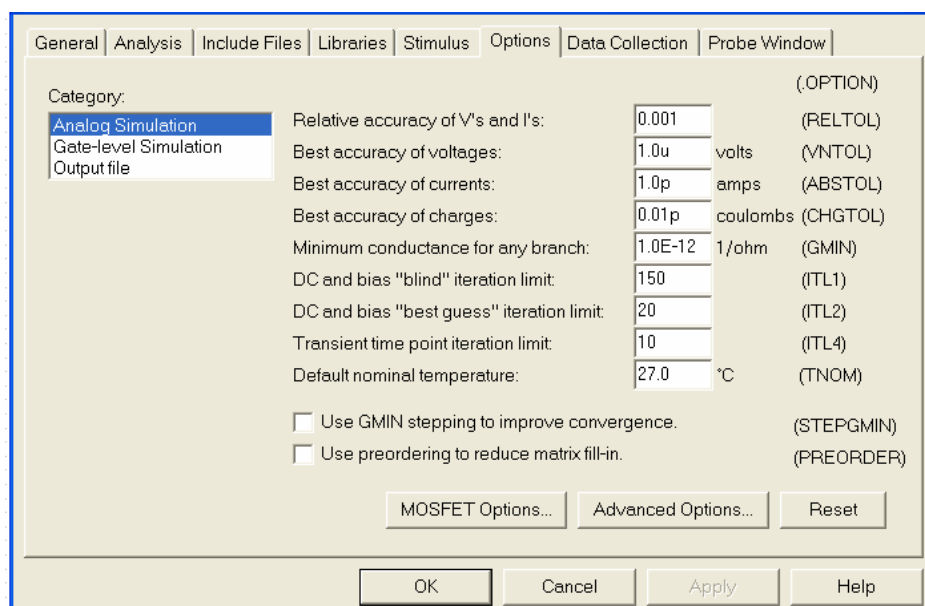

Convergence Problems: Options