

 


 

schematic2

 


schematic3




schematic1

 Kreiranje šeme za simulaciju pomoću hijerarhijskih blokova



 Simulacija digitalnih kola i uočavanje kašnjenja



Timer 555 i binarni brojac: Tran 40m (+7442a)