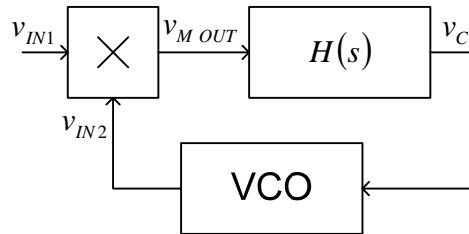


5. Na slici 5 je prikazan PLL kod koga je $v_{IN1} = 2 \text{ V} \sin(\omega_X t)$, $v_{IN2} = 2 \text{ V} \sin(\omega_X t - \varphi)$, $v_{M OUT} = (v_{IN1} v_{IN2}) / (0.5 \text{ V})$, $H(s) = 1 / (1 + (s / \omega_p))$, $f_{VCO} = 1 \text{ MHz} + 10(\text{kHz/V}) v_C$.

a) [4] Odrediti prenosnu karakteristiku faznog detektora $\overline{v_{M OUT}}(\varphi)$.

b) [6] Nacrtati vremenske dijagrame v_{IN1} , v_{IN2} , $v_{M OUT}$ i v_C za $v_{IN1} = 2 \text{ V} \sin(2\pi(1020 \text{ kHz})t)$.


Smatrati $\omega_p \ll \omega_X$.




Slika 5

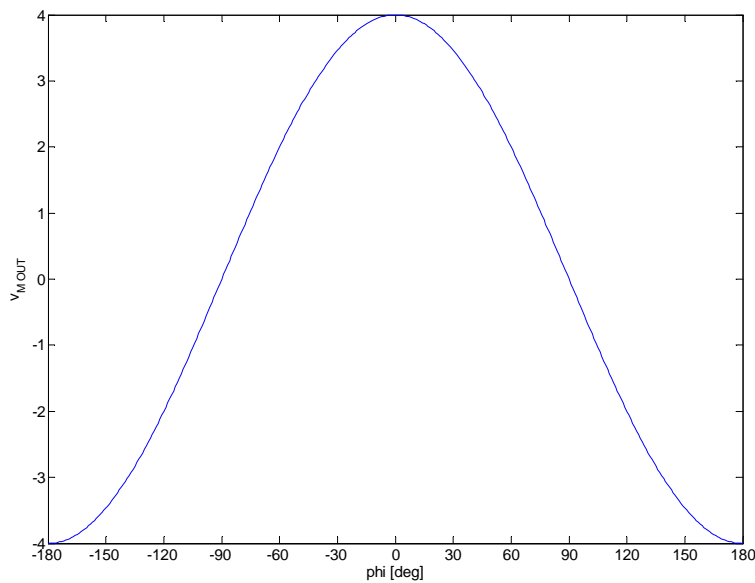a)
$$v_{M OUT} = 8 \text{ V} \sin(\omega_X t) \sin(\omega_X t - \varphi) = 4 \text{ V} (\cos(\varphi) - \cos(2\omega_X t - \varphi))$$

$$\overline{v_{M OUT}} = 4 \text{ V} \cos(\varphi)$$



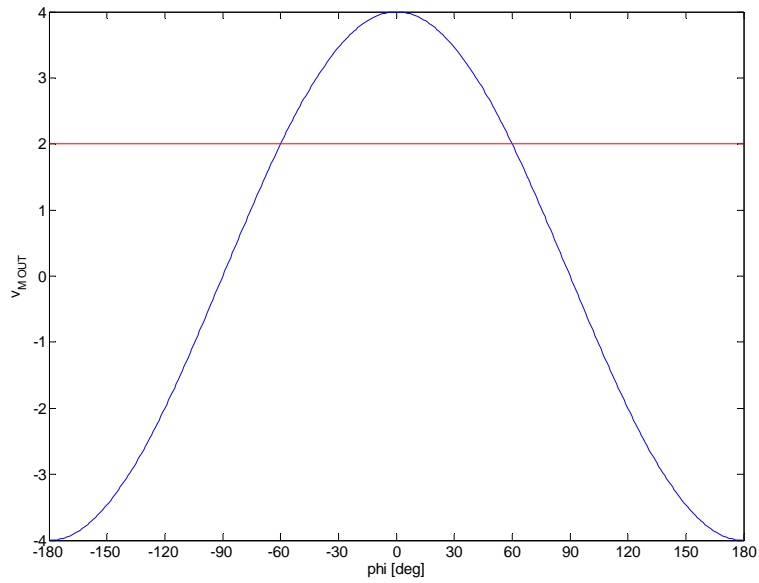b) $1020 \text{ kHz} = 1000 \text{ kHz} + 10(\text{kHz/V}) v_C$, $v_C = 2 \text{ V}$
 $2 \text{ V} = 4 \text{ V} \cos(\varphi)$, $\cos(\varphi) = 1/2$, $\varphi_1 = -60^\circ$, $\varphi_2 = 60^\circ$



nas zanima stabilno rešenje; $\alpha = \omega_x t$, $\beta = \omega_x t - \varphi$, $\varphi = \alpha - \beta$; $v_C \uparrow$, $\omega_{VCO} \uparrow$, $\beta \uparrow$, $\varphi \downarrow$, treba da dovede do $v_{MOUT} \downarrow$ da bi $v_C \downarrow$; $\varphi = -60^\circ$

