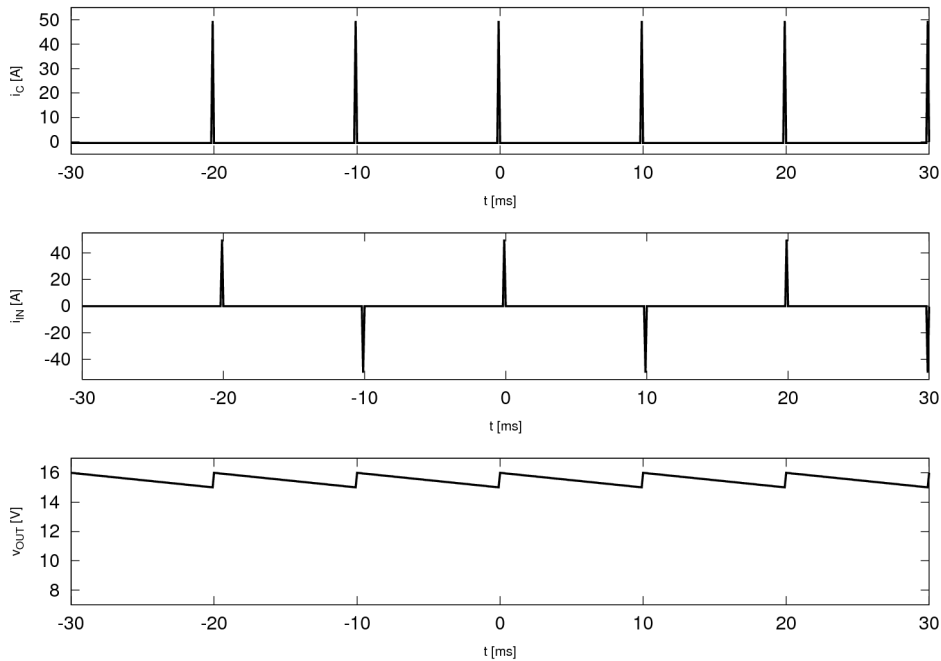


3.


$$a) V_{OUT} + 2V_D = \frac{V_{RMS} \sqrt{2}}{n}, \quad 16V + 2 \cdot 1V = \frac{220V \sqrt{2}}{n}, \quad n = 17.28$$

$$b) V_{OUT} = 16V - \frac{1}{4f_0 C} I_{OUT}, \quad \frac{1A}{4 \cdot 50Hz \cdot C} = 1V, \quad C = 5mF$$

$$c) Q = 10ms \cdot 0.5A = 5mC, \quad d), \quad Q_{IN} = Q/n = 289\mu C, \quad e)$$



pazite kod i_C , detaljnije:

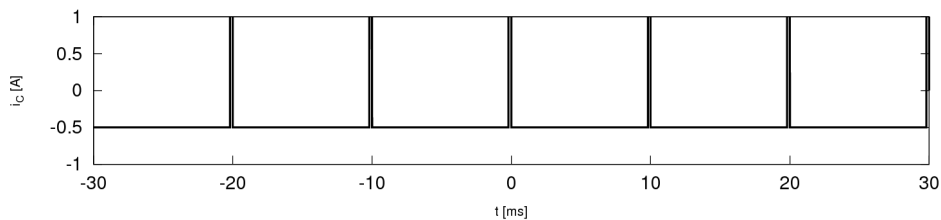

$$f) \gamma = \frac{1}{\sqrt{3}} \cdot \frac{\Delta v_{OUT}}{V_{OUT}}, \quad \gamma = \frac{1}{\sqrt{3}} \cdot \frac{0.5V}{15.5V}, \quad \gamma = 1.86\%$$

$$g) P_D = \frac{1}{2} V_D I_{OUT}, \quad P_D = 0.5W$$

$$h) \eta = \frac{P_{OUT}}{P_{IN}} = \frac{P_{OUT}}{P_{OUT} + 4P_D}, \quad \eta = \frac{15W}{17W} = 88.23\%$$