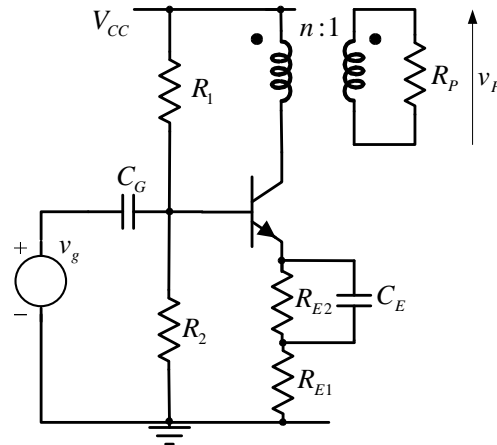


2. Na slici 2 je prikazan pojačavač snage u klasi A. Poznato je: $R_1 = 111 \Omega$, $R_2 = 39 \Omega$, $R_{E1} = 1 \Omega$, $R_{E2} = 7 \Omega$, $R_P = 4 \Omega$, $V_{CC} = 15 \text{ V}$, $\beta_F = 50$, $V_{BE} = 0.7 \text{ V}$, $V_{CES} = 0.5 \text{ V}$, $L_m \rightarrow \infty$, $C_G \rightarrow \infty$, $C_E \rightarrow \infty$, $n = 2$. Napon na izlazu je sinusnog talasnog oblika maksimalne moguće amplitude za zadate parametre.
- [3] Nacrtati jednosmernu i dinamičku radnu pravu pojačavača.
 - [10] Odrediti i nacrtati vremenske oblike napona v_p i v_{CE} , struja i_p i i_C , i snaga p_p , p_D i p_{CC} .
 - [3] Izračunati koeficijent korisnog dejstva pojačavača.
 - [4] Izvesti izraz za optimalnu vrednost parametra n , tako da se na izlazu dobija najveća moguća amplituda neizobličenog napona.



Slika 2

Rešenje:

a)

Jednosmerna radna prava:

$$V_{CEQ} = V_{CC} - (R_{E1} + R_{E2}) \frac{\beta + 1}{\beta} I_{CQ} = 15 - 8.16 I_{CQ}$$

Određivanje I_{CQ} i V_{CEQ} :

$$\frac{V_{CC} - V_B}{R_1} = \frac{V_B}{R_2} + I_B$$

$$I_E = \frac{V_B - V_{BE}}{R_{E1} + R_{E2}} = (1 + \beta_F) I_B$$

$$V_B = \frac{\frac{V_{BE}}{R_{E1} + R_{E2}} + \frac{(1 + \beta_F) V_{CC}}{R_1}}{\frac{1}{R_{E1} + R_{E2}} + \frac{1 + \beta_F}{R_1 \parallel R_2}} = 3.7 \text{ V}$$

$$V_E = V_B - V_{BE} = 3 \text{ V}$$

$$I_E = \frac{V_E}{R_E} = 375 \text{ mA}$$

$$I_{CQ} = \frac{\beta_F}{\beta_F + 1} I_E = 368 \text{ mA}$$

$$V_{CEQ} = V_{CC} - R_E I_{EQ} = 12\text{V}$$

Dinamička radna prava:

$$i_c = -\frac{v_{ce}}{n^2 R_p + R_{E1}}$$

$$i_c - I_{CQ} = -\frac{v_{CE} - V_{CEQ}}{n^2 R_p + R_{E1}}$$

$$i_c = I_{CQ} + \frac{V_{CEQ}}{n^2 R_p + R_{E1}} - \frac{v_{CE}}{n^2 R_p + R_{E1}} = 1.074 - \frac{v_{CE}}{17}$$

Uslov da se tranzistor ne isključi:


$$i_c > 0$$

$$I_{CQ} - \frac{v_{CE} - V_{CEQ}}{n^2 R_p + R_{E1}} > 0$$

$$v_{CE} < (n^2 R_p + R_{E1}) I_{CQ} + V_{CEQ}, \quad v_{CE \max} = 18.256 \text{ V}$$

$$V_{ce \max} = 6.256 \text{ V} (< V_{CEQ} - V_{CES}) - \text{ograničenje}$$

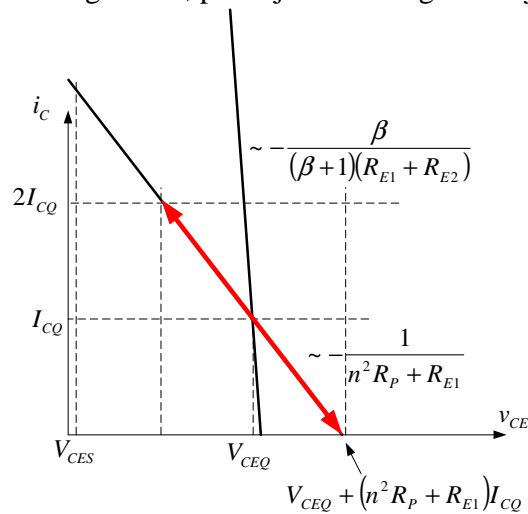Nema potrebe proveravati drugi uslov, pošto je uočeno ograničenje, i to usled isključenja.



$$V_p = \frac{1}{n} V_c = \frac{1}{n} \frac{n^2 R_p}{n^2 R_p + R_{E1}} V_{ce \max} = 2.944 \text{ V}$$

b)

$$v_p = V_p \sin \omega t = 2.944 \text{ V} \sin \omega t$$

$$v_{CE} = V_{CEQ} + v_{ce} = V_{CEQ} - \frac{n^2 R_p + R_{E1}}{n^2 R_p} v_c = V_{CEQ} - \frac{n^2 R_p + R_{E1}}{n^2 R_p} n v_p =$$

$$= V_{CEQ} - \frac{n^2 R_p + R_{E1}}{n^2 R_p} n V_p \sin \omega t = 12 \text{ V} - 6.256 \text{ V} \sin \omega t$$

$$i_p = \frac{v_p}{R_p} = \frac{V_p}{R_p} \sin \omega t = 0.736 \text{ A} \sin \omega t$$

$$i_C = I_{CQ} + \frac{i_p}{n} = I_{CQ} + \frac{1}{n} \frac{V_p}{R_p} \sin \omega t = 0.368 \text{ A}(1 + \sin \omega t)$$

$$p_p = \frac{v_p^2}{R_p} = \frac{V_p^2}{R_p} \sin^2 \omega t = 2.167 \text{ W} \sin^2 \omega t$$

$$\begin{aligned} p_D &= v_{CE} i_C + R_{E1} i_C^2 + R_{E2} I_{CQ}^2 = (v_{CE} + R_{E1} i_C) i_C + R_{E2} I_{CQ}^2 = \\ &= [(12 \text{ V} - 6.256 \text{ V} \sin \omega t) + (0.368 \text{ V}(1 + \sin \omega t))] 0.368 \text{ A}(1 + \sin \omega t) + 0.948 \text{ W} = \\ &= 0.368(12.368 - 5.888 \sin \omega t)(1 + \sin \omega t) \text{ W} + 0.948 \text{ W} = (5.50 + 2.38 \sin \omega t - 2.17 \sin^2 \omega t) \text{ W} \end{aligned}$$



$$p_D(0) = 5.50 \text{ W}, p_D\left(\frac{T}{8}\right) = 6.10 \text{ W}$$

$$p_D\left(\frac{T}{4}\right) = 5.71 \text{ W}, p_D\left(\frac{3T}{8}\right) = 6.10 \text{ W}$$

$$p_D\left(\frac{T}{2}\right) = 5.50 \text{ W}, p_D\left(\frac{5T}{8}\right) = 2.73 \text{ W}$$

$$p_D\left(\frac{3T}{4}\right) = 0.95 \text{ W}, p_D\left(\frac{7T}{8}\right) = 2.73 \text{ W}$$
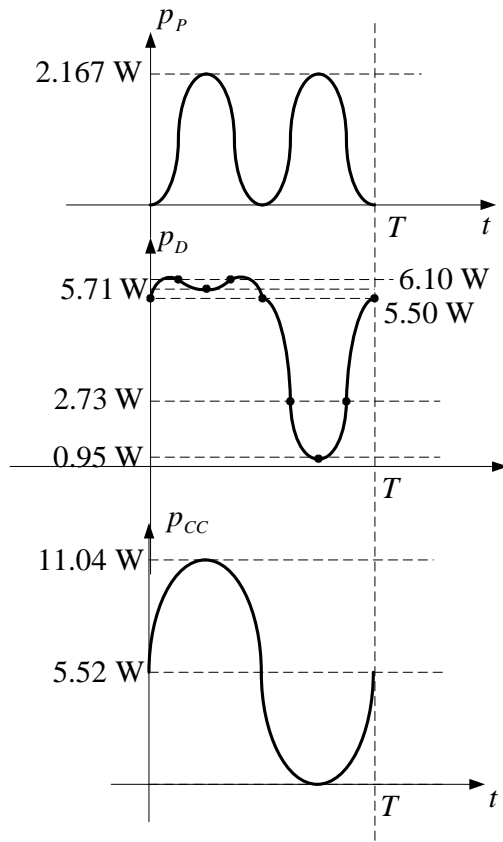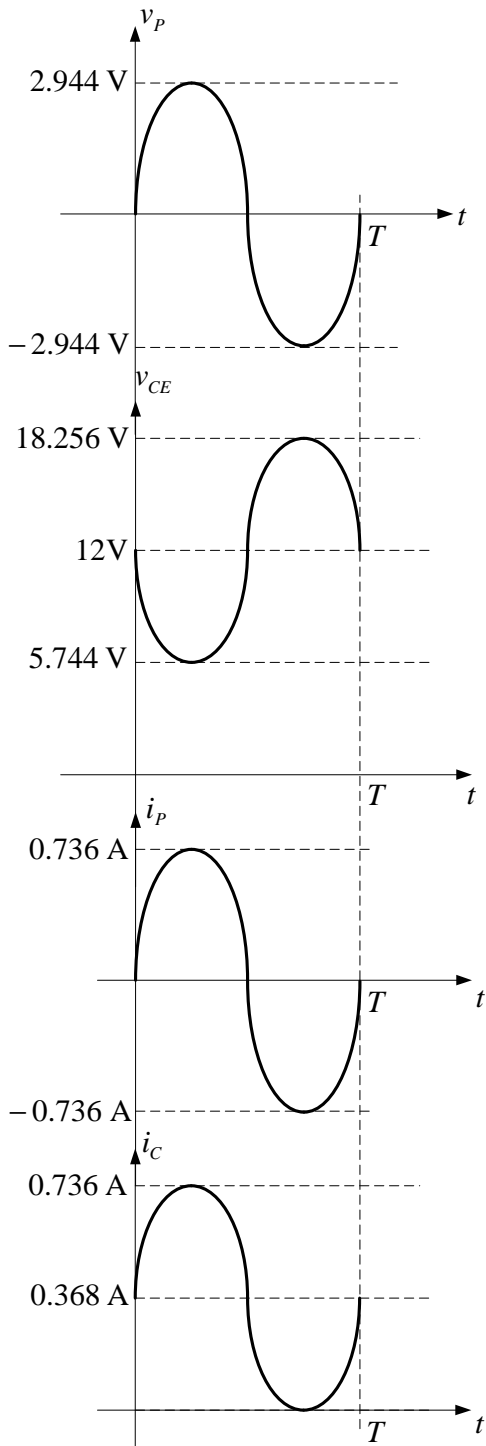
$$p_{CC} = V_{CC} i_C = 5.52 \text{ W}(1 + \sin \omega t)$$



c)

$$P_P = \overline{p_P} = \frac{V_P^2}{R_P} \overline{\sin^2 \omega t} = \frac{V_P^2}{2R_P} = 1.0835 \text{ W}$$

$$P_{CC} = \overline{p_{CC}} = V_{CC} \overline{i_C} = 5.52 \text{ W}$$

$$\eta = \frac{P_P}{P_{CC}} = 19.63\%$$

d)

Maksimalna amplituda neizobličenog napona dobija se kada se mirna radna tačka nalazi na polovini dinamičke radne prave, odnosno ako se istovremeno dostižu naponsko i strujno ograničenje:

$$i_{C \max} = 2I_{CQ} = I_{CQ} + \frac{V_{CEQ} - V_{CES}}{n^2 R_P + R_{E1}}$$

$$v_{CE \min} = V_{CES} = V_{CEQ} - (n^2 R_P + R_{E1}) I_{CQ}$$

$$n_{OPT} = \sqrt{\frac{V_{CC} - V_{CES} - R_{E1} \left(1 + \frac{\beta + 1}{\beta}\right) - R_{E2} \frac{\beta + 1}{\beta}}{R_P} I_{CQ}} = 2.75$$