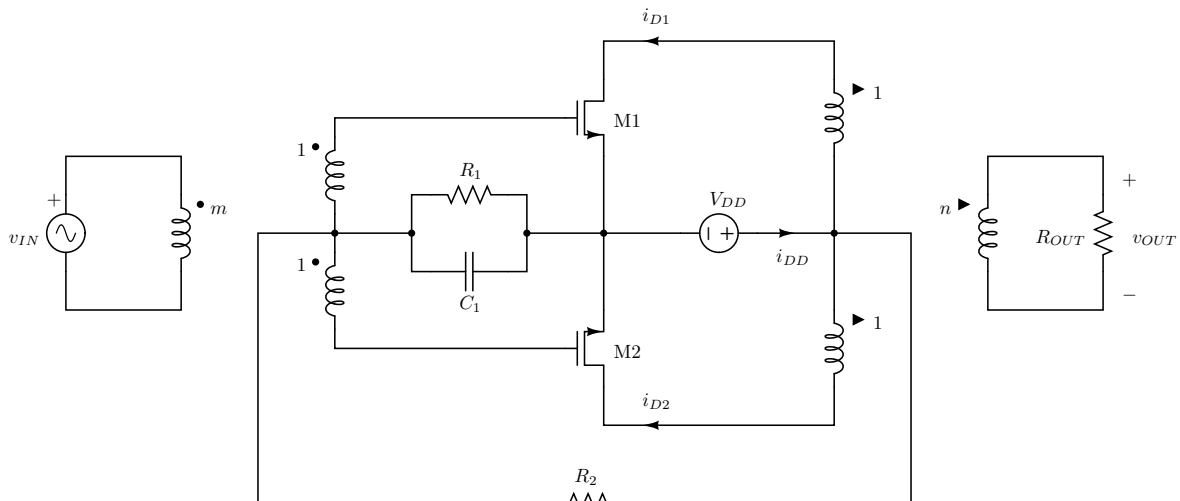


1. Na slici 1 je prikazan pojačavač snage u klasi A kod koga je  $V_{DD} = 12 \text{ V}$ ,  $m = 2$ ,  $R_1 = 10 \text{ k}\Omega$ ,  $R_2 = 30 \text{ k}\Omega$ ,  $C_1 \rightarrow \infty$ ,  $n = 5$ ,  $R_{OUT} = 625 \Omega$ , tranzistori su sa  $B = 200 \text{ mA/V}^2$ ,  $V_T = 2 \text{ V}$ .

- a) [2] Odrediti disipacije na tranzistorima u mirnoj radnoj tački,  $P_{D1Q}$  i  $P_{D2Q}$ .  
 b) [2] Odrediti prenosnu funkciju  $v_{OUT}(v_{IN})$  pod pretpostavkom da su tranzistori u zasićenju.

Za  $v_{IN} = 2 \text{ V} \sin(\omega t)$ :

- c) [2] Odrediti vremenske dijagrame  $v_{GS1}$ ,  $v_{GS2}$ ,  $v_{DS1}$ ,  $v_{DS2}$  i  $v_{OUT}$ .  
 d) [2] Odrediti vremenske dijagrame  $i_{D1}$ ,  $i_{D2}$ , i  $i_{DD}$ .  
 e) [2] Odrediti koeficijent korisnog dejstva  $\eta$ .



Slika 1.

### REŠENJE:

- a) [2]

$$V_{GS1Q} = V_{GS2Q} = V_{GSQ} = \frac{R_1}{R_1 + R_2} V_{DD} = \frac{10 \text{ k}\Omega}{10 \text{ k}\Omega + 30 \text{ k}\Omega} 12 \text{ V} = 3 \text{ V}$$

$$I_{D1Q} = I_{D2Q} = \frac{B}{2} (V_{GSQ} - V_T)^2 = 100 \frac{\text{mA}}{\text{V}^2} (3 \text{ V} - 2 \text{ V})^2 = 100 \text{ mA}$$

$$P_{D1Q} = P_{D2Q} = V_{DD} I_{DQ} = 1.2 \text{ W}$$

- b) [2]

$$v_{GS1} = V_{GSQ} + \frac{v_{IN}}{m}$$

$$v_{GS2} = V_{GSQ} - \frac{v_{IN}}{m}$$

$$i_{D1} = \frac{B}{2} (v_{GS1} - V_T)^2 = \frac{B}{2} \left( V_{GSQ} - V_T + \frac{v_{IN}}{m} \right)^2$$

$$i_{D2} = \frac{B}{2} (v_{GS2} - V_T)^2 = \frac{B}{2} \left( V_{GSQ} - V_T - \frac{v_{IN}}{m} \right)^2$$

$$n i_{OUT} = n \frac{v_{OUT}}{R_{OUT}} = i_{D2} - i_{D1}$$

$$v_{OUT} = \frac{R_{OUT}}{n} (i_{D2} - i_{D1})$$

$$v_{OUT} = -\frac{2BR_{OUT}}{nm} (V_{GSQ} - V_T) v_{IN} = -25 v_{IN}$$

c) [2] (slike na kraju)

$$v_{GS1} = V_{GSQ} + \frac{v_{IN}}{m} = 3 \text{ V} + 1 \text{ V} \sin(\omega t)$$

$$v_{GS2} = V_{GSQ} - \frac{v_{IN}}{m} = 3 \text{ V} - 1 \text{ V} \sin(\omega t)$$

$$v_{OUT} = -25 v_{IN} = -50 \text{ V} \sin(\omega t)$$

$$v_{DS1} = V_{DD} + \frac{v_{OUT}}{n} = 12 \text{ V} - 10 \text{ V} \sin(\omega t)$$

$$v_{DS2} = V_{DD} - \frac{v_{OUT}}{n} = 12 \text{ V} + 10 \text{ V} \sin(\omega t)$$

d) [2] (slike na kraju)

$$i_{D1} = \frac{B}{2} \left( V_{GSQ} - V_T + \frac{v_{IN}}{m} \right)^2 = 100 \text{ mA} (1 + \sin(\omega t))^2$$

$$i_{D2} = \frac{B}{2} \left( V_{GSQ} - V_T - \frac{v_{IN}}{m} \right)^2 = 100 \text{ mA} (1 - \sin(\omega t))^2$$

$$i_{DD} = i_{D1} + i_{D2} = 200 \text{ mA} (1 + \sin^2(\omega t)) = 300 \text{ mA} - 100 \text{ mA} \cos(2\omega t)$$

gornji rezultat je dobijen uz zanemarivanje struje razdelnika  $\frac{V_{DD}}{R_1 + R_2} = 0.3 \text{ mA}$

e) [2]

$$\eta = \frac{P_{OUT}}{P_{DD}}$$

$$P_{OUT} = \frac{V_{OUTm}^2}{2R_{OUT}} = \frac{(50 \text{ V})^2}{2 \times 625 \Omega} = 2 \text{ W}$$

$$P_{DD} = V_{DD} \overline{i_{DD}} = 12 \text{ V} \times 300 \text{ mA} = 3.6 \text{ W}$$

$$\eta = \frac{2 \text{ W}}{3.6 \text{ W}} = \frac{5}{9} = 55.56\%$$

