

$$t_1 = \frac{T}{4} + \sqrt{\left(\frac{L}{R}\right)^2 + \left(\frac{T}{4}\right)^2} - \frac{L}{R}$$


$$t_1 = 31\mu\text{s}$$

$$v_p(t_1) = 10\text{V}\Delta(t_1) = -2.36\text{V}$$

Tranzistor Q_1 se ponovo uključuje kada ponovo postane $i_p > 0$, odnosno (zbog simetrije)

$$t_2 = \frac{T}{2} + t_1 = 81\mu\text{s}$$
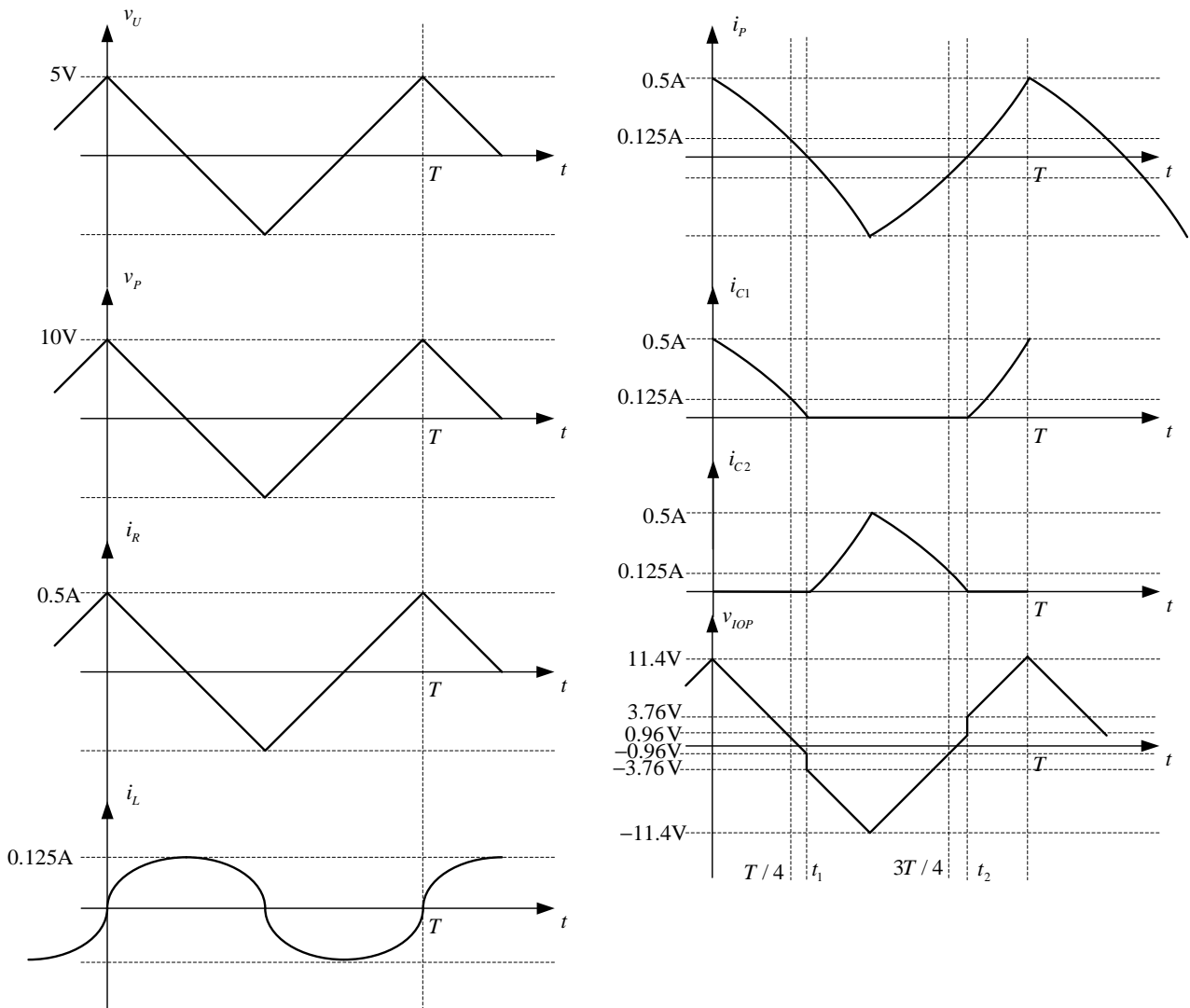
$$v_{IOP} = \begin{cases} v_p + 2V_{BE} = 10\text{V}\Delta(t) + 1.4\text{V} & i_p > 0 \\ v_p - 2V_{BE} = 10\text{V}\Delta(t) - 1.4\text{V} & i_p < 0 \end{cases}$$



b)

$$P_{D1} = v_{CE1} i_{C1} = \begin{cases} (V_{CC} - v_P) i_P, & i_P > 0 \\ 0, & i_P \leq 0 \end{cases}$$

$$\begin{aligned} P_{D1} &= \frac{1}{T} \int_{nT}^{nT+t_1} (V_{CC} - v_P) i_P dt + \frac{1}{T} \int_{t_2}^{(n+1)T} (V_{CC} - v_P) i_P dt = \\ &= \frac{1}{T} \int_{nT}^{nT+t_1} (15 - 10V\Delta(t)) (0.5A\Delta(t) + 0.125A(1 - \Delta^2(t))\Pi(t)) dt + \\ &+ \frac{1}{T} \int_{nT+t_2}^{(n+1)T} (15 - 10V\Delta(t)) (0.5A\Delta(t) + 0.125A(1 - \Delta^2(t))\Pi(t)) dt \\ P_{D1} &= \frac{1}{T} \int_{nT}^{nT+t_1} (15 - 10V\Delta(t)) (0.5A\Delta(t) + 0.125A(1 - \Delta^2(t))) dt + \\ &+ \frac{1}{T} \int_{nT+t_2}^{(n+1)T} (15 - 10V\Delta(t)) (0.5A\Delta(t) - 0.125A(1 - \Delta^2(t))) dt \end{aligned}$$

$$\begin{aligned} P_{D1} &= \frac{1}{T} \int_0^{t_1} \left(15 - 10 \left(1 - 4 \frac{t}{T} \right) \right) \left(0.5A \left(1 - 4 \frac{t}{T} \right) + 0.125A \left(1 - \left(1 - 4 \frac{t}{T} \right)^2 \right) \right) dt + \\ &+ \frac{1}{T} \int_{t_2}^T \left(15 - 10V \left(-3 + 4 \frac{t}{T} \right) \right) \left(0.5A \left(-3 + 4 \frac{t}{T} \right) - 0.125A \left(1 - \left(-3 + 4 \frac{t}{T} \right)^2 \right) \right) dt \end{aligned}$$

Smena $u = \frac{t}{T}$:

$$\begin{aligned} P_{D1} &= \int_0^{t_1/T} (15 - 10(1 - 4u)) (0.5A(1 - 4u) + 0.125A(1 - (1 - 4u)^2)) du + \\ &+ \int_{t_2/T}^1 (15 - 10(-3 + 4u)) (0.5A(-3 + 4u) - 0.125A(1 - (-3 + 4u)^2)) du = \\ &= \int_0^{t_1/T} (5 + 40u)(0.5 - u - 2u^2) du + \int_{t_2/T}^1 (45 - 40u)(-0.5 - u + 2u^2) du = \dots = 1.15 \text{ W} \end{aligned}$$

c)

naponsko ograničenje izlaza operacionog pojačavača: $V_{u\max} = \frac{V_{CC} - 2V_{BE}}{2} = 6.8 \text{ V}$

strujno ograničenje se javlja kada je $i_{P\max} = (1 + \beta_{FP})^2 i_{OP\max} = 4.805 \text{ A}$ (gledamo i_{C2} , zbog manjeg strujnog pojačanja pnp tranzistora)

Da li je maksimalna jačina struje kroz potrošač $\frac{2V_u}{R}$, kako se čini sa **skiciranog** dijagrama?

$$i_P = \frac{2V_u}{R} \Delta(t) + \frac{V_u T}{4L} (1 - \Delta^2(t)) \Pi(t)$$

Posmatramo prvu poluperiodu, kada je $\Pi(t) = 1$, $\Delta(t) = 1 - 4 \frac{t}{T}$

$$i_P = \frac{2V_u}{R} \Delta(t) + \frac{V_u T}{4L} (1 - \Delta^2(t))$$

Pitanje je da li ova funkcija ima maksimum na intervalu $(0, t_1)$?

$$\frac{di_p}{dt} = \frac{2V_u}{R} \Delta'(t) - \frac{2V_u T}{4L} \Delta(t) \Delta'(t) = 0$$

$$\frac{d^2 i_p}{dt^2} = -\frac{2V_u T}{4L} (\Delta'(t))^2 < 0$$

Kako je drugi izvod uvek negativan, funkcija može imati samo maksimum.

$$\frac{1}{R} - \frac{T}{4L} \Delta(t) = 0$$

$$\Delta(t) = \frac{4L}{RT}, \quad 1 - 4 \frac{t}{T} = \frac{4L}{RT}$$

$$t = \frac{T}{4} - \frac{L}{R}$$

Da bi postojao maksimum na intervalu, mora biti $t_1 > t > 0$, odakle se dobija

$$T > \frac{4L}{R} = 200 \mu s$$

Minimum struje potrošača (maksimum struje tranzistora Q_2) je odavde


$$i_{p_{\max}} = \begin{cases} \frac{V_u}{L} \left(\left(\frac{L}{R} \right)^2 \frac{4}{T} + \frac{T}{4} \right) & T > 200 \mu s \\ \frac{2V_u}{R} & T < 200 \mu s \end{cases}$$

$$V_u = \begin{cases} \frac{i_{p_{\max}} L}{\left(\frac{L}{R} \right)^2 \frac{4}{T} + \frac{T}{4}} & T > 200 \mu s \\ \frac{R i_{p_{\max}}}{2} = 48.05 V & T < 200 \mu s \end{cases}$$

Uzima se strožiji od dva uslova. Za male vrednosti T to je naponsko, za velike strujno, granična vrednost periode se određuje na osnovu jednačine

$$\frac{i_{p_{\max}} L}{\left(\frac{L}{R} \right)^2 \frac{4}{T} + \frac{T}{4}} = 6.8 V, \quad T = 2.8 ms.$$
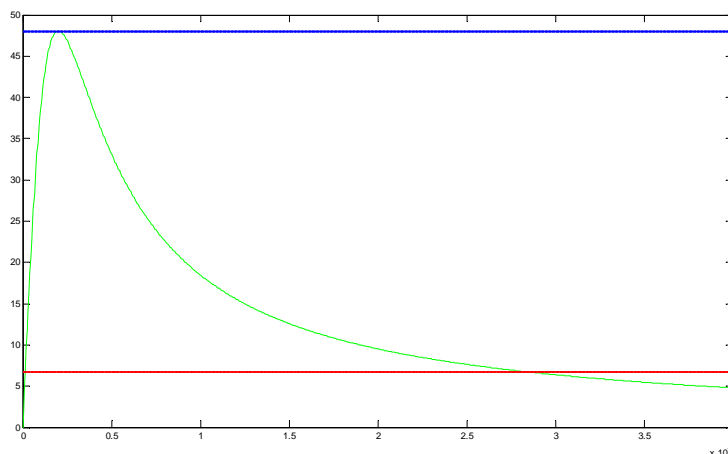
$$V_u = \begin{cases} 6.8 V & T < 2.8 ms \\ \frac{i_{p_{\max}} L}{\left(\frac{L}{R} \right)^2 \frac{4}{T} + \frac{T}{4}} & T > 2.8 ms \end{cases}$$



d)

$$\begin{aligned}
 P_{D1} &= \frac{1}{T} \left(\int_0^{T/4} (V_{CC} - v_P) i_R dt + \int_{3T/4}^T (V_{CC} - v_P) i_R dt \right) \\
 P_{D1} &= \frac{1}{T} \left(\int_0^{T/4} (V_{CC} - 2V_u \Delta(t)) \left(\frac{2V_u}{R} \Delta(t) \right) dt + \int_{3T/4}^T (V_{CC} - 2V_u \Delta(t)) \left(\frac{2V_u}{R} \Delta(t) \right) dt \right) = \\
 &= \frac{1}{T} \left(V_{CC} \frac{2V_u}{R} \left(\int_0^{T/4} \Delta(t) dt + \int_{3T/4}^T \Delta(t) dt \right) - \frac{4V_u^2}{R} \left(\int_0^{T/4} \Delta^2(t) dt + \int_{3T/4}^T \Delta^2(t) dt \right) \right) \\
 P_{D1} &= \frac{1}{T} \left(7.5 \text{ W} \left(\int_0^{T/4} \Delta(t) dt + \int_{3T/4}^T \Delta(t) dt \right) - 5 \text{ W} \left(\int_0^{T/4} \Delta^2(t) dt + \int_{3T/4}^T \Delta^2(t) dt \right) \right) = \dots
 \end{aligned}$$

Može direktno, ali može i... Zakon o održanju energije:

$$\begin{aligned}
 P_{D1} &= \frac{2P_{CC} - P_{OUT}}{2} \\
 P_{CC} &= V_{CC} I_{C1} = V_{CC} \overline{i_{C1}} = \dots = \langle \text{sa slike} \rangle = V_{CC} \frac{2V_u}{4R} = \frac{V_{CC}}{2R} V_u \\
 P_{OUT} &= \frac{\overline{v_P^2}}{R} = \frac{(2V_u)^2 \overline{\Delta^2(t)}}{R} = \frac{4V_u^2}{3R} \\
 P_{D1} &= \frac{2 \frac{V_{CC}}{2R} V_u - \frac{4}{3R} V_u^2}{2} = \frac{V_{CC}}{2R} V_u - \frac{2}{3R} V_u^2 = \frac{1}{R} V_u \left(\frac{V_{CC}}{2} - \frac{2V_u}{3} \right)
 \end{aligned}$$

Maksimum ove funkcije...

$$\begin{aligned}
 \frac{dP_{D1}}{dV_u} &= \frac{V_{CC}}{2R} - \frac{4V_u}{3R} = 0 \\
 V_u &= \frac{3V_{CC}}{8} = 5.625 \text{ V} \\
 P_{D1\max} &= 1.05 \text{ W}
 \end{aligned}$$