
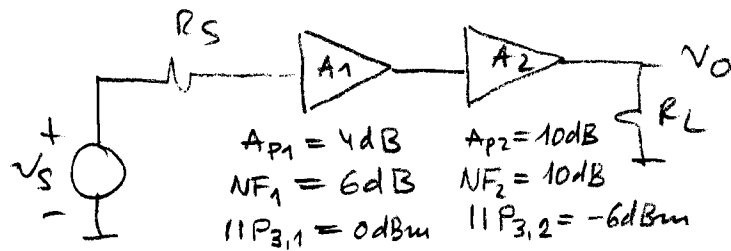


(2)

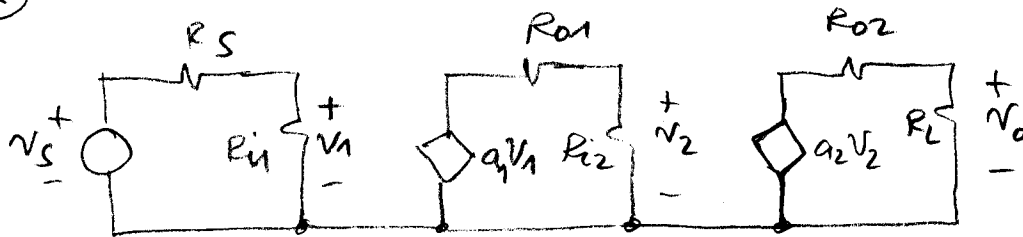

Smatrajući da su pojačavači prilagođeni odrediti NF , A_p , IIP_3 .

(R)



$$R_{i1} = R_S, R_{i2} = R_{o1}, R_L = R_{o2}$$

$$P_O = \frac{V_O^2}{R_L} = \frac{1}{R_L} a_1^2 \cdot \frac{1}{4} \cdot a_2^2 \cdot \frac{1}{4} \cdot \frac{V_S^2}{4}$$

$$A_{p1} = \frac{P_{o1}}{P_{in}} = \frac{\frac{1}{4} (a_1 V_1)^2 / R_{i2}}{\frac{1}{4} V_S^2 / R_{i1}} = \frac{\frac{1}{4} a_1^2 \cdot \frac{1}{4} V_S^2 / R_{i2}}{\frac{1}{4} V_S^2 / R_{i1}} = \frac{1}{4} a_1^2 \cdot \frac{R_{i1}}{R_{i2}} = \frac{1}{4} a_1^2$$

$$A_p = A_{p1} \cdot A_{p2} = \frac{a_1^2}{4} \cdot \frac{a_2^2}{4}$$

$$a_p = A_{p1} [dB] + A_{p2} [dB] = 14 dB$$

$$NF_1 = 6 dB \Rightarrow F_1 = 10^{0.6} = 3.98$$

$$NF_2 = 10 dB \Rightarrow F_2 = 10^1 = 10$$

Frissova j-na

$$F = 1 + (F_1 - 1) + \frac{F_2 - 1}{A_{p1}}, A_{p1} = 10^{0.4} = 2.51$$

$$F = 7.57 \Rightarrow NF = 10 \log F = 8.79 dB$$

$$\frac{1}{IIP_3^2} = \frac{1}{IIP_{3,1}^2} + \frac{a_1^2}{IIP_{3,2}^2}$$

$$\frac{a_1^2}{4} = 4 dB \Rightarrow a_1 = 3.17$$

$$IIP_{3,1} = 0 dBm \Rightarrow 10 \log \frac{V_{rms1}^2 / 50}{1 mW} = 0 \Rightarrow V_{rms}^2 = 50 \cdot 10^{-3} V^2$$

$$IIP_{3,2} = -6 dBm \Rightarrow V_{rms2}^2 = 12.5 \cdot 10^{-3} V^2$$

$$\frac{1}{IIP_3^2} = \frac{1}{50 \cdot 10^{-3}} + \frac{10}{12.5 \cdot 10^{-3}} \Rightarrow IIP_3 = 34.9 \cdot 10^{-3} V$$


$$\Rightarrow IIP_3 = 10 \log \frac{IIP_3^2 / 50}{1 mW} = -16 dBm$$

- ⑦ a) Na ulaz jednog RF pojačavača se dovodi signal osnovne učestanosti snage -30 dBm . Tada se na njegovom izlazu dobije signal na osnovnoj učestanosti, čije je snage -10 dBm . Kada se na ulaz istog pojačavača dovedu dva tona čije su snage -30 dBm , na izlazu se dobije 1 MHz komponenta čija je snaga -70 dBm .

a1) odrediti pojačanje snage RF pojačavača

a2) odrediti IIP_3 .

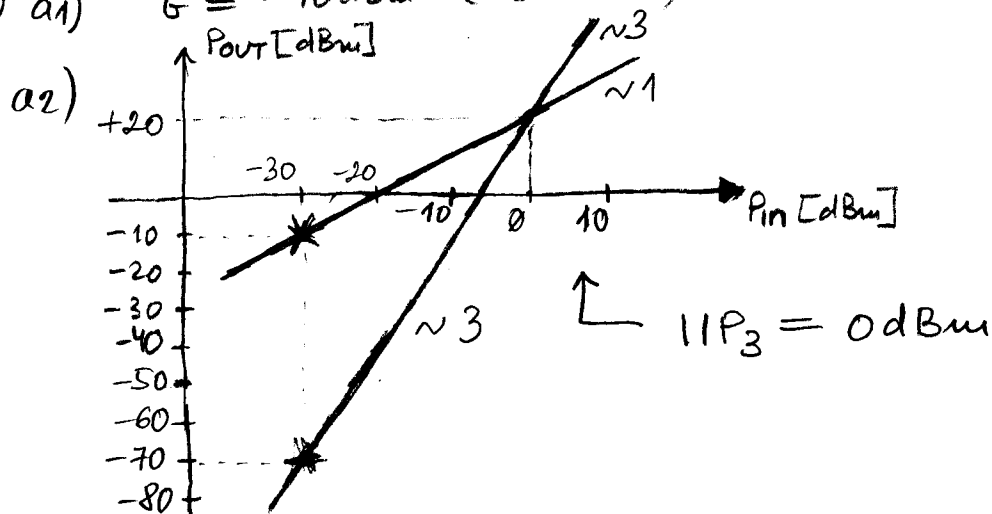⑧ a1) $G = -10\text{ dBm} - (-30\text{ dBm}) = 20\text{ dB}$



- ⑦ b) Ako je propusni opseg pojačavača 10 MHz i faktor šuma 14 dB , odrediti minimalni signal koji se može detektovati na ulazu pojačavača MDS

c) odrediti SFDR (Spurious Free Dynamic Range)

⑧ b) $P_S = P_N \Rightarrow P_{\text{MDS}} = 10 \log(kTB) + NF$

$$P_{\text{MDS}} = -174 \frac{\text{dBm}}{\text{Hz}} + 10 \log(B) + NF$$


$$P_{\text{MDS}} = -174 + 70 + 14 = -90\text{ dBm}$$

Šum na izlazu $P_{\text{out}} = G \cdot P_{\text{in}} = -90\text{ dBm} + 20\text{ dB} = -70\text{ dBm}$

c) Pošto je nivo šuma na izlazu -70 dBm to je

$$\text{SFDR} = -10\text{ dBm} - (-70\text{ dBm}) = \underline{\underline{60\text{ dB}}}$$

(Z)

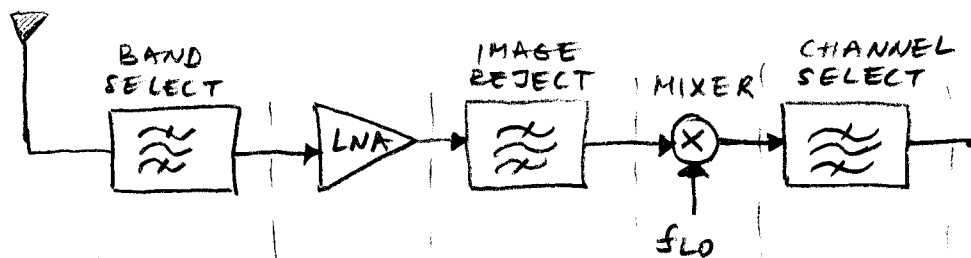

NF [dB]	0	3	0	10	0
POJAČANJE SNAGE [dB]	-3	20	-3	10	-3

Na slici je prikazan blok šema FRONT-END dela jednog RF prijemnika, a pored svakog dela prijemnika dat je njegov faktor šuma i pojačanje snage. Poznato je $f_{RF} = 900 \text{ MHz}$, $f_{LO} = 850 \text{ MHz}$.

- odrediti međufrekventnu učestanost f_{IF}
- odrediti Q -faktor filtra za selektovanje kanala koji zauzimaju propusni opseg 2 MHz
- odrediti faktor šuma prijemnika NF .

(R)

a) $f_{IF} = f_{RF} - f_{LO} = 50 \text{ MHz}$

b) $Q = \frac{f_0}{\Delta f} = \frac{f_{IF}}{\Delta f} = \frac{50 \text{ MHz}}{2 \text{ MHz}} = 25$

c) Friisova j-na

$$F_{TOT} = 1 + F_1 - 1 + \frac{F_2 - 1}{G_1} + \frac{F_3 - 1}{G_1 G_2} + \frac{F_4 - 1}{G_1 G_2 G_3} + \frac{F_5 - 1}{G_1 G_2 G_3 G_4}$$

	BS	LNA	IR	MIX	CS
N	1	2	3	4	5
F	1	2	1	10	1
G	1/2	100	1/2	10	1/2

$$NF = 10 \log F$$


$$G[\text{dB}] = 10 \log G$$

$$F_{TOT} = 1 + (1-1) + \frac{2-1}{1/2} + \frac{1-1}{\frac{1}{2} \cdot 100} + \frac{10-1}{\frac{1}{2} \cdot \frac{1}{2} \cdot 100} + \frac{1-1}{\frac{1}{2} \cdot \frac{1}{2} \cdot 100 \cdot 10}$$

$$F_{TOT} = 1 + 0 + 2 + 0 + \frac{36}{100} + 0 = 3.36$$

$$NF = 10 \log F_{TOT} = 5.26 \text{ dB}.$$

②

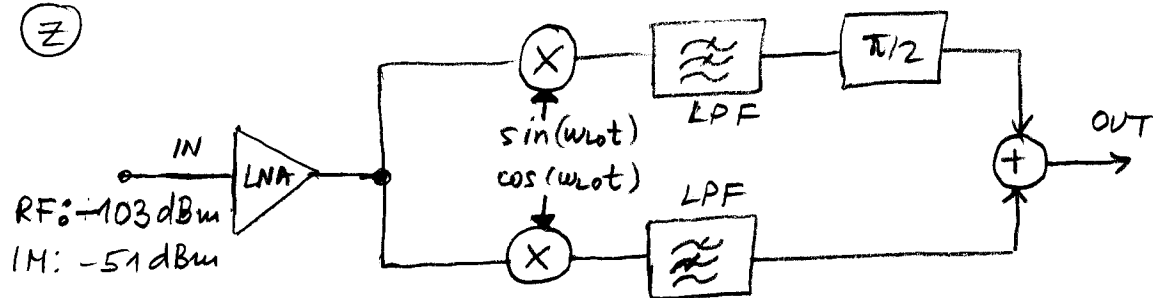

Hartleyeva arhitektura za potiskivanje simetrične f .
 Prihvatljiv nivo interferirajoče komponente na simetrični
 učestanosti na izlazu je $P_{OUTIM} = P_{OUTRF} + 12\text{dB}$.
 Ako je pojačanje od ulaza do izlaza $A_{IN-OUT} = 50\text{dB}$, odrediti
 potrebni faktor potiskivanja simetrične učestanosti IRR .

③ Bez potiskivanja simetrične učestanosti je

$$P_{RFOUT} = -103\text{dBm} + 50\text{dB} = -53\text{dBm}$$

$$P_{IMOUT} = -51\text{dBm} + 50\text{dB} = -1\text{dBm}$$


Prihvatljiv nivo IM smetnji je

$$P_{IM,ACC} = P_{RFOUT} + 12\text{dB} = -41\text{dBm}$$

Faktor potiskivanja mora biti veći od

$$IRR = -1\text{dBm} - (-41\text{dBm}) = \underline{\underline{40\text{dB}}}$$

(Z)

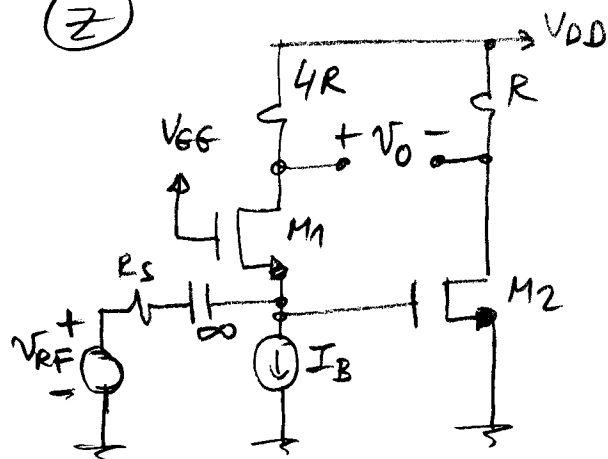

U širokopojasnom pojačavaču sa slike je $g_{m2} = 4g_{m1}$

- odrediti g_{m1} tako da se ostvari prilagođenje po snazi
- odrediti naponsko pojačanje u propusnom opsegu
- odrediti faktor šuma $F(NF)$

Razmatrati samo uticaj termičkog šuma.

(R)


$$a) R_S = \frac{1}{g_{m1}} \Rightarrow g_{m1} = \frac{1}{R_S}$$

$$b) V_{S1} = \frac{\frac{1}{g_{m1}}}{\frac{1}{g_{m1}} + R_S} V_{RF} = \frac{V_{RF}}{2}$$

$$V_O = V_{d1} - V_{d2} = 4R \cdot g_{m1} \cdot \frac{V_{RF}}{2} - R(-g_{m2} \frac{V_{RF}}{2})$$

$$V_O = 8R g_{m1} \frac{V_{RF}}{2} \Rightarrow A_V = \frac{V_O}{V_{RF}} = 4R g_{m1}$$

c)

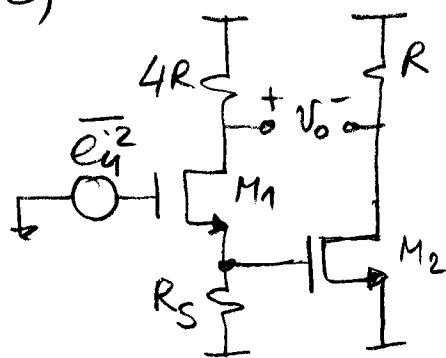


$$\frac{\overline{e_i^2}}{\Delta f} = \frac{8}{3} \frac{KT}{g_m}$$

$$M1: V_{on1} = -\frac{g_{m1} 4R}{1 + g_{m1} R_S} e_{i1}$$

$$V_{on1} = -\frac{g_{m1}}{2} 4R \cdot e_{i1}$$

$$M2: V_{on2} = \frac{g_{m1} R_S}{1 + g_{m1} R_S} \cdot g_{m2} R e_{i1}$$
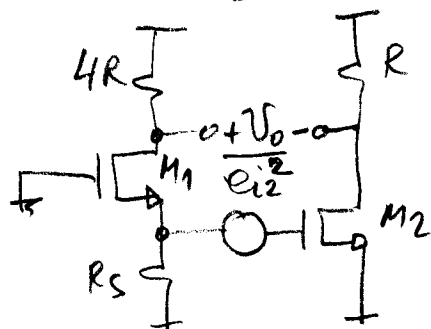
$$V_{on2} = \frac{g_{m1}}{2} 4R e_{i1} \Rightarrow V_{on} = V_{on1} + V_{on2} = 0$$



$$V_{on} = g_{m2} R e_{i2}$$

$$\Rightarrow V_{on}^2 = (4g_{m1} R)^2 \cdot \frac{8}{3} \frac{KT}{4g_{m1}}$$

Šum na izlazu koji potiče od R_S

$$\frac{V_{on}^2}{\Delta f} = 4KTR_S \cdot (4R g_{m1})^2$$

$$\frac{8}{3} \frac{KT}{4g_{m1}} \cdot (4g_{m1} R)^2$$

$$\text{FAKTOR ŠUMA} \cdot F = 1 + \frac{\frac{8}{3} \frac{KT}{4g_{m1}} \cdot (4g_{m1} R)^2}{4KTR_S (4R g_{m1})^2}$$

$$F = 1 + \frac{1}{6} = \frac{7}{6} \circ$$