

## Elementi elektronike – JUL 2018 – REŠENJA

3. DC analiza:

$$I_{D1} = I_{D2} = I_G$$

$$V_i = V_{D2} + R_3 I_G = 1.7V$$

AC analiza:

$$r_{d1} = \frac{V_i}{I_{D1}} = 2.5 \Omega$$

$$r_{d2} = \frac{V_i}{I_{D2}} = 2.5 \Omega$$

$$V_i = (R_4 \parallel (R_3 + r_{d2})) I_g = 336.07 mV$$

$$v_i = V_i \sin(\omega t)$$

Ukupni signal je jednak  $v_i = V_i + v_i$ .

4. a)

$$A_v = \frac{(R_D \parallel R_P) g_m}{1 + g_m R_1 + \frac{R_1}{R_S}}$$

$$R_u = R_1 + \frac{1}{g_m} \parallel R_S$$

b)

$$V_{GS} = 2V$$


$$I_D = 1.5mA$$

$$g_m = \sqrt{2k_n I_D} = 3mS$$

$$A_v = 2.4708$$

$$R_u = 335.71 \Omega$$

7.

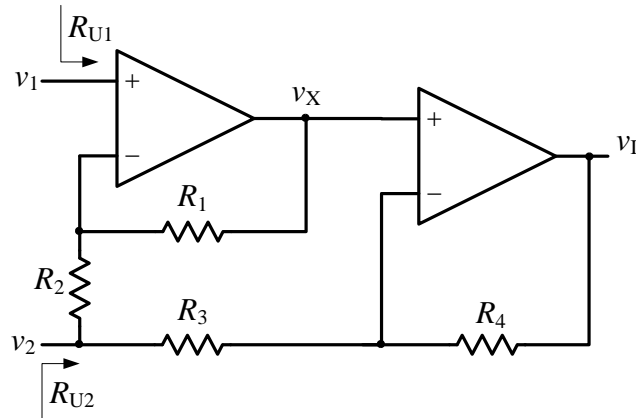


$$v_X = v_1 - R_1 \frac{v_2 - v_1}{R_2} = v_1 \left( 1 + \frac{R_1}{R_2} \right) - \frac{R_1}{R_2} v_2$$

$$v_I = v_X - R_4 \frac{v_2 - v_X}{R_3} = v_1 \left( 1 + \frac{R_1}{R_2} \right) \left( 1 + \frac{R_4}{R_3} \right) - v_2 \left( \frac{R_4}{R_3} + \frac{R_1}{R_2} \left( 1 + \frac{R_4}{R_3} \right) \right)$$


$$R_{U1} = \infty$$

Određivanje  $R_{U2}$ :

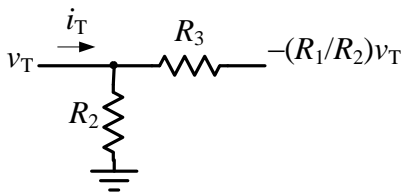


$$R_{U2} = \frac{v_T}{i_T} = R_2 \parallel \frac{R_3}{1 + \frac{R_1}{R_2}}$$

8. a)  $Y = AB + BC + CD$

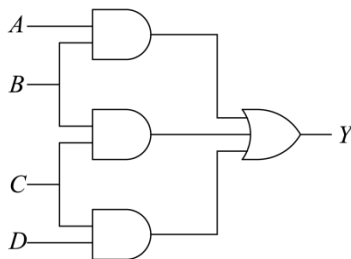


Slika 1. Rešenje tačke pod a).

b)  $Y = AB + BC + CD = \overline{\overline{AB + BC + CD}} = \overline{\overline{AB} \cdot \overline{BC} \cdot \overline{CD}} = \overline{\overline{AB} \cdot \overline{BC} \cdot \overline{CD}}$

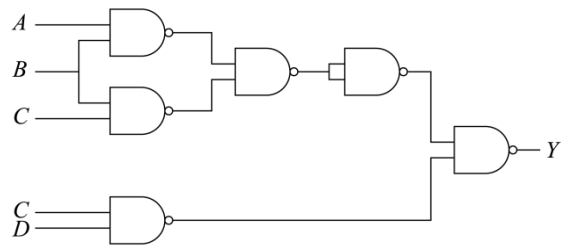

Slika 2. Rešenje tačke pod b)

c)

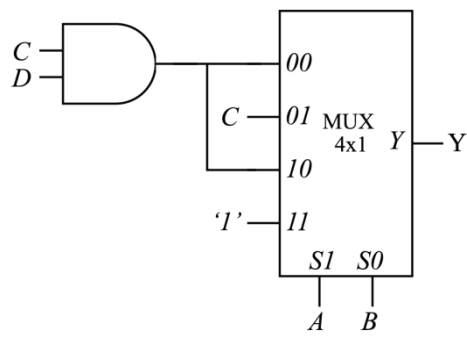

Slika 3. Rešenje tačke pod c).

9. Moduo brojanja brojača je pet.

