

Elementi elektronike – OKTOBAR 2016 - REŠENJA

2. $V_{ut}=9.7\text{V}$, $V_{imax}=10.63\text{V}$, $V_{umin}=-20\text{V}$

3. a)

$$V_{CC} - R_B I_B - V_{BE} - (1 + \beta) I_B R_E = 0$$

$$V_E = (1 + \beta) I_B R_E$$

$$I_B = \frac{V_E}{(1 + \beta) R_E}$$

$$R_B = \frac{V_{CC} - V_{BE} - V_E}{I_B} = 368.65 \text{ k}\Omega$$

b) Na osnovu šeme za male signale prikazane na slici može se pisati:

$$v_p = i_c (R_E \parallel R_P)$$

$$i_c = (1 + \beta) i_b$$


$$i_b = \frac{v_g}{R_X}$$

Lako se izvodi da je: $R_X = r_\pi + (1 + \beta)(R_E \parallel R_P)$

$$R_U = R_X \parallel R_B = (r_\pi + (1 + \beta)(R_E \parallel R_P)) \parallel R_B.$$

Naponsko pojačanje je jednako:
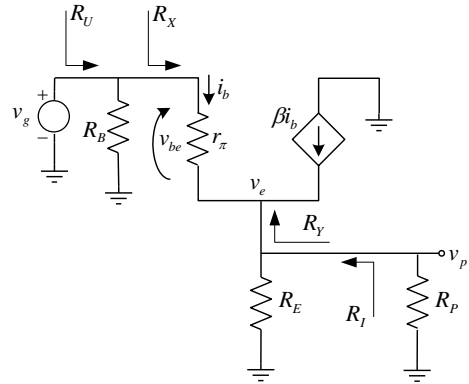
$$A_v = \frac{(1 + \beta)(R_E \parallel R_P)}{r_\pi + (1 + \beta)(R_E \parallel R_P)}.$$



c) Na osnovu poznate struje baze u mirnoj radnoj tački određene pod a) dobija se:

$$I_C = \beta I_B = 1.98 \text{ mA}$$

$$g_m = \frac{I_C}{V_T} = 79.2 \text{ mS}$$

$$r_\pi = \frac{\beta}{g_m} = 1262.5 \Omega$$


Vrednosti traženih parametara su:

$$R_U = 80 \text{ k}\Omega$$

$$A_v = 0.99$$

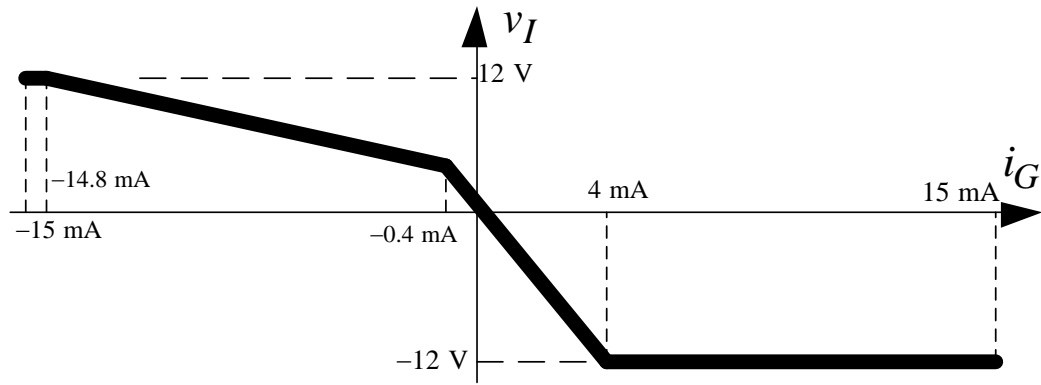6.

$$v_I = \begin{cases} 12 \text{ V} & i_G \leq -14.8 \text{ mA} \\ 0.9 \text{ V} - 750 \Omega \cdot i_G & -14.8 \text{ mA} < i_G \leq -0.4 \text{ mA} \\ -3 \text{ k}\Omega \cdot i_G & -0.4 \text{ mA} \leq i_G < 4 \text{ mA} \\ -12 \text{ V} & i_G \geq 4 \text{ mA} \end{cases}$$





7.

a)

x_3	x_2	x_1	x_0	Y
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	1
0	1	0	1	0
0	1	1	0	1
0	1	1	1	1
1	0	0	0	0
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	1
1	1	0	1	0
1	1	1	0	1
1	1	1	1	1

b)

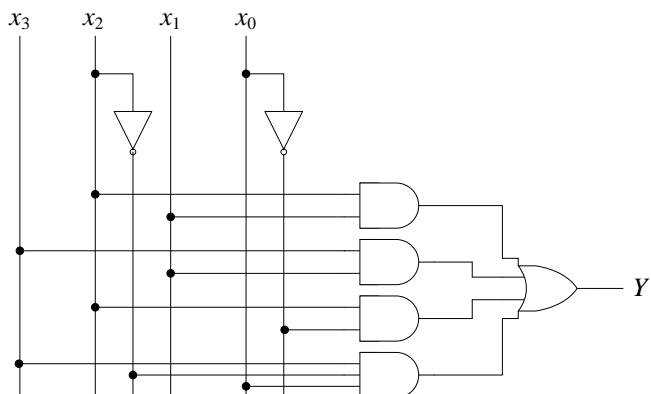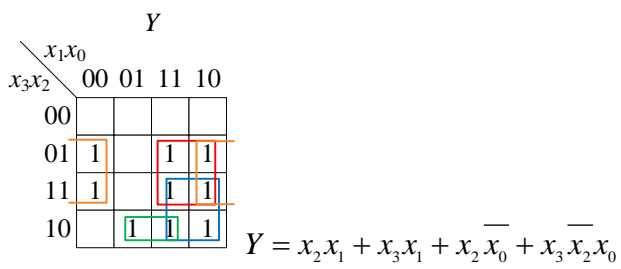

c)

