

REŠENJA ZADATAKA

1. a) $I_{C1} \approx 162\mu A$; $I_{C2} \approx 530\mu A$.

$$b) a = \frac{v_i}{v_s} = \frac{R_2 \parallel \frac{r_{\pi 1}}{\beta_0 + 1}}{R_1 + R_2 \parallel \frac{r_{\pi 1}}{\beta_0 + 1}} g_{m1} [R_3 \parallel (r_{\pi 2} + (\beta_0 + 1)R_4)] \frac{g_{m2} R_4}{1 + g_{m2} R_4} \approx 15.73.$$

$$c) R_{ul} = R_1 + R_2 \parallel \frac{r_{\pi 1}}{\beta_0 + 1} \approx 100\Omega; \quad R_{izl} = R_4 \parallel \frac{r_{\pi 2} + R_3}{\beta_0 + 1} = 70\Omega.$$

4.

$v_I[V] = 12V$, za $-12V \leq v_G \leq -4.8V$ (IOP-poz. zasićenje, D_1 -OFF, D_2 -ON);

$v_I[V] = -2v_G[V] + 2.4$, za $-4.8V \leq v_G \leq -1.2V$ (IOP- lin. režim, D_1 -OFF, D_2 -ON);

$v_I[V] = -4v_G[V]$, za $-1.2V \leq v_G \leq 1.2V$ (IOP-lin. režim, D_1 -OFF, D_2 -OFF);

$v_I[V] = -2v_G[V] - 2.4$, za $1.2V \leq v_G \leq 4.8V$ (IOP-lin. režim, D_1 -ON, D_2 -OFF);

$v_I[V] = -12V$, za $4.8V \leq v_G \leq 12V$ (IOP-neg. zasićenje, D_1 -ON, D_2 -OFF).